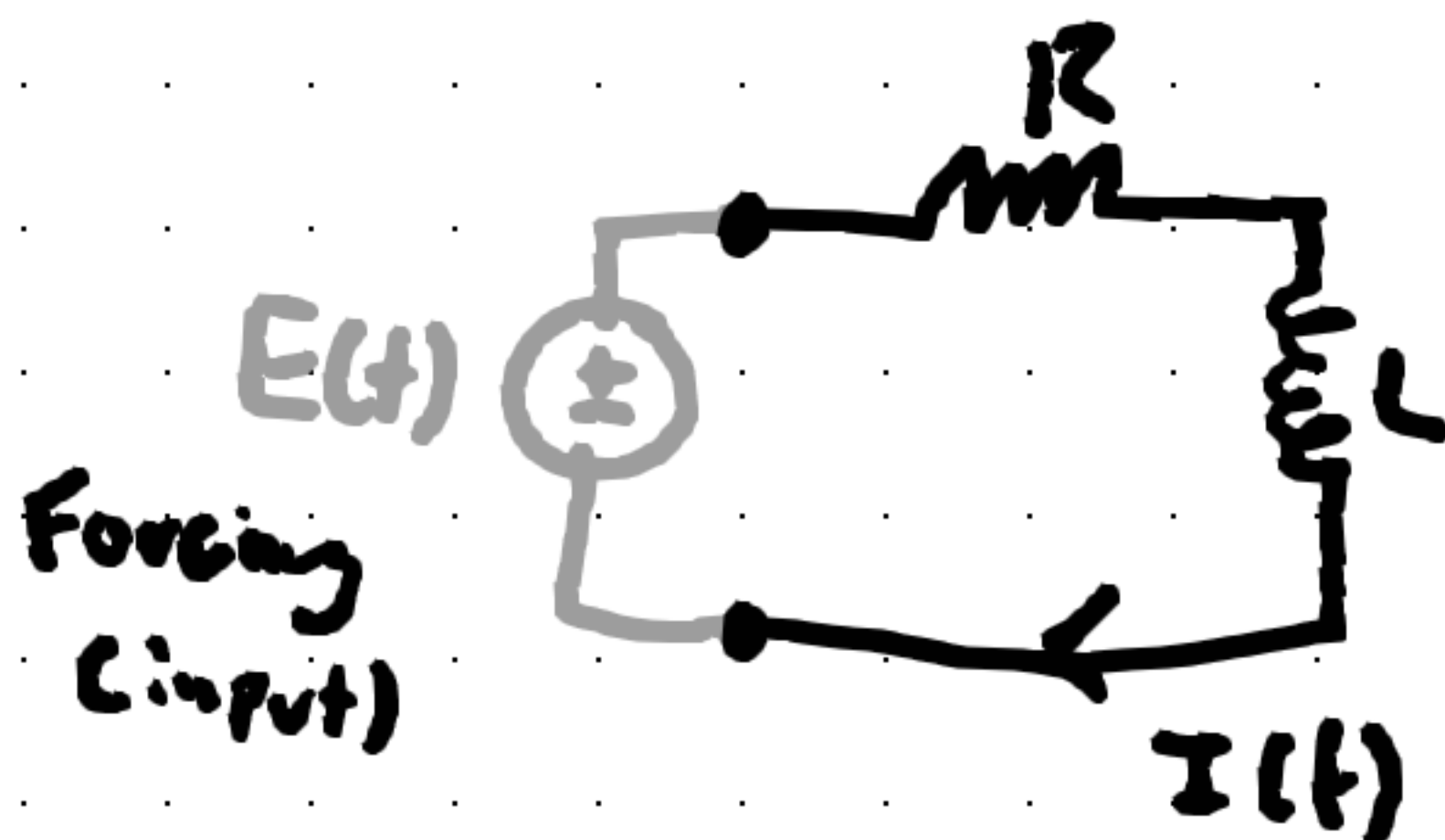


First order LTI Systems

Consider a Series RL Circuit with a voltage supply $E(t)$:



• These R 's and L 's are our parameters in differential Equations

Response (output)

In DE, we take a sitting system, and drive them with an input. We then get a corresponding output.

From KVL, we have the model

$$\underbrace{L \frac{dI}{dt} + RI}_{\text{LTI "System"}}$$

$= \underbrace{E(t)}_{\text{Forcing}}$

Linear

Model only involves linear terms in I

$$I, \frac{dI}{dt}, \frac{dI^2}{dt}$$

Time-Invariant ("constant coefficient")

Parameters are static in time

No matter if I power on circuit at $8am$, or $8pm$, it will be the same.

Assume DC Voltage Source

$$E(t) = E_0$$

and initial conditions

$$I(0) = I_0$$

$$\dot{I} = \frac{dI}{dt}$$

$$L\dot{I} + RI = E_0, \quad I(0) = I_0$$


State Space

The state of the system at time t is given by $(I(t), \dot{I}(t))$

If we re-arrange our DE,

$$\dot{I}(t) = \frac{E_0}{L} - \frac{R}{L} I(t)$$

State Space Diagram

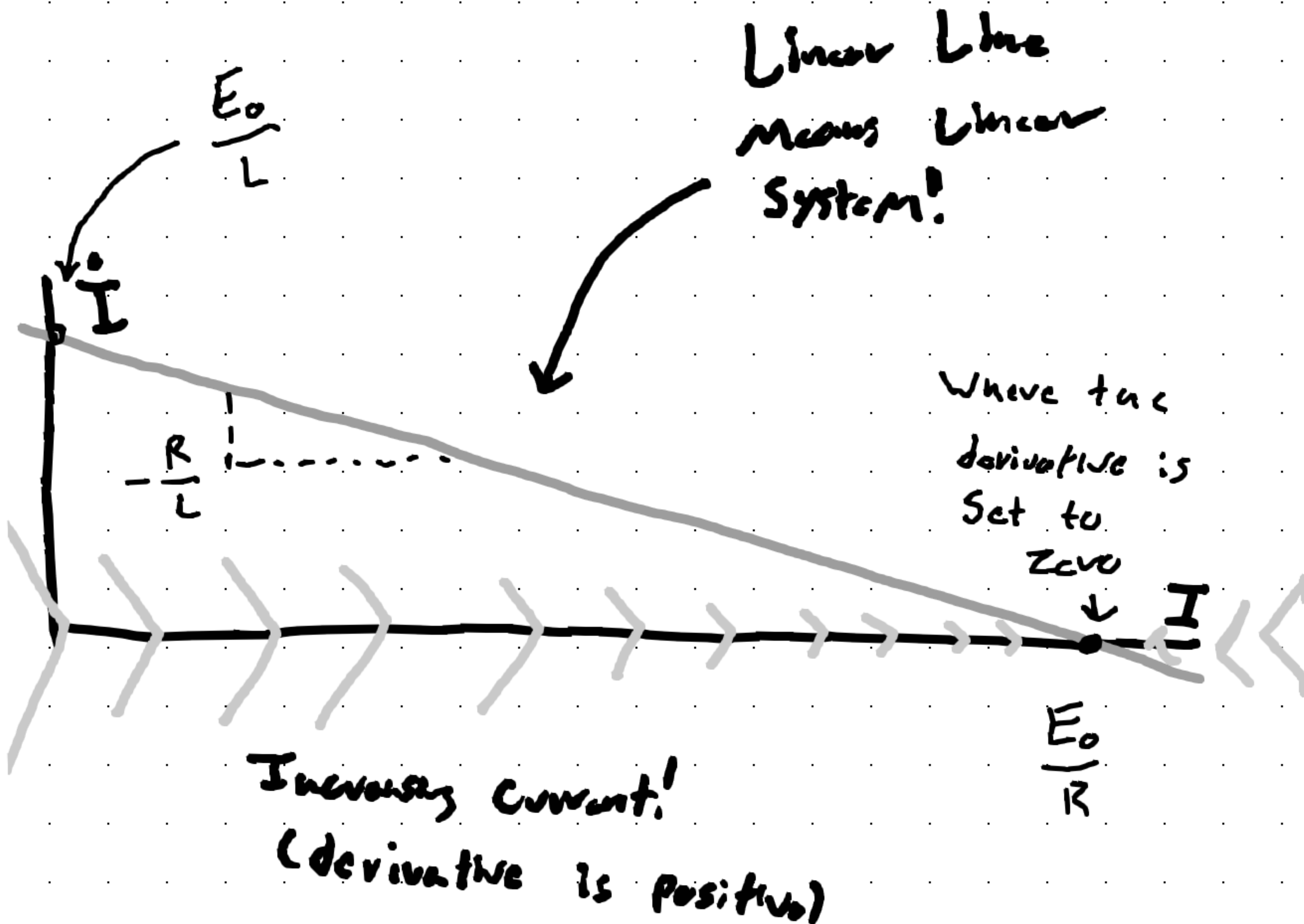


$I = \frac{E_2}{R}$ is a **Stable Fixed point** of the system.

↑
The zero point on the graph

(i) Fixed point $\dot{I} = 0 \rightarrow$ **No change in I.**
 \rightarrow System in **Steady State**

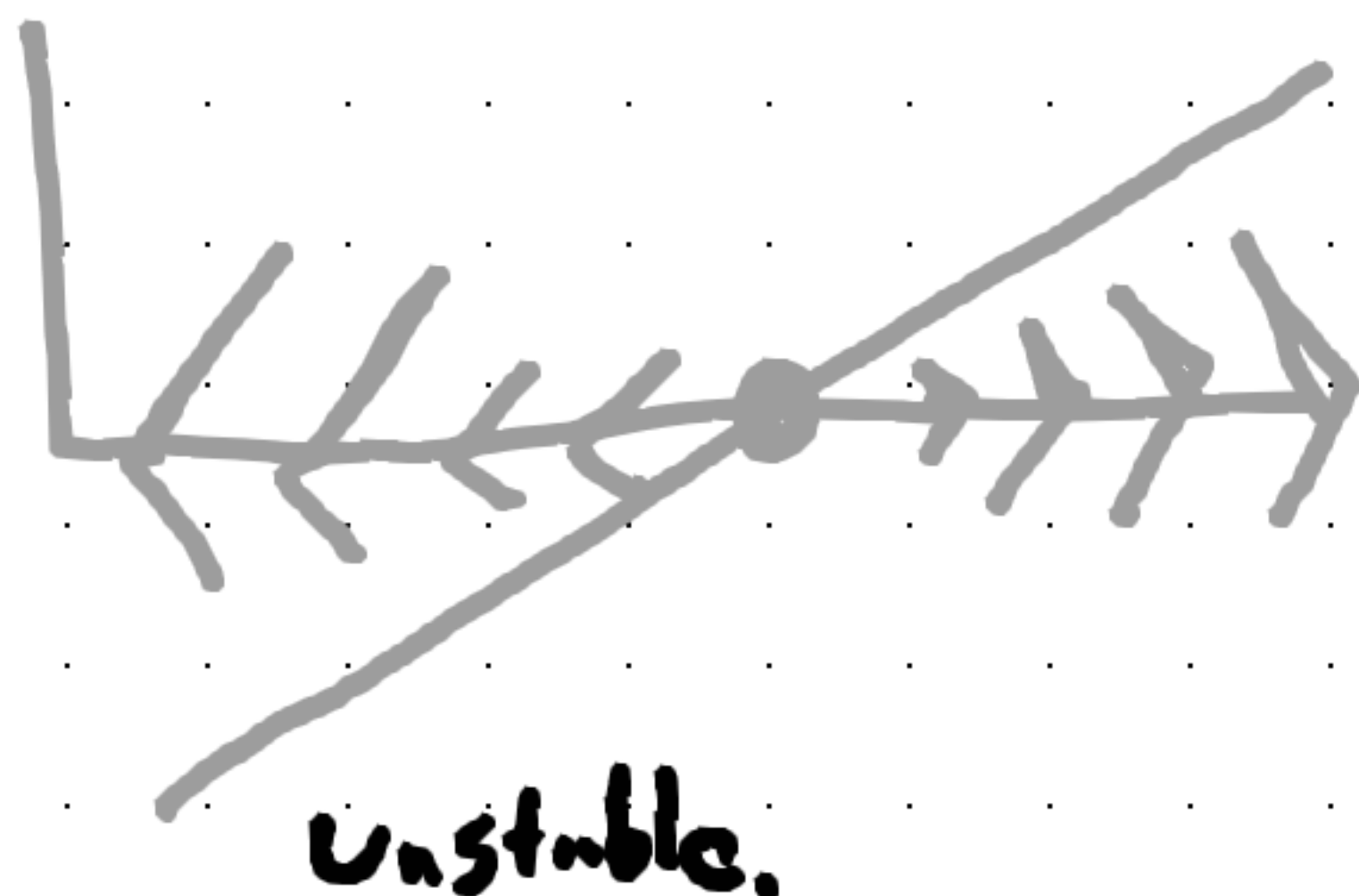(ii) Stable: The system is attracted to this fixed point

\hookrightarrow This system can be unstable
This means it is repelled from the point.



Money is unstable for instance!

Now, let's Solve this dE!

We are searching for some current that makes

$$L\dot{I} + RI = E_0$$

True!

(This is hard!)

Method of undetermined coefficients (MUC)

$$L\dot{I} + RI = E_0, \quad I(0) = I_0$$

1. Get homogeneous solution I_h (natural response)

$$L\dot{I}_h + RI_h = 0$$

↑ Zero forcing.

(What happens if we do nothing to the system?)

Exponentials are really good for first order LTI Systems!

They grow and decay exponentially!

Assume $I_h = C e^{\lambda t}$

↑ Free Coefficient

differentiating

$$\dot{I}_h = \lambda C e^{\lambda t}$$

Eigenvalue

Eigenfunction

We got the same thing! This is why this works!

Any multiple of the Eigenfunction is the same!

Plugging back in...

$$L(\lambda C e^{\lambda t}) + R(C e^{\lambda t}) = 0$$

$$C e^{\lambda t} (L\lambda + R) = 0$$

This is
the

Characteristic
Equation



$$L\lambda + R = 0$$

$$\lambda = -\frac{R}{L}$$

~~~~~

$$I_h = C e^{-\frac{R}{L} t}$$

↑ rate [S<sup>-1</sup>]

↙ Stable

This is a decaying  
Exponential

This because time is linear!  
You cannot have time in an  
exponential.

Is also

$$I_h \propto e^{-t/\tau}$$

↑ PTC ↓

# Process Time Constant

$$\tau = \frac{L}{R}$$

↑  
[S]

→ This characterizes the speed of the system's response.

$$L\dot{I} + RI = E_0$$

$$\tau\dot{I} + I = \frac{E_0}{R}$$

[S] [A/s] [A]      [A]

## 2. Get Particular Solution

$$L\dot{I}_p + RI_p = E_0$$

(This is kind of the same, but without the  $+C$  from the homogeneous)

Linear systems mimic their forcings.

Have we had...

Constant forcing  $E_0 \Rightarrow$  Constant Response  $I_p = D$

↑  
Undetermined Coefficient.

So now we have...

$$L(0) + RD = E_0$$

$$D = \frac{E_0}{R}$$

$$I_p = \frac{E_0}{R}$$

... Hey... This looks like our fixed point on the graph...

### 3. Satisfy Initial Condition

$$I(0) = I_0$$

$$L \dot{I} + RI = E$$

$$L(\dot{I}_p + \dot{I}_h) + R(I_p + I_h) = E_0 + 0$$

- A mix of the particular, and homogeneous system!

$$I = I_h + I_p$$

$$I(t) = C e^{-\frac{R}{L}t} + \frac{E_0}{R}$$

$$I(0) = C e^{-\frac{R}{L}(0)} + \frac{E_0}{R}$$

$I_0$                        $1$


$$C = I_0 - \frac{E_0}{R}$$

$$I(t) = \left(I_0 - \frac{E_0}{R}\right) e^{-\frac{R}{L}t} + \frac{E_0}{R}$$

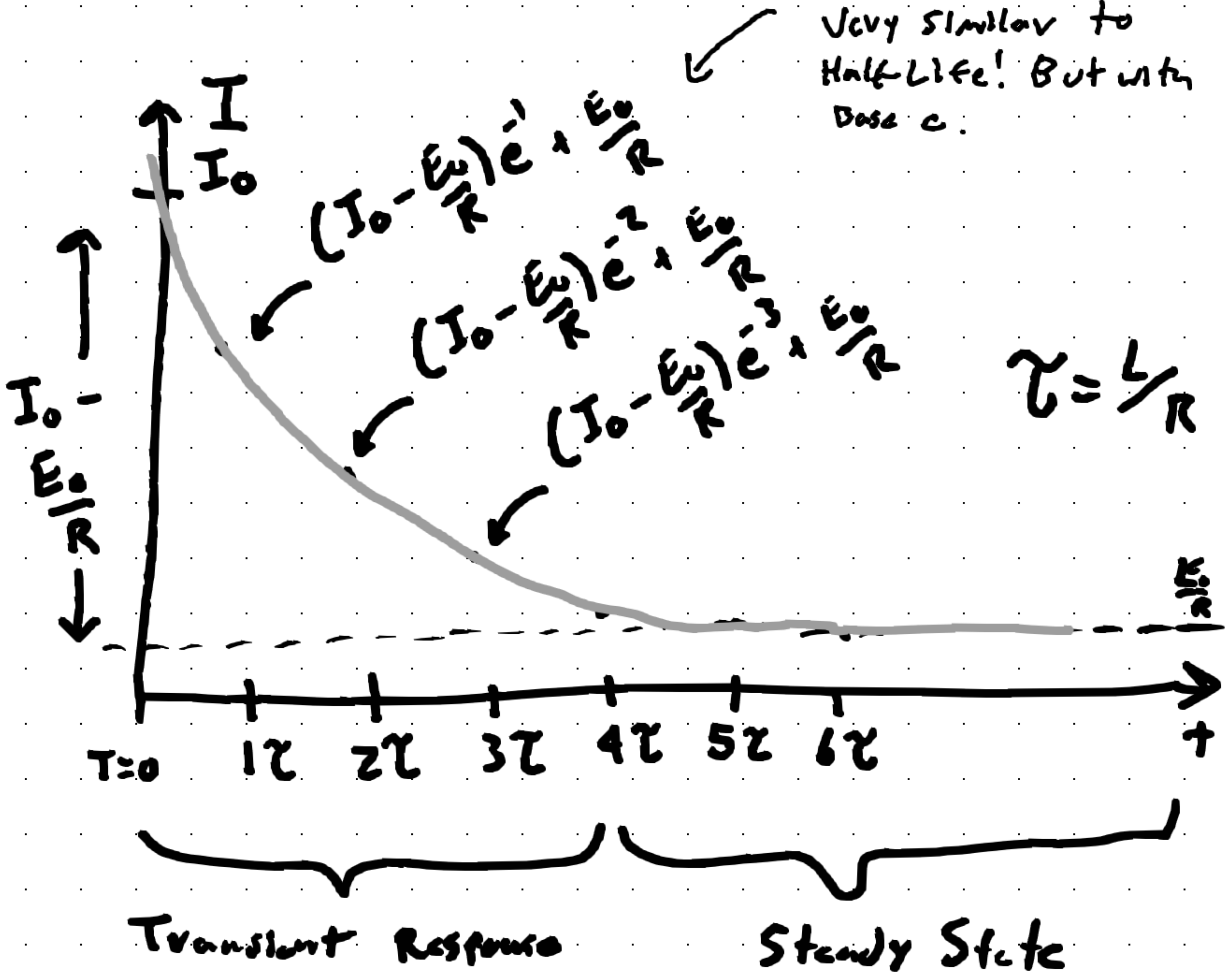4. Sketch  $I(t)$   $I(t) = (I_0 - \frac{E_0}{R})e^{-\frac{R}{L}t} + \frac{E_0}{R}$

$T \geq 3\tau$ ,  $I(t) = I_p$ , response in Steady State.

This is known as e-folding. Very similar to Half-Life! But with Dose  $e$ .




This is really just a decaying exponential! Shifted up.

$$I(t) = \underbrace{\left(I_0 - \frac{E_0}{R}\right) e^{-\frac{R}{L}t}}_{\text{Transient Response}} + \underbrace{\frac{E_0}{R}}_{\text{Steady Response}}$$

Just about  $3\tau$ , the system has  
no memory of its initial state.
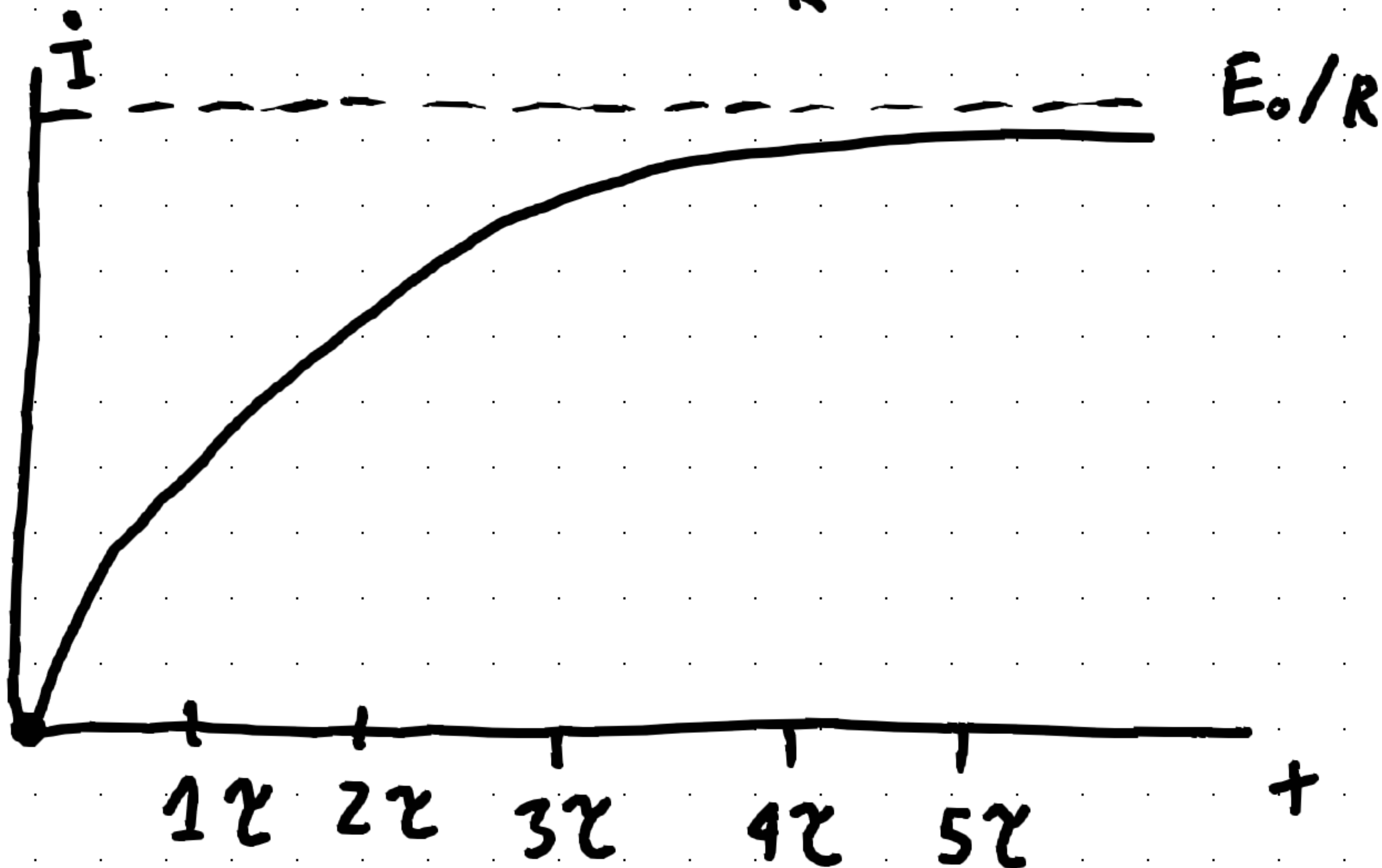
$$I_0 = 0 \quad I(t) = \frac{E_0}{R} (1 - e^{-\frac{R}{L}t})$$



| $t$     | $I(t)$       |
|---------|--------------|
| $1\tau$ | $0.63 E_0/R$ |
| $2\tau$ | $0.86 E_0/R$ |
| $3\tau$ | $0.95 E_0/R$ |
| $4\tau$ | $0.98 E_0/R$ |
| $5\tau$ | $\sim E_0/R$ |


The first three rows (1τ to 3τ) are grouped by a bracket and labeled "Transient".  
 The last two rows (4τ to 5τ) are grouped by a bracket and labeled "Steady State".

$$\underbrace{Li}_{\text{Voltage drop across inductor}} + \underbrace{RI}_{\text{Voltage drop across resistor}} = \underbrace{E_0}_{\text{Total voltage to allocate across L and R}}$$

Voltage drop across inductor

Voltage drop across resistor.

Total voltage to allocate across L and R

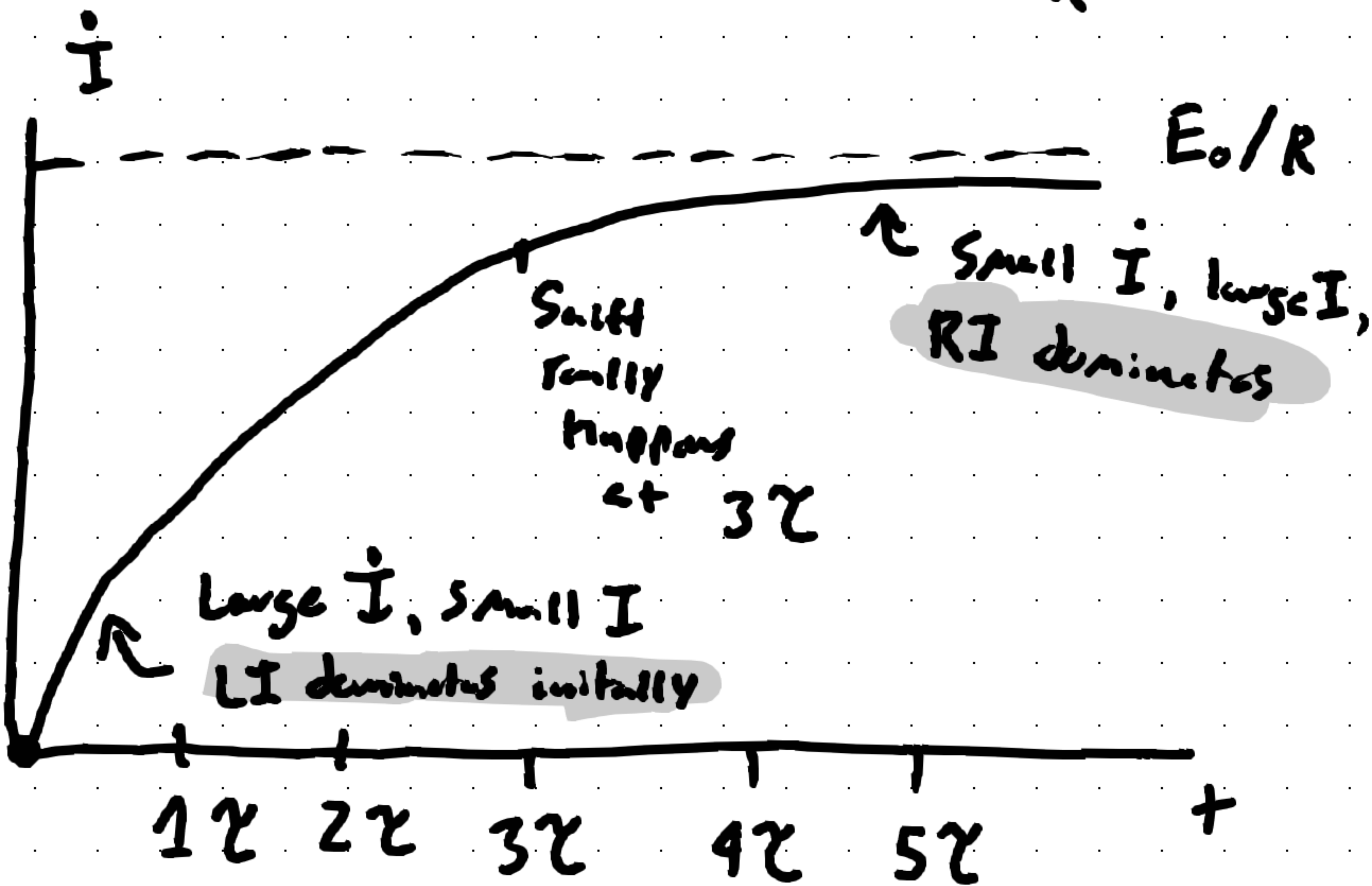



So initially, the total voltage is being used by mostly the inductor!

Whereas just  $3\tau$ , or at a later time the resistor dominates.

At small time:

$$e^u = 1 + u$$

$$I(t) \approx \frac{E_0}{R} \left[ 1 - \left( 1 - \frac{R}{L} t \right) \right]$$

near  
 $u=0$

$$\approx \frac{E_0}{L} t \quad \text{linear approximation}$$