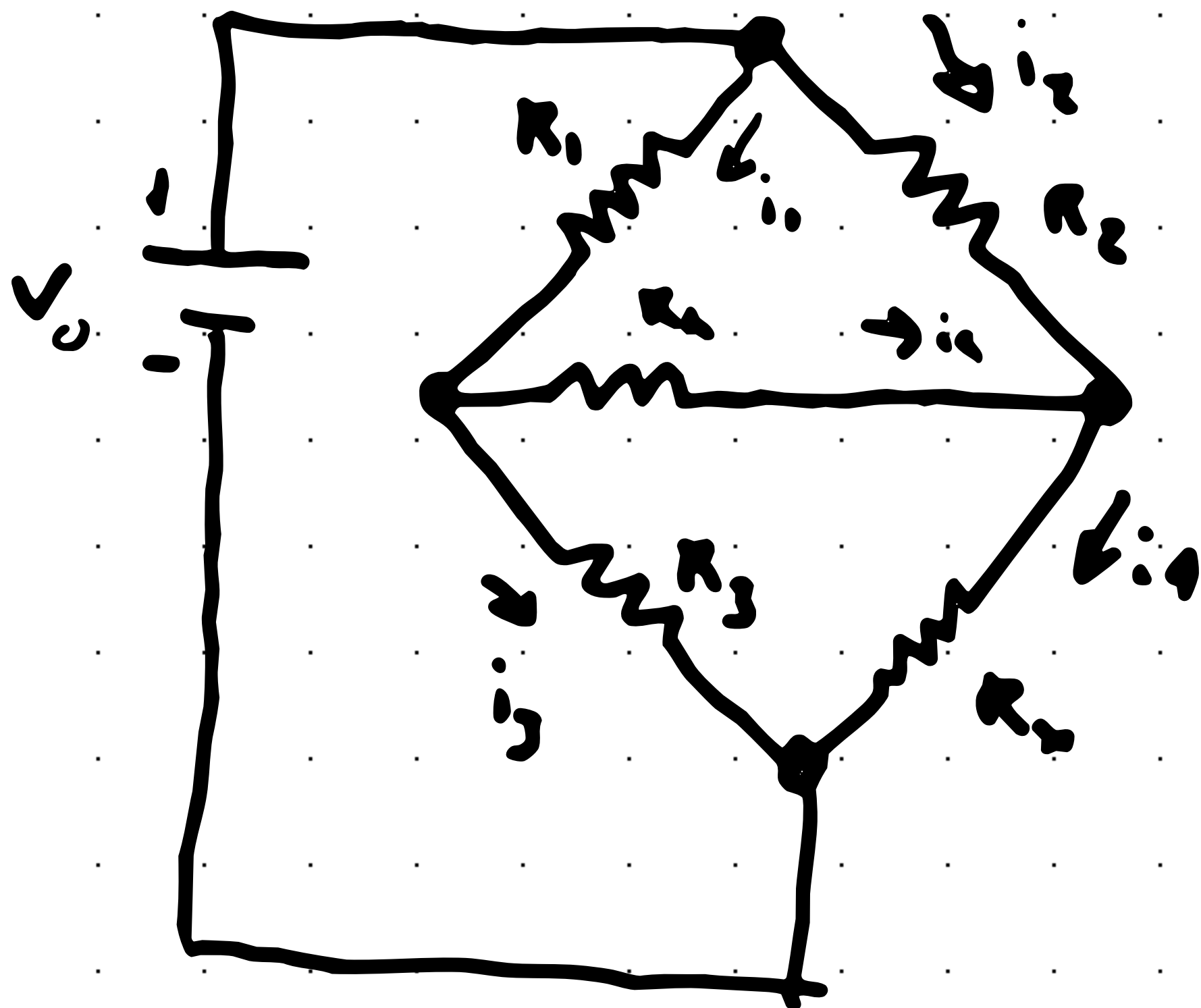


# Tutorial 3 Solutions

ECED2000

a) If  $R_1 = 1\Omega$  and  
 $R_2 = 2\Omega$  and  
 $R_x = 3\Omega$  what value  
should  $R_3$  be adjusted  
so as to ensure a  
balanced condition?



a) Use <sup>Wheatstone</sup> Bridge equation

$$R_x R_1 = R_2 R_3$$

$$(3)(1) = (2)R_3$$


$$R_3 = \frac{3}{2} = 1.5\Omega$$

b) If  $V_0 = 6V$ ,  $R_1 = 0.1\Omega$  and  $R_x$  is a variable  
to be  $3.01\Omega$ , what would be reading on the  
ammeter?

KVL and KCL will

do here

# Mesh Analysis

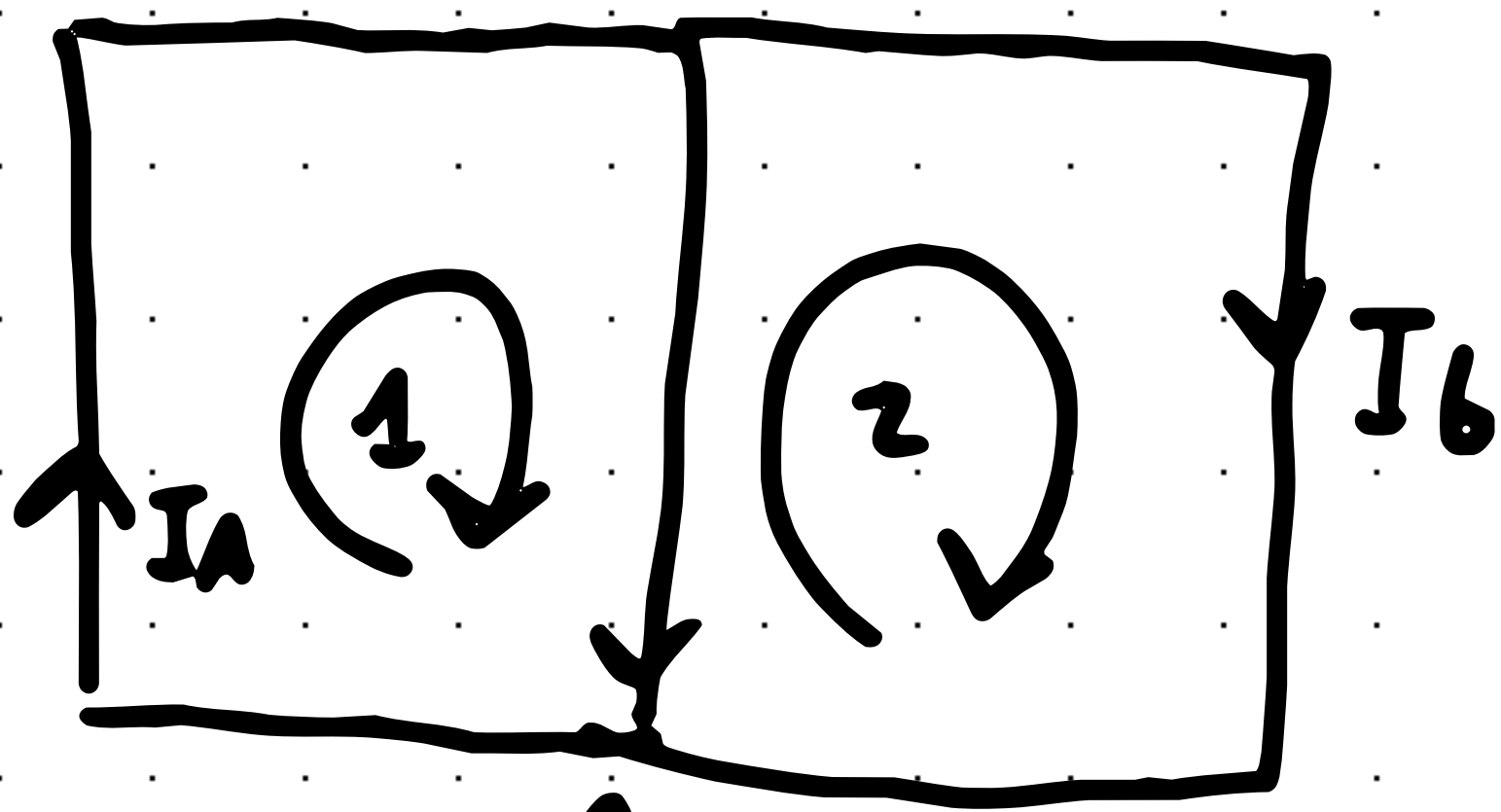


This would be  
 $I_A - I_B!$

- Both loops have to be going the same way!
- Fundamentally very similar to KCL and KVL.
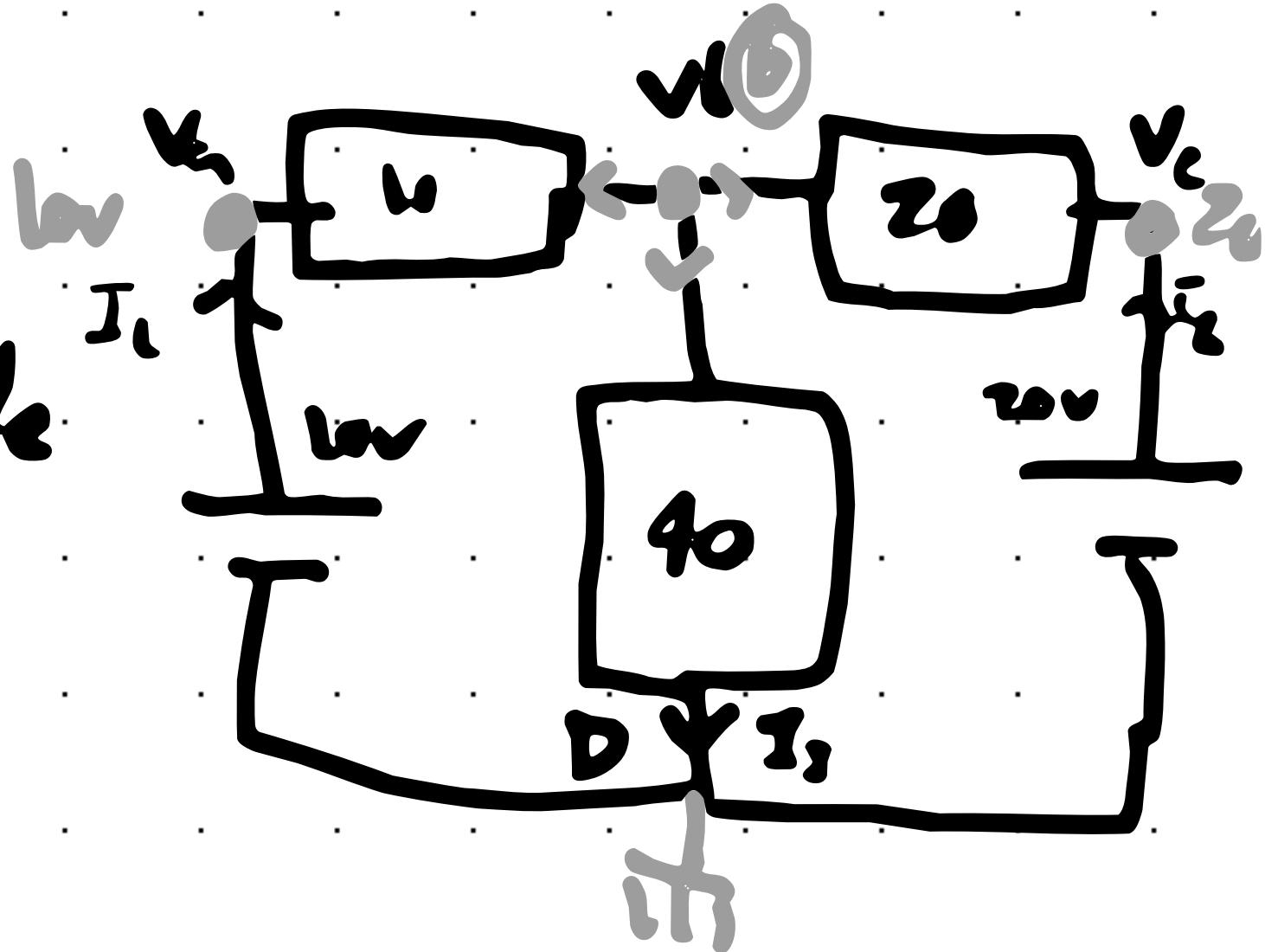
## Problem 2

Calculate  $I_1$ ,  $I_2$ ,  $I_3$  and calculate the total power dissipated.



### Node Analysis

$$\sum I = 0 \quad \frac{V_6 - 10}{10} + \frac{V_6 - 20}{20} + \frac{V_6}{40} = 0$$

Node B


$$V_6 = \frac{80}{7} \text{ V}$$

$$V = IA$$

$$I_1 = \frac{10 - \frac{80}{7}}{10} = -0.14 \text{ A}, \quad I_2 = \frac{20 - \frac{80}{7}}{20} = 0.43 \text{ A}$$

$$I_3 = \frac{V_6}{40} = \frac{\frac{80}{7}}{40} = \frac{2}{7} \text{ A}$$

Now, do it with Mesh Analysis

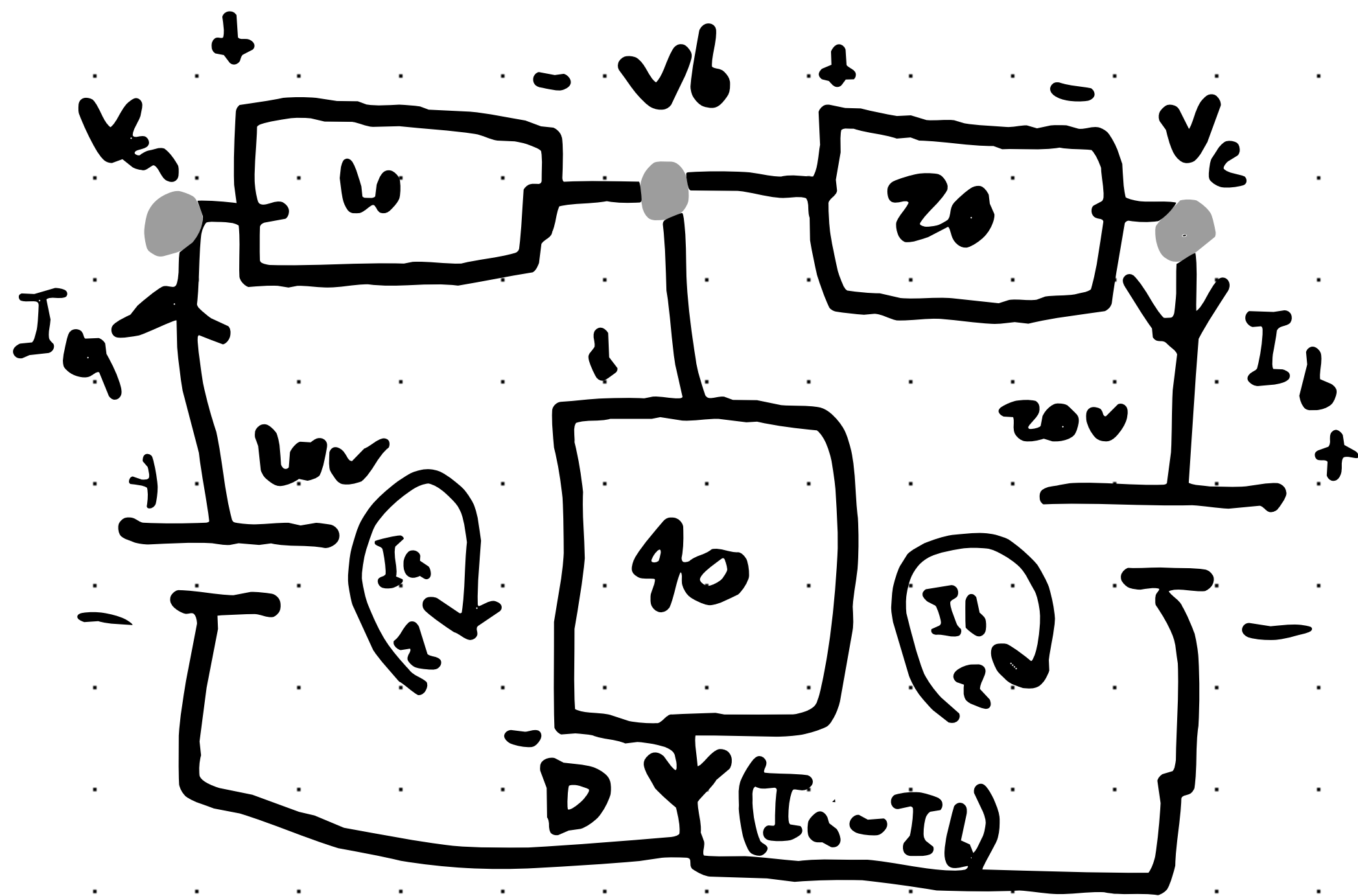

$$\sum V = 0$$

Mesh 1

$$10 - 10I_a - 40(I_a - I_b)$$

①

$$\sum V = 0$$


Mesh 2

$$40(I_a - I_b) - 20I_b - 20 = 0$$

②
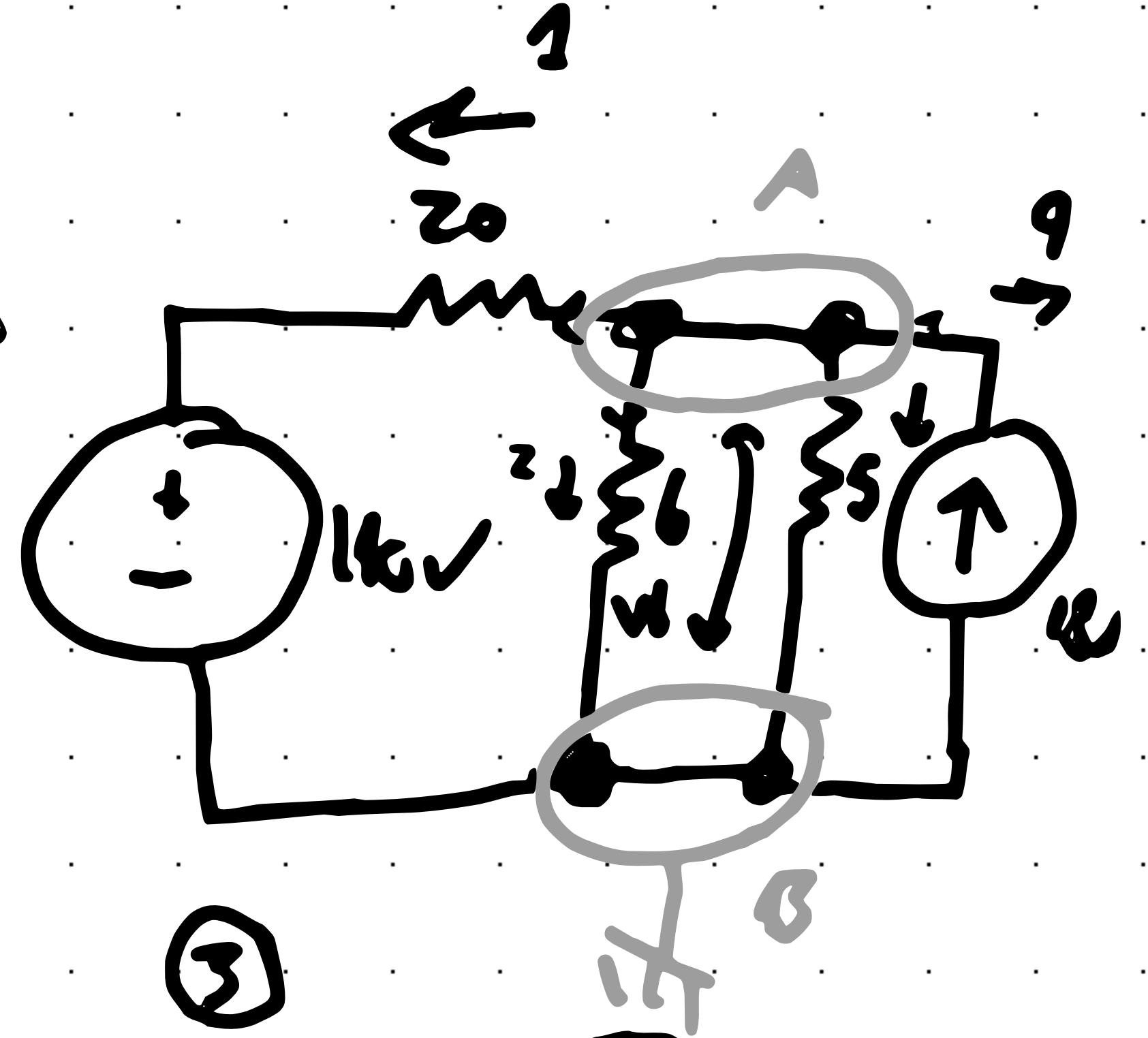
### Question 3

Use node analysis to calculate  $V_b$  and the current in  $Z_0 \Omega$




$$\sum I = 0 \text{ Node A}$$
$$\textcircled{1} \frac{V_b - 140}{Z_0} + \textcircled{2} \frac{V_b}{6} + \textcircled{3} \frac{V_b}{5} + \textcircled{4} (-18) = 0$$

$$V_b = 60V$$
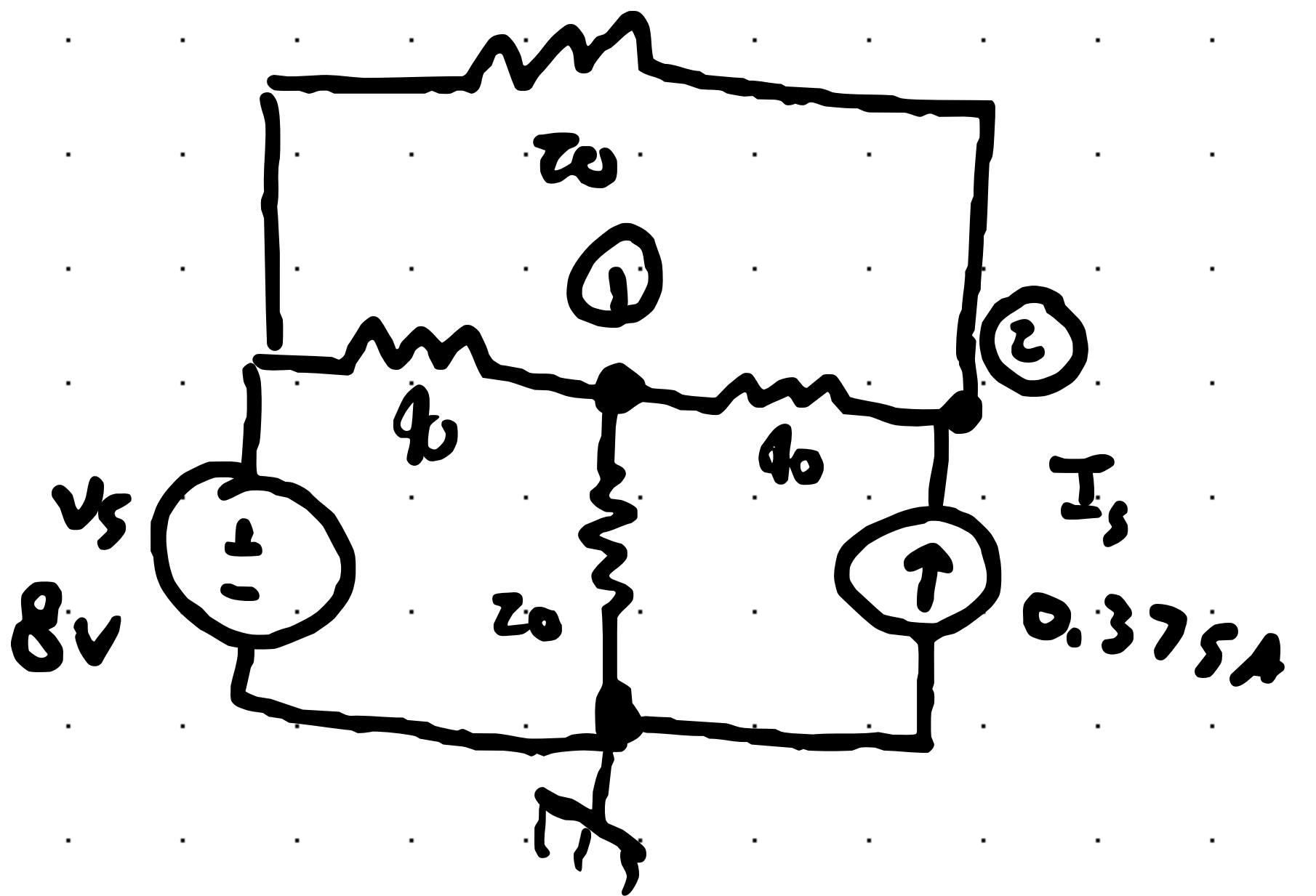
# Question 4

Use the loop voltage method to calculate the current in  $R_1$  and  $R_3$ .



$$\sum I = 0 \quad \text{Node 1} \quad \frac{V_1 - 8}{40} + \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{40}$$

$$\sum I = 0 \quad \text{Node 2} \quad \frac{V_2 - V_1}{40} + \frac{V_1 - 8}{20} + (-0.375) = 0$$

$$V_1 = 5V$$

$$V_2 = 12V$$


$$I_1 = \frac{8 - 5}{40} = \frac{3}{40} A$$

$$I_2 = \frac{V_2 - V_1}{40} = \frac{12 - 5}{40} =$$

$$0.175A$$

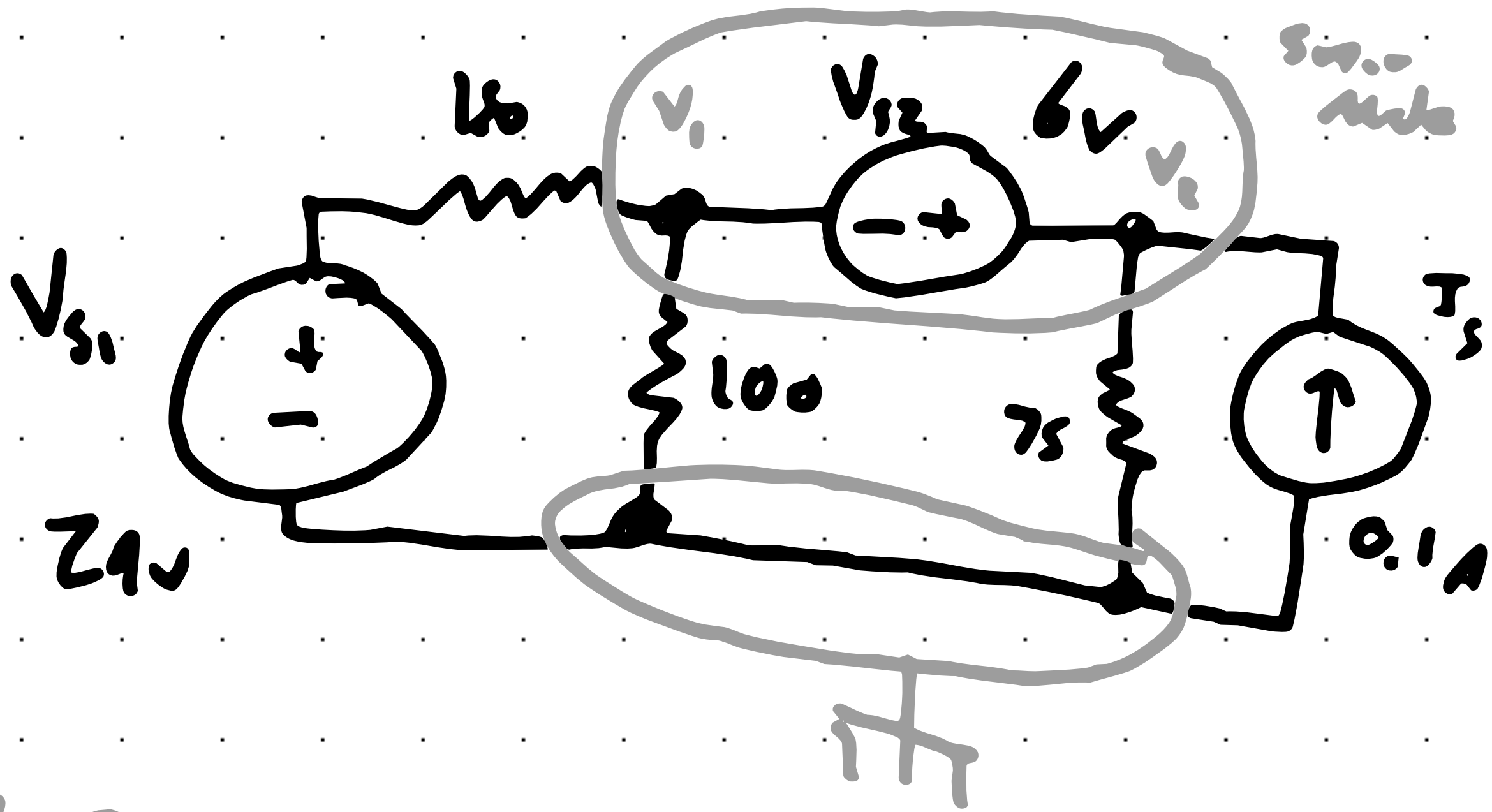Q5

Calculate the current in  $R_1$  and  $R_2$  using nodal analysis.



$$\sum I = 0 \quad \frac{v_1 - 24}{150} + \frac{v_1}{100} + \frac{v_2}{75} + (0.1) = 0 \quad (1)$$

$$v_2 - v_1 = 6V, \quad v_2 = 6 + v_1 \quad (2)$$

Sub eqn 2 into eqn 1

$$\frac{v_1 - 24}{150} + \frac{v_1}{100} + \frac{6 + v_1}{75} - 0.1 = 0$$

$$v_1 = 6V$$

$$v_2 = 6 + v_1 = 12V$$

$$I_1 = \frac{24 - 6}{150} = \frac{18}{150} A$$

$$I_2 = \frac{v_2}{75} = \frac{12}{75} A$$