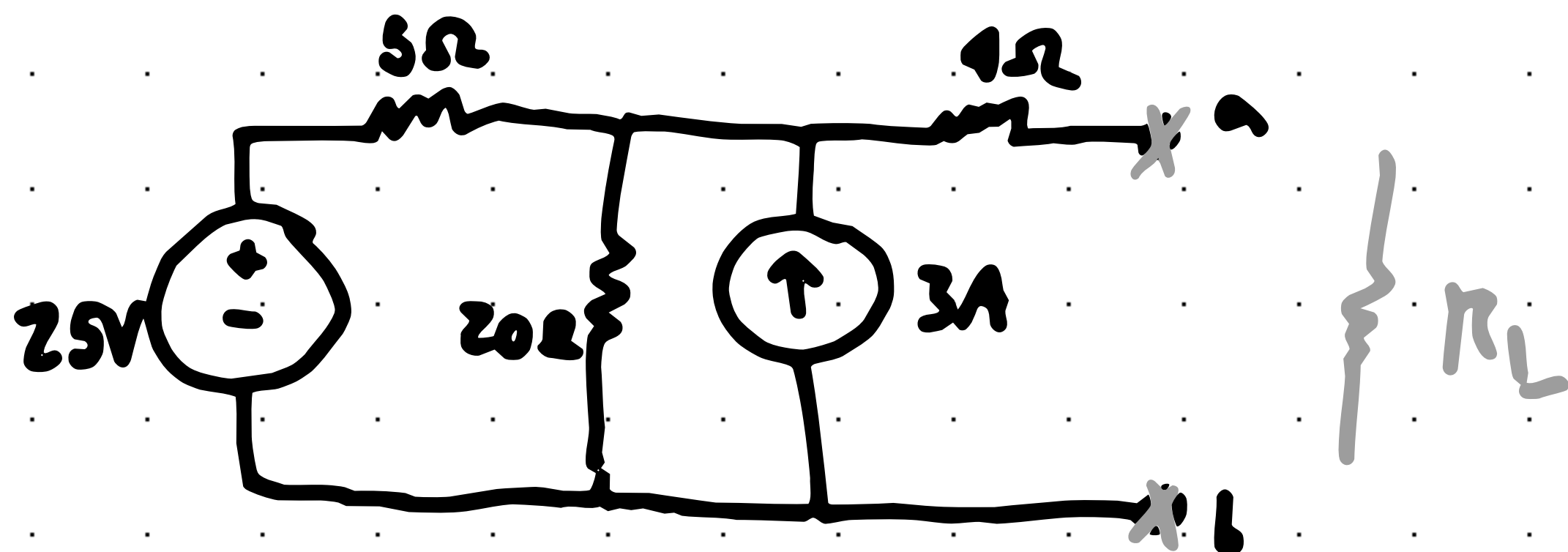



Thevenin and Norton's equivalents problem

Ex. Find Thevenin and Norton equivalent between a and b for the following circuits



Calculate the value of R_L for max power and max power

Soln V_{oc}

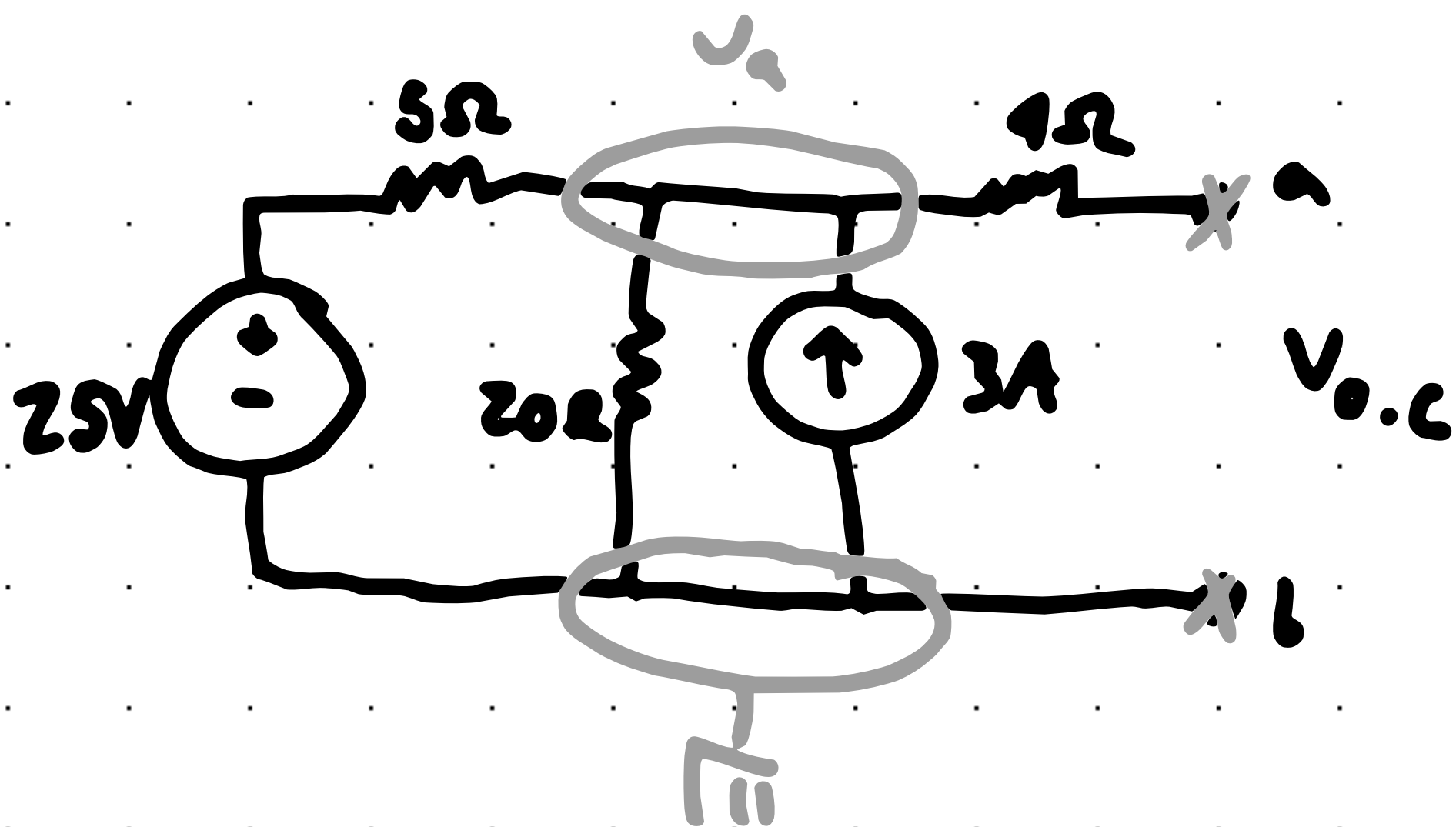


$$\frac{V_a - 25}{5} + \frac{V_a}{20} - 3 = 0$$

$$V_a = 32 \text{ V}$$

$$V_{o.c} = V_a = V_{TH} = 32 \text{ V}$$

To Calculate I_N

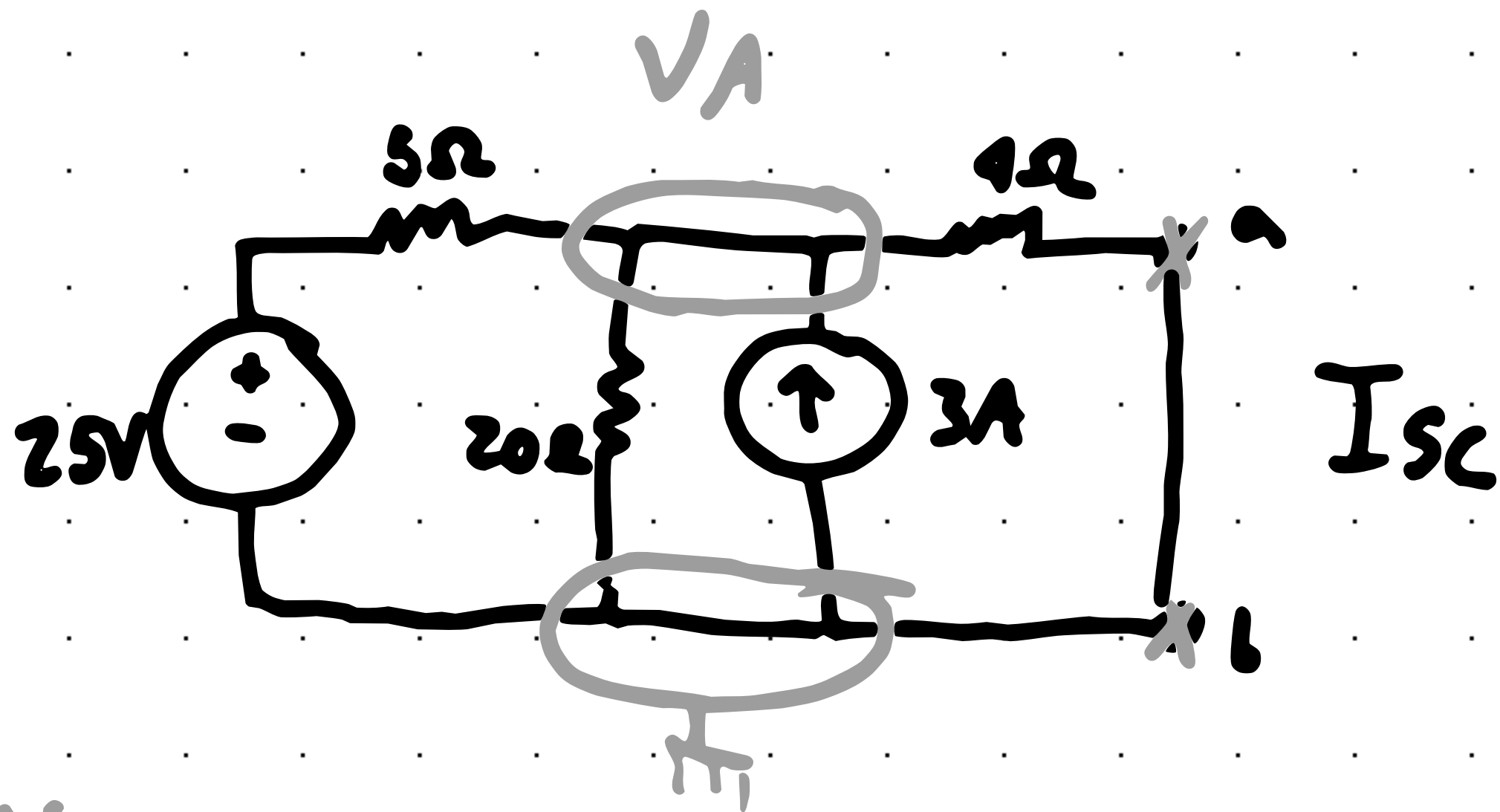

$$I_{sc} = \frac{V_a}{4}$$

$$\frac{V_a - 25}{5} + \frac{V_a}{20} + (-3) + \frac{V_a}{4} = 0 \quad V_a = 16V$$

$$I_{sc} = \frac{16}{4} = 4A$$


$$I_N = I_{sc} = 4A$$

Calculating R_{TH}

$$R_{TH} = \frac{V_{TH}}{I_N} = \frac{32}{4} = 8\Omega$$

Another Method for R_{Th}


Remove
Independent
Sources

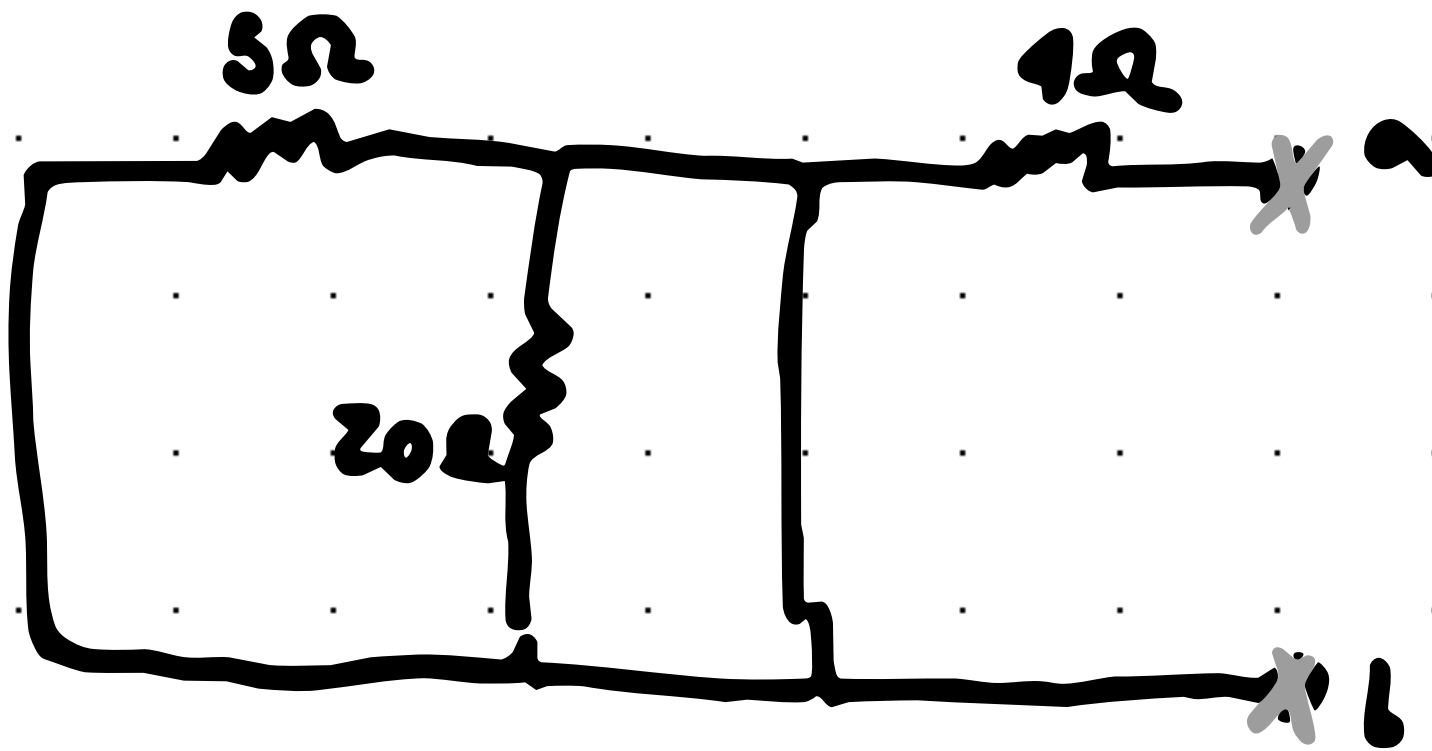


$$R_{eq} = 5 // 20 + 4$$

$$R_{eq} = 8\Omega$$

Thévenin Equivalent

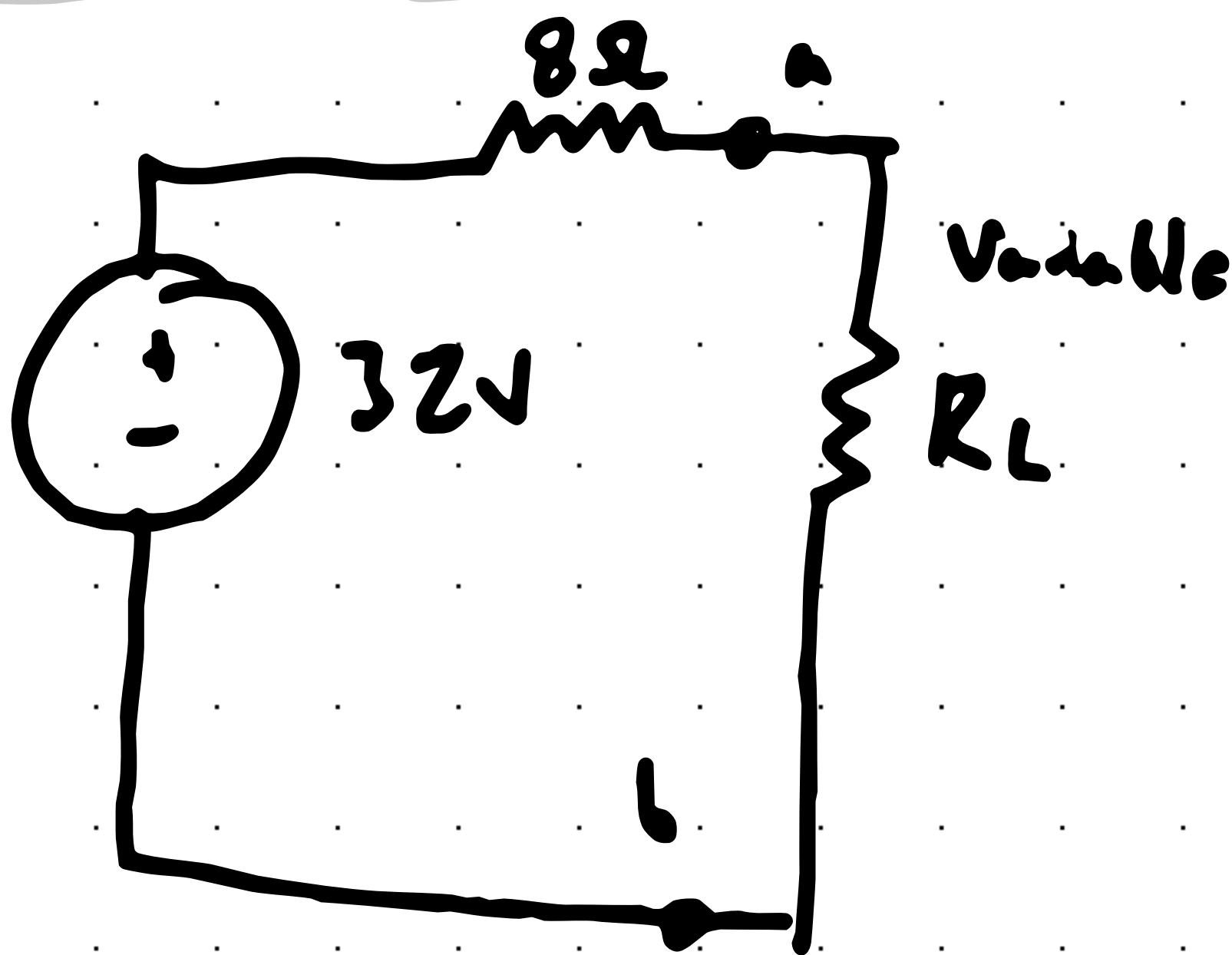

Norton Equivalent

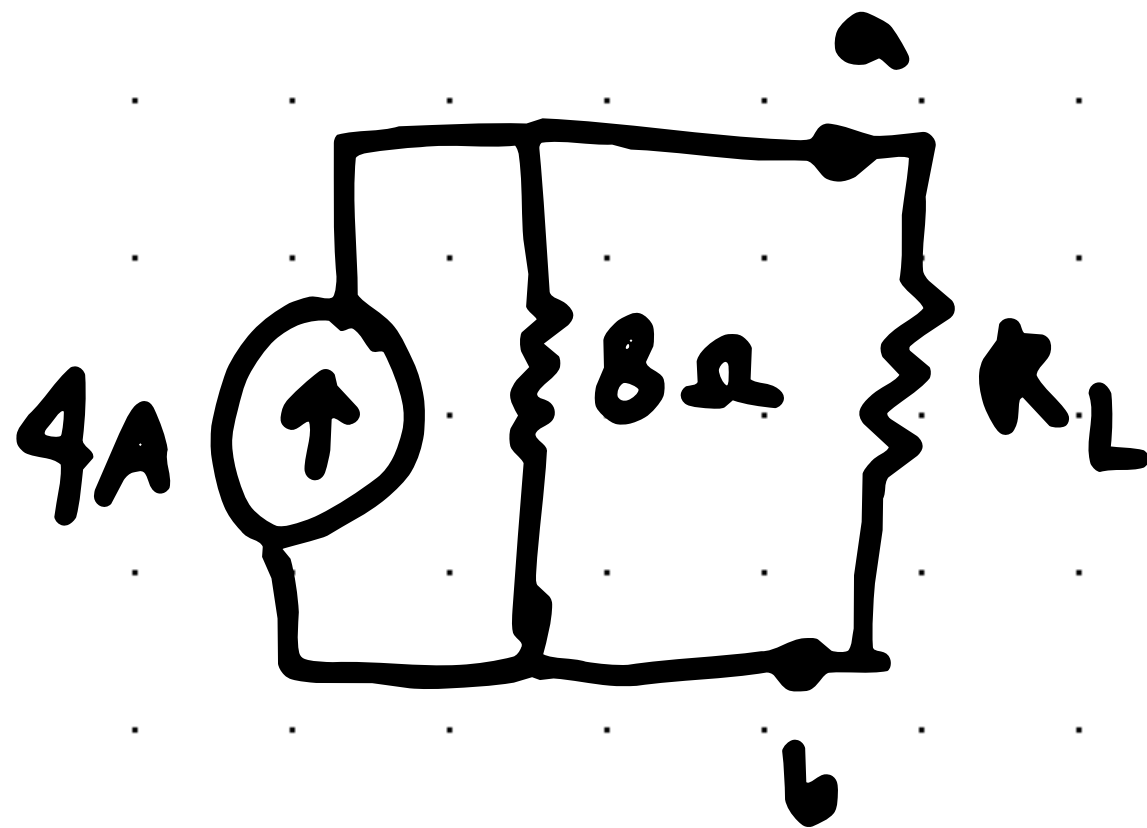


For Max Power

$$R_L = R_{Th} = 8\Omega$$

$$P_{RL} = I^2 R = \left(\frac{3}{8+8} \right)^2 8 \text{ Watts}$$

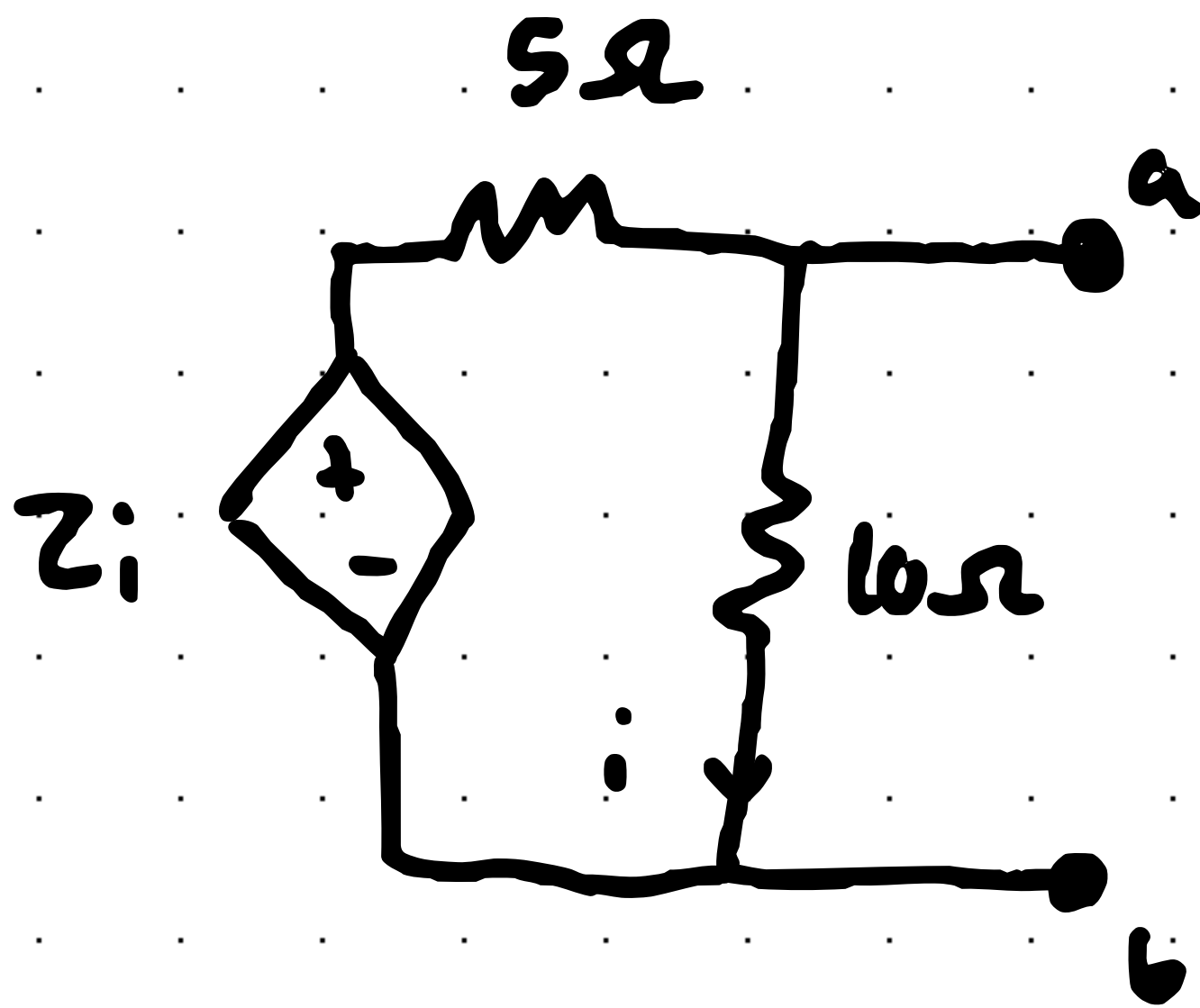Example 2 Find Thevenin and Norton equivalents between a and b.



SOL

$$V_{o.c} = 10i$$

$$\sum V = 0$$

loop ①

To Calculate V_{TH}

$$z_i - 5i - 10i = 0$$


$$-13i = 0$$

$i = 0?$

What?

How does this

make sense?

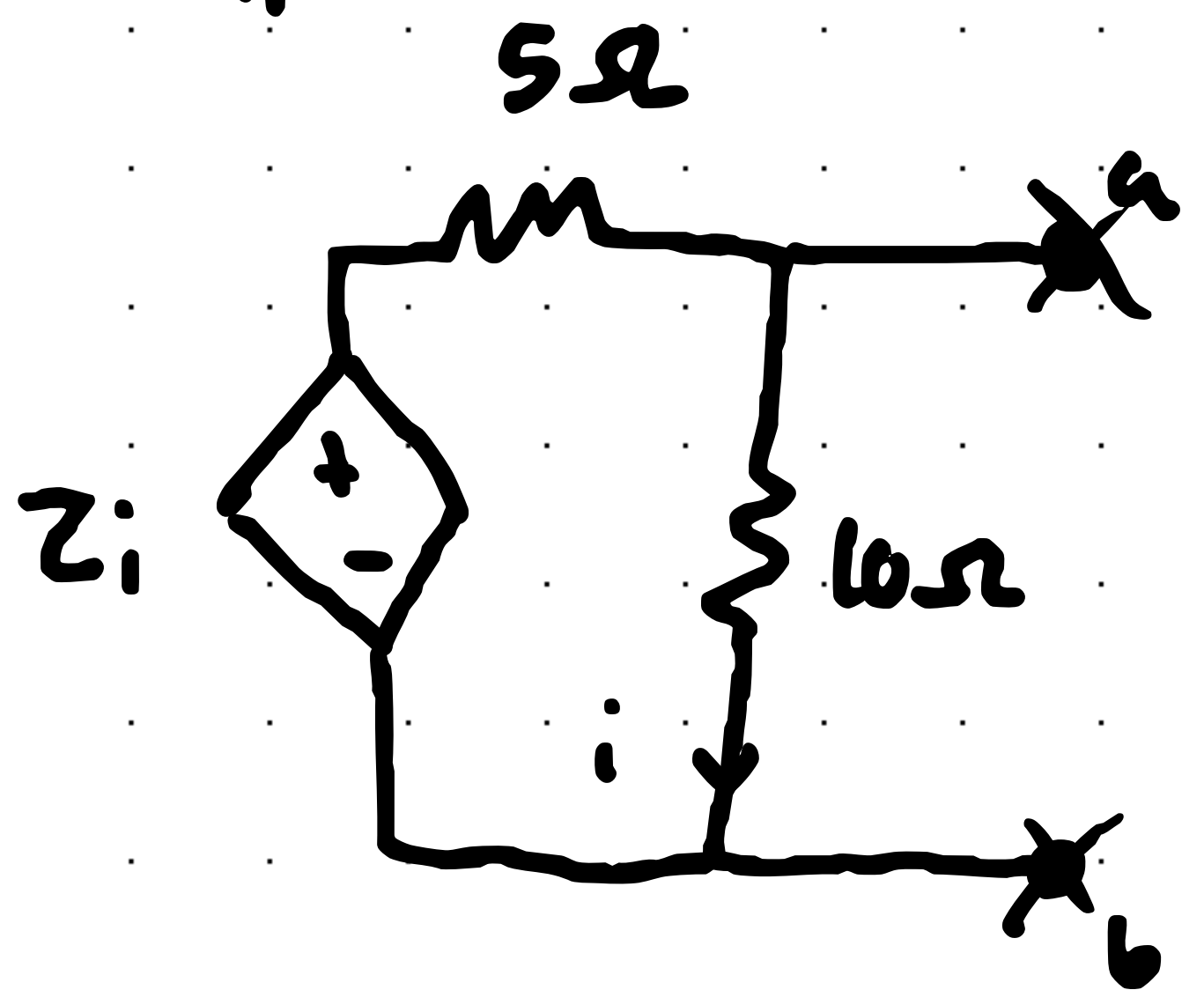


Well, There are no independent sources here...

Since there are no independent sources, I should be expecting that current is equal to zero...

So, Method one doesn't really work does it?
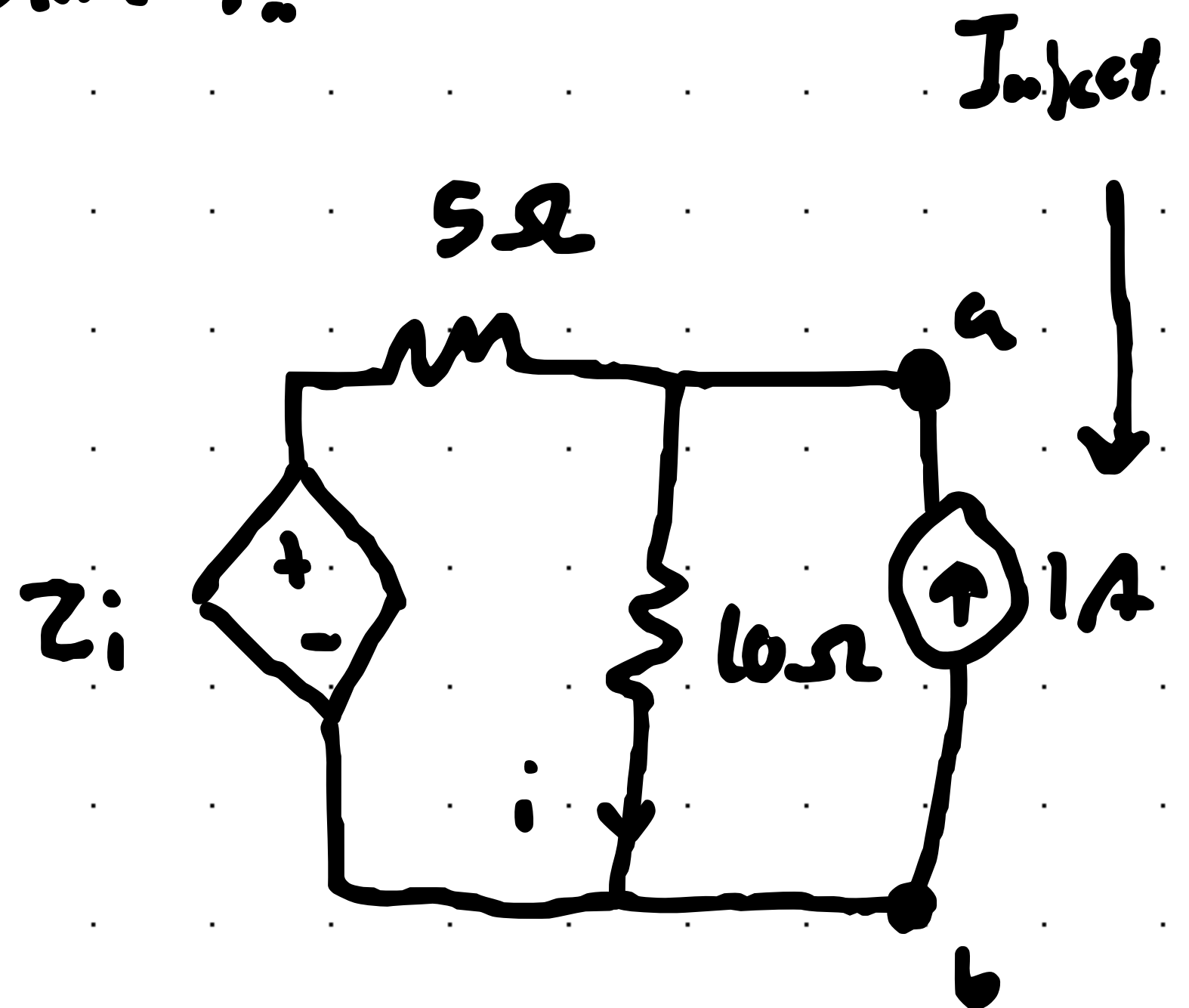
$$R_{TH} = \frac{0}{0} = \text{undefined...}$$



To calculate $R_N = R_{TH}$

$$\sum I = 0$$

Node ①

$$\frac{v_1 - z_i}{5} + \frac{v_1}{10} + (-1) = 0$$

$$i = \frac{v_1}{10}$$

$$\frac{v_1 - 2\left(\frac{v_1}{10}\right)}{5} + \frac{v_1}{10} + (-1) = 0$$

$$v_1 = 3.85$$

$$R_{TH} = R_N = \frac{v_1}{i} = \boxed{3.85 \Omega}$$