
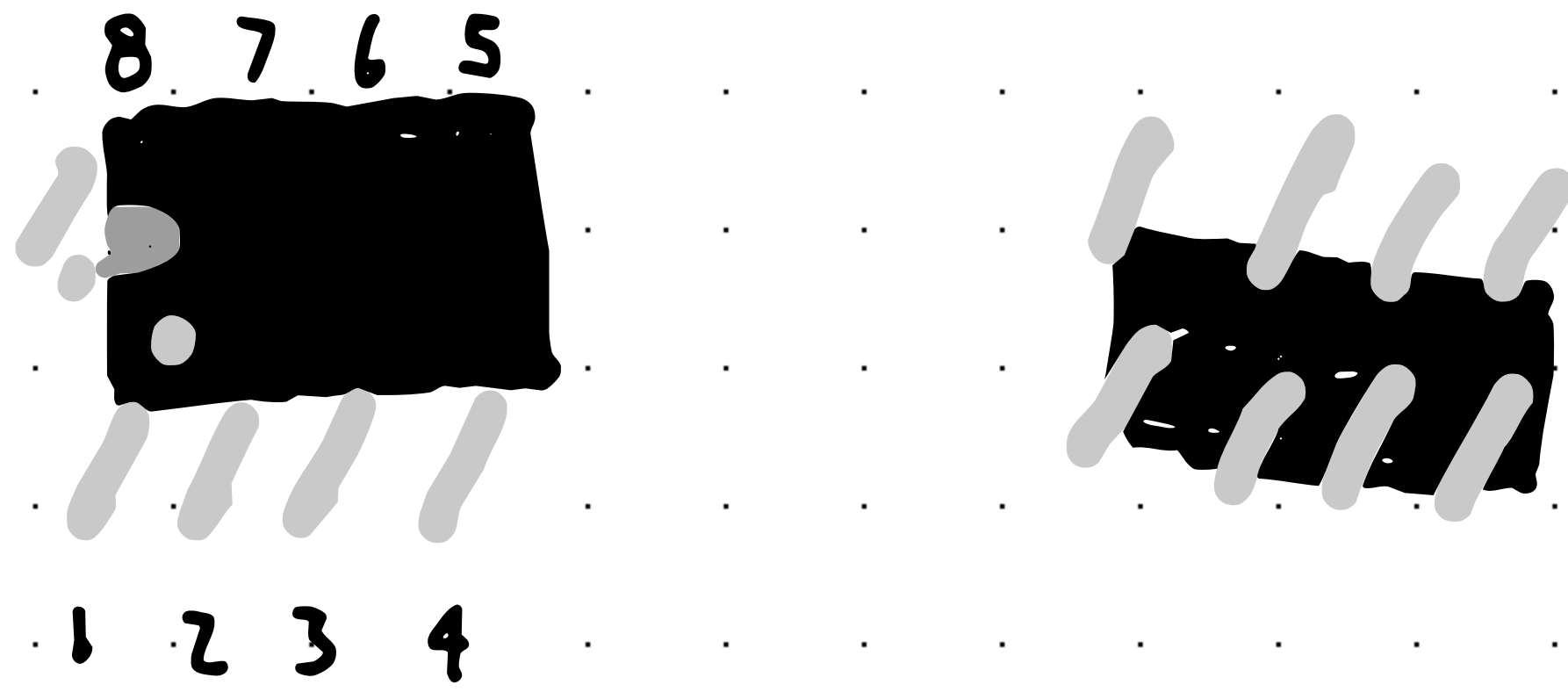


Operational Amplifiers (OP-Amps)

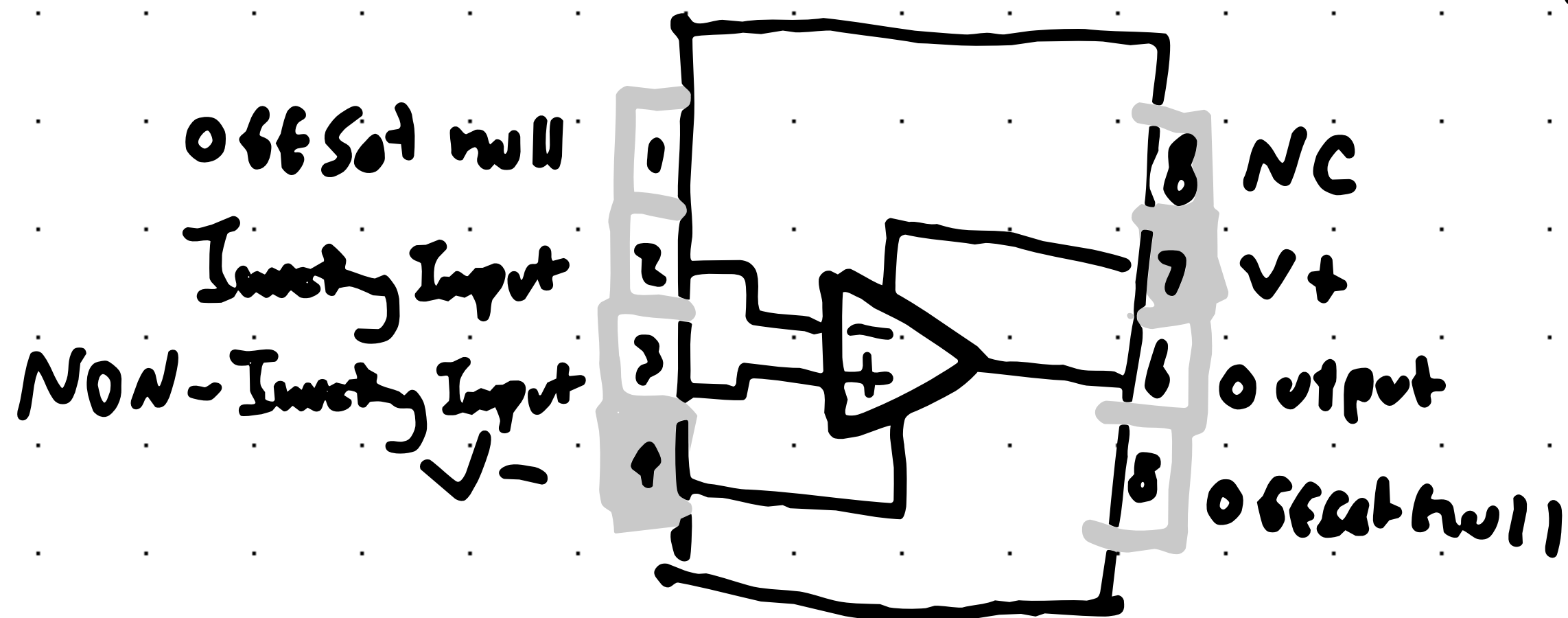


TYPE 741



741 IC Pinout
(Integrated Circuit)

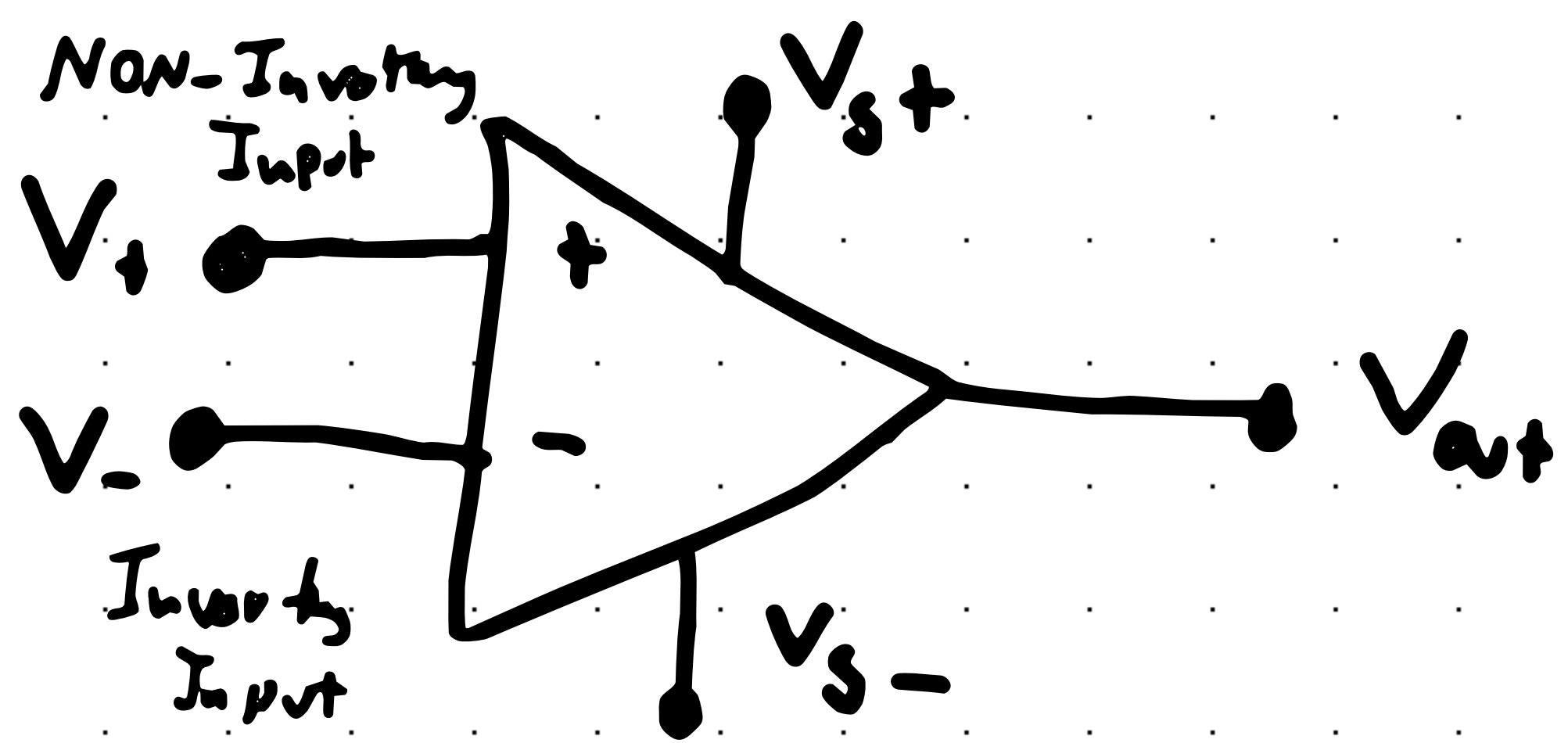- Purpose: Add, Subtract, divide, Multiply, adjust voltage




NON-Inverting Input:


If I'd like to Amplify a voltage, without changing the polarity, use the Non-Inverting Input.

Inverting Input:

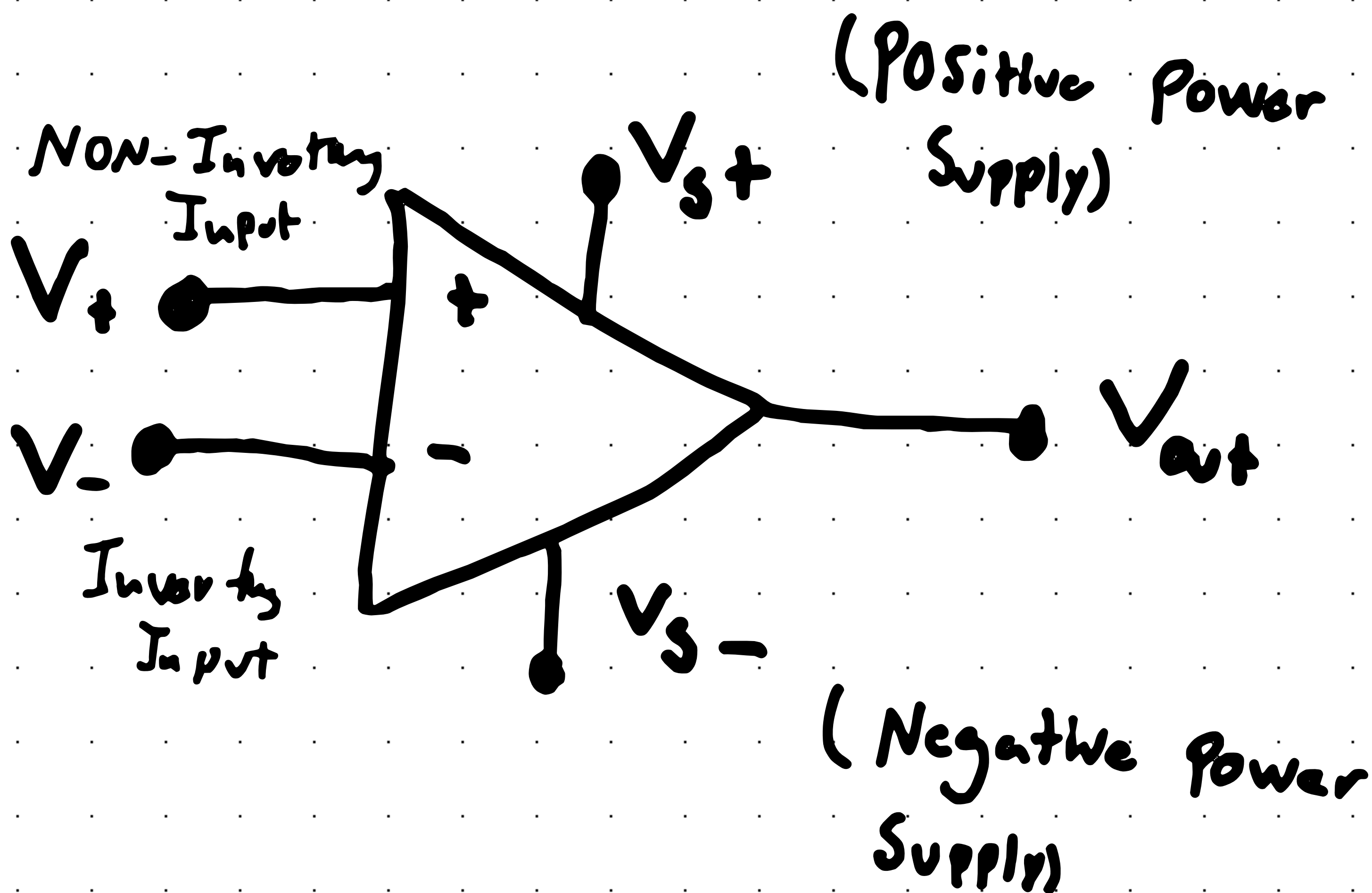If I'd like to Amplify a voltage, AND change the polarity, use the Inverting Input.



Terminal Voltages and Currents

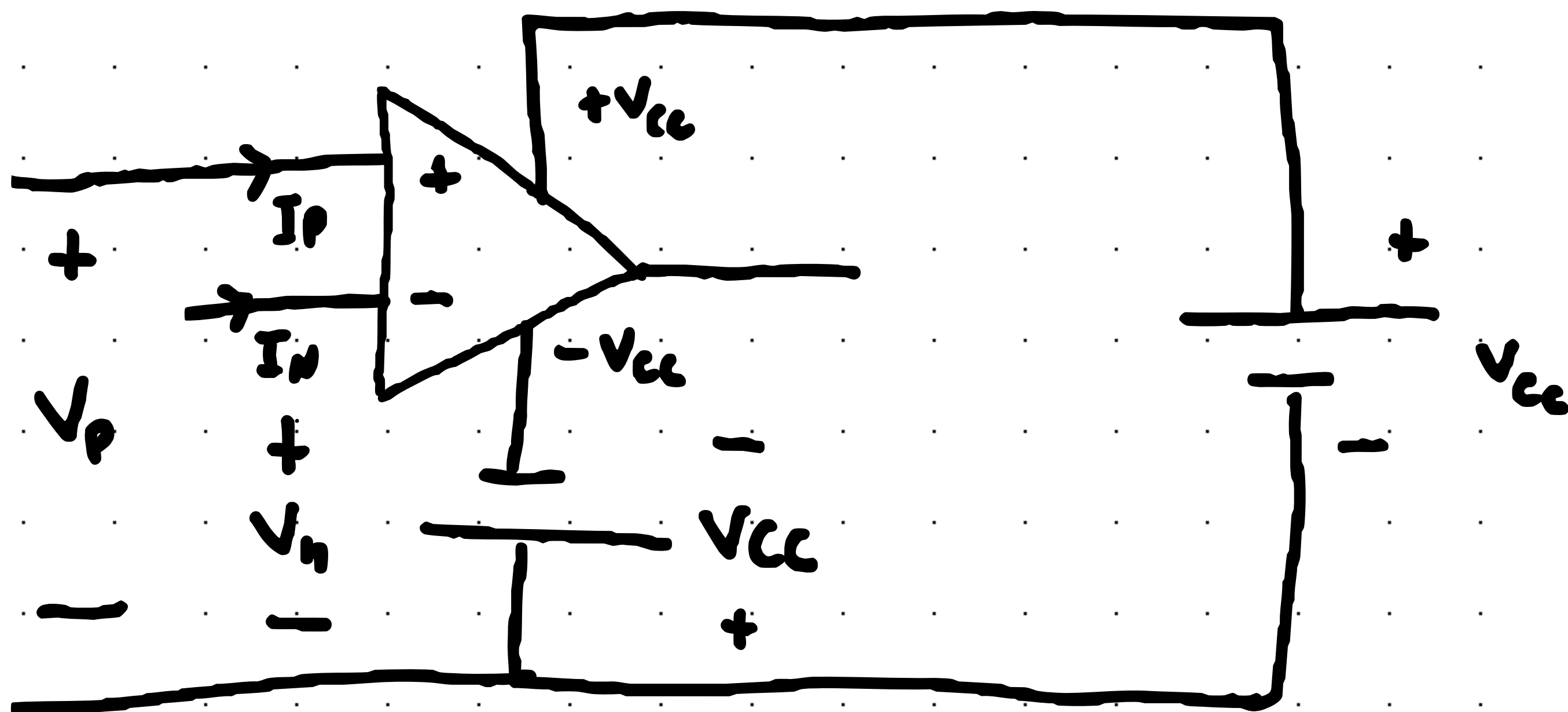

V_p : Positive Voltage

V_n : Negative Voltage


I_p : Positive Current

I_n : Negative Current

Ideal Op Amp

$$i_p = i_n = 0$$

$$V_p = V_n$$

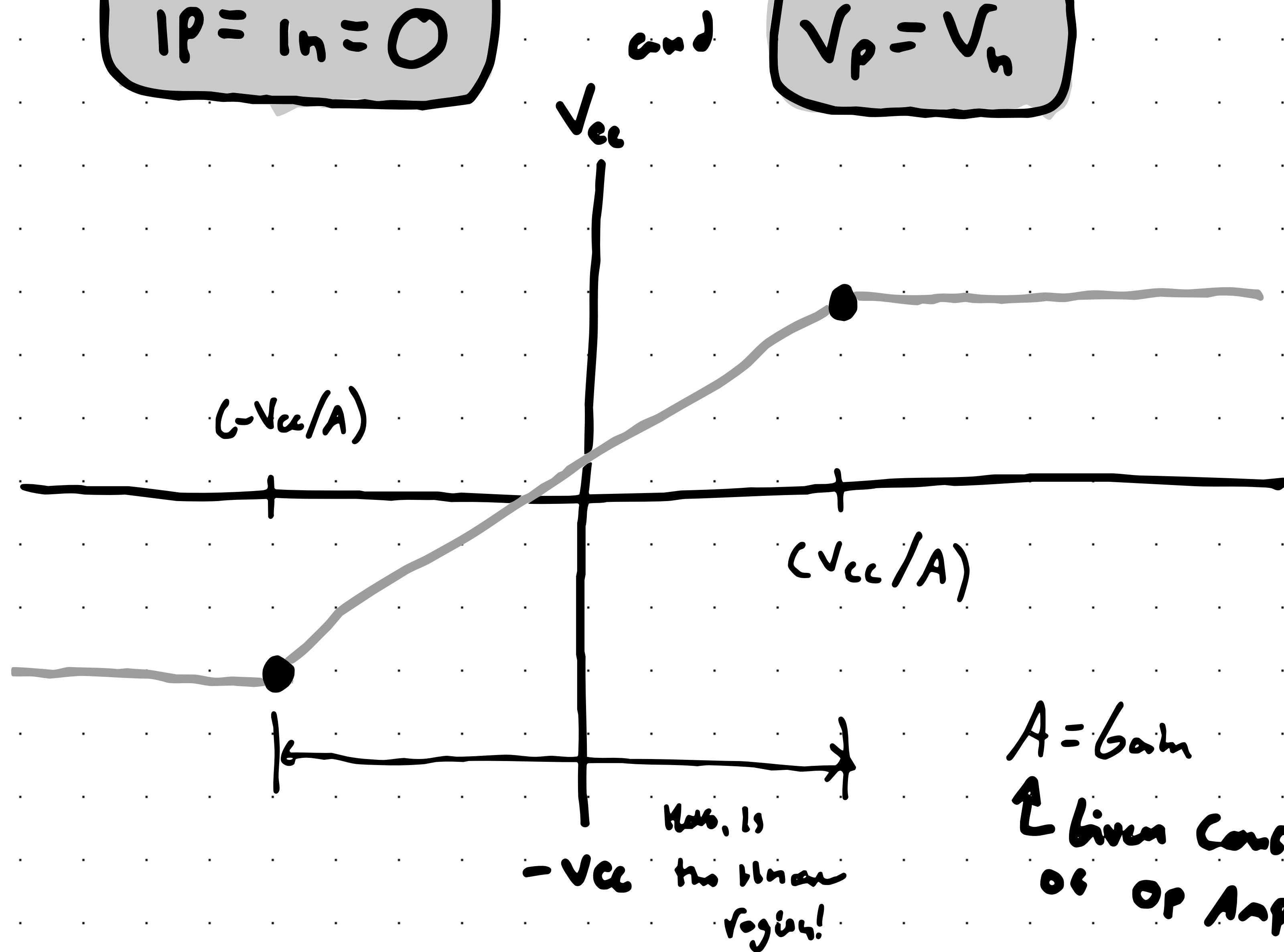


$$V_o = \begin{cases} -V_{cc} \\ A(V_p - V_n) \\ +V_{cc} \end{cases}$$

$$-V_{cc} \leq A(V_p - V_n) \leq V_{cc}$$

Range of Op Amp operations

- If we are not in the range of the linear region, or above or below $-V_{cc}$ or V_{cc} , the V_o just becomes $-V_{cc}$ or $+V_{cc}$

Example

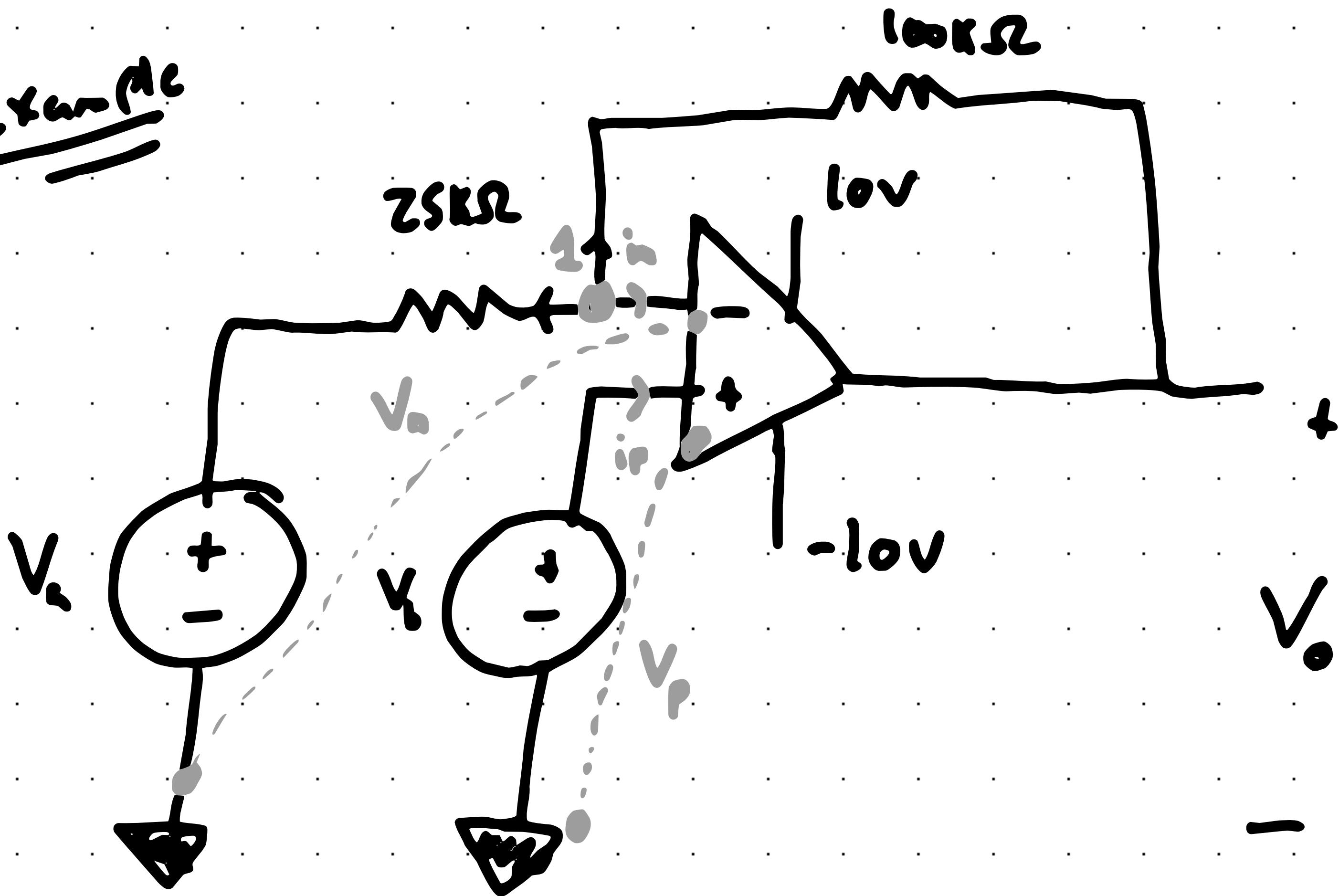

- Calculate V_o if $V_a = 1$ and $V_b = 0$
- Repeat @ for $V_a = 1V$ and $V_b = 2V$
- If $V_a = 1.5V$, Specify the range of V_b that avoids amplifier saturation.

Solution

$$i_p = i_n = 0, \quad V_p = V_n$$

$$V_p = V_b \rightarrow V_p = V_n = V_b$$

$$\sum_{\text{Node 1}} I = 0 \quad \frac{V_n - V_a}{25K} + \frac{V_n - V_o}{100K} + \cancel{I_n} = 0$$

Case a)

$$V_a = 1, V_b = 0$$

Calculate V_o

$$V_p = V_n = V_o$$

$$\frac{V_n - V_a}{25K} + \frac{V_n - V_o}{100K} \rightarrow \frac{0 - 1}{25,000} + \frac{0 - V_o}{100,000} = 0$$

$$V_o = -4V$$

$$V_o = -4V$$

$$-10 \leq -4 \leq 10$$

In active range!

Case b

$$V_a = 1$$

$$V_b = 2$$

$$\frac{2 - 1}{25,000} + \frac{2 - V_o}{100,000} = 0$$

$$V_o = 6V$$

$$V_o = 6V$$

$$-10 \leq 6 \leq 10$$

In active region!

Case C

$$V_a = 1.5V$$

$$V_b = ?$$

Range?

If $V_o = -10V$

min

$$\frac{V_b - 1.5}{25,000} + \frac{V_b - (-10)}{100,000}$$

If $V_o = 10V$

max

$$\frac{V_b - 1.5}{25,000} + \frac{V_b - (10)}{100,000}$$

$-0.8 \leq V_b \leq 3.2$

