


Voltage and Current Sources

☆ Ideal Voltage Source: is a circuit element that maintains a prescribed voltage across its terminals regardless of the current flowing in these terminals.

☆ Ideal Current Source: is a circuit element that maintains a prescribed current through its terminals regardless of the voltage across these terminals.

- Active circuit elements generate power
- Passive circuit elements absorb power
(i.e., resistor)


Types of Sources

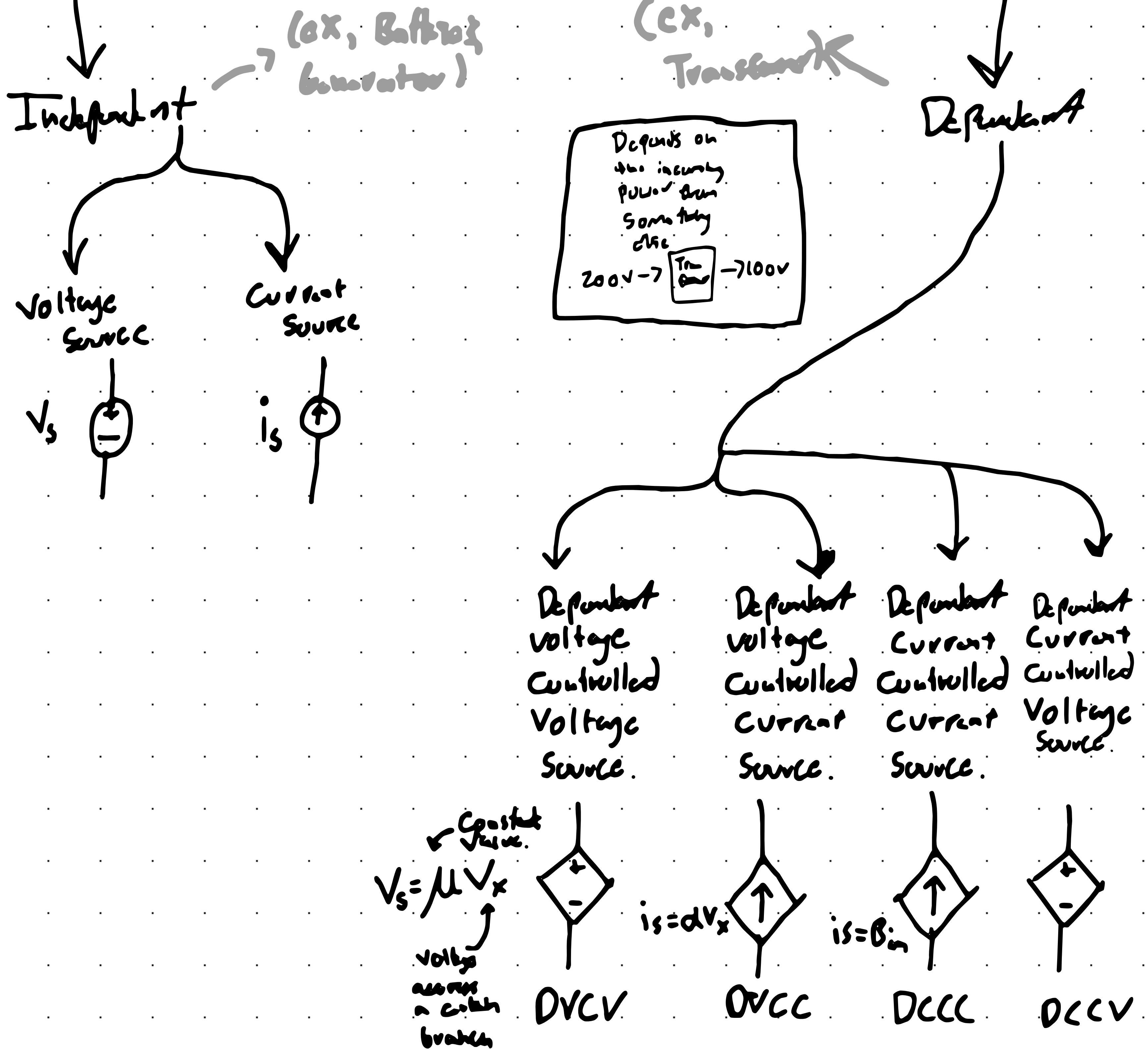

The current flows from \ominus to \oplus

Types of elements in any circuit

Active

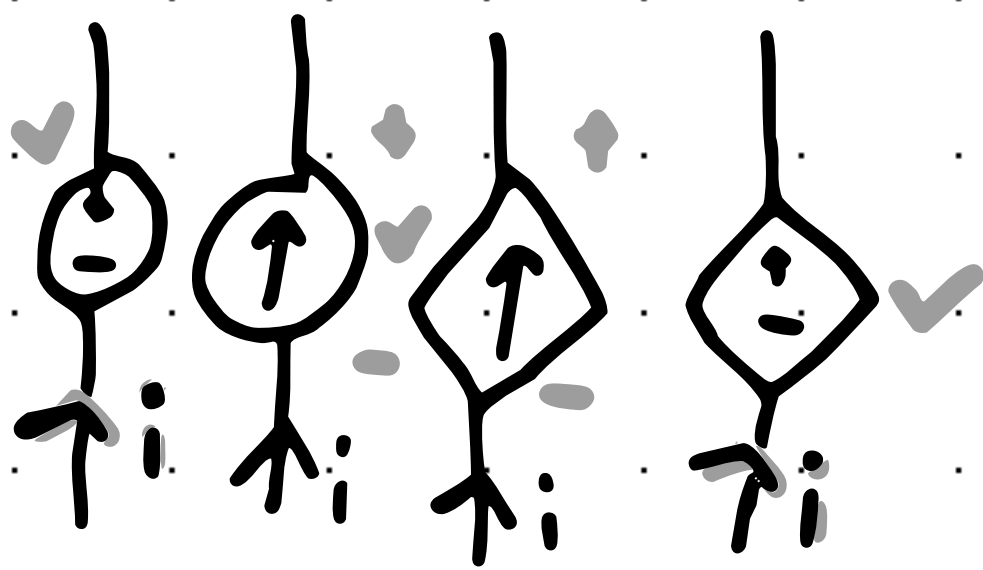


The current flows from \ominus to \oplus

The power is generated

$$P = -vi$$

Passive

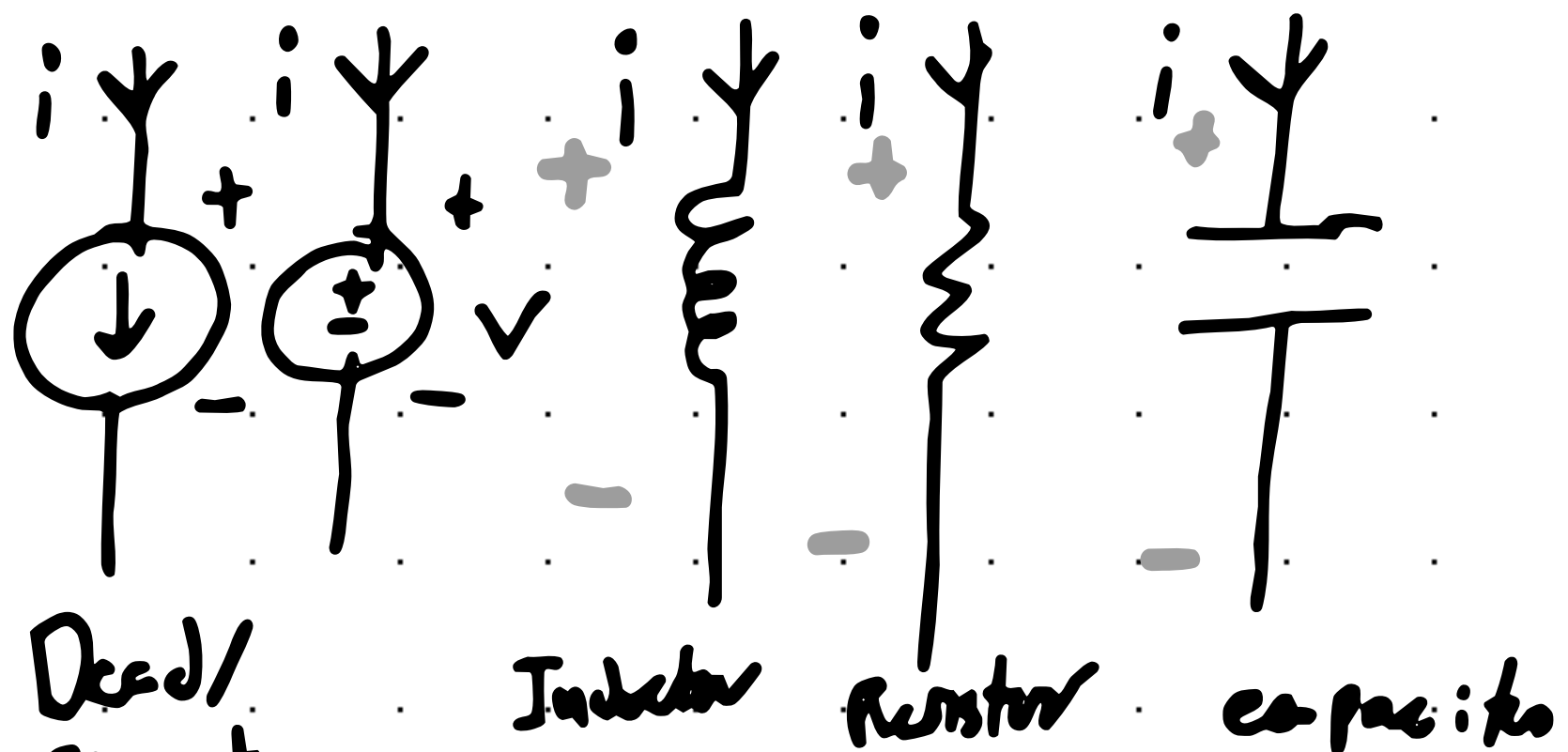

Dead/Charging Batteries

Inductor Resistor capacitor

The current flows from \oplus to \ominus


The power is absorbed.

$$P = vi$$

Batteries can be either or! Depending on charging, or not.


Ohm's Law

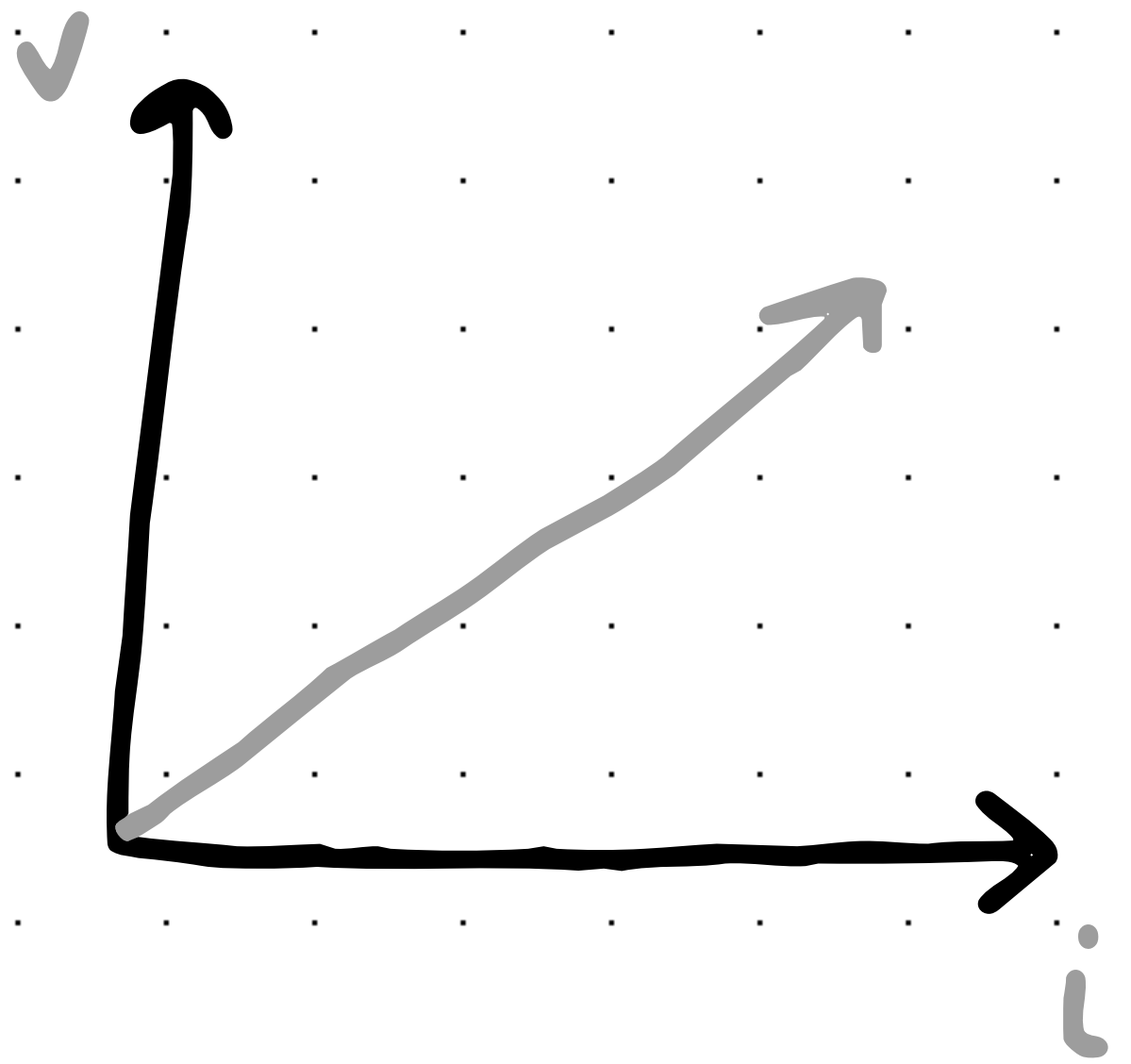Ohm did a bunch of cool experiments with wires, to discover Resistance!



Giving us what we all know
as...

$$\underline{V = IR}$$


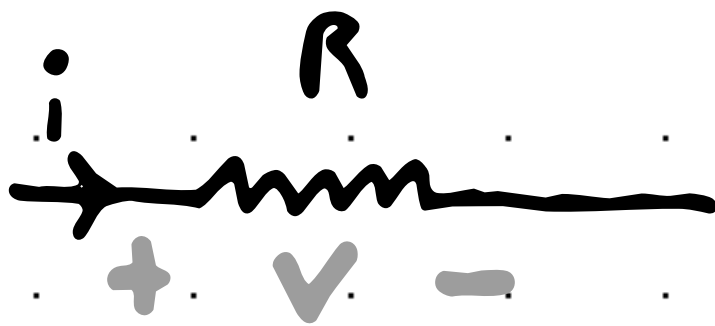


R: Resistance \rightarrow Unit Ohms (Ω)

$\frac{1}{R} = G$: conductance \rightarrow Unit Siemens (S)
Mhos (\mathcal{U})

Kirchoff's Laws

① Kirchoff's Current Law (KCL)

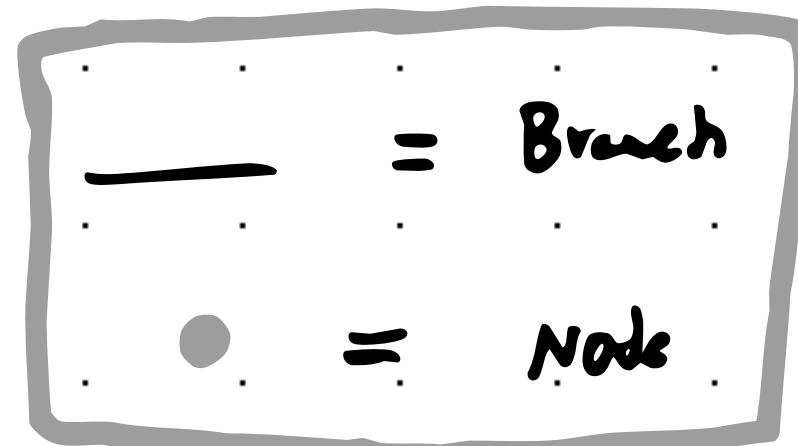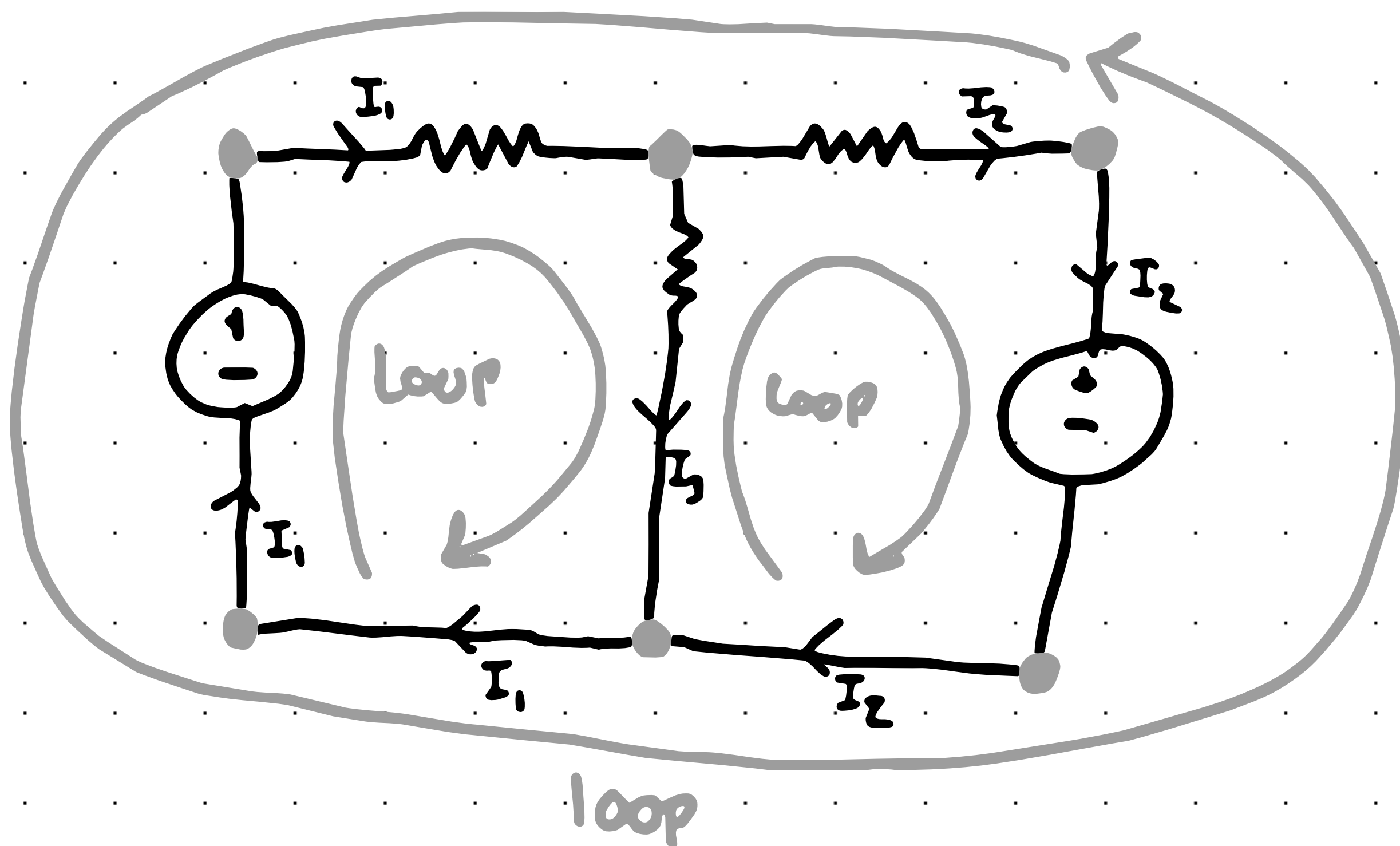

$$\sum I = 0$$


At each node!

Let's assume the current entering the node is positive, and the current leaving is negative

ie, The sum of all currents going in is equal to the sum of all currents going out!

$$I_1 - I_2 - I_3 = 0$$

b) Kirchoff's voltage laws (KVL)

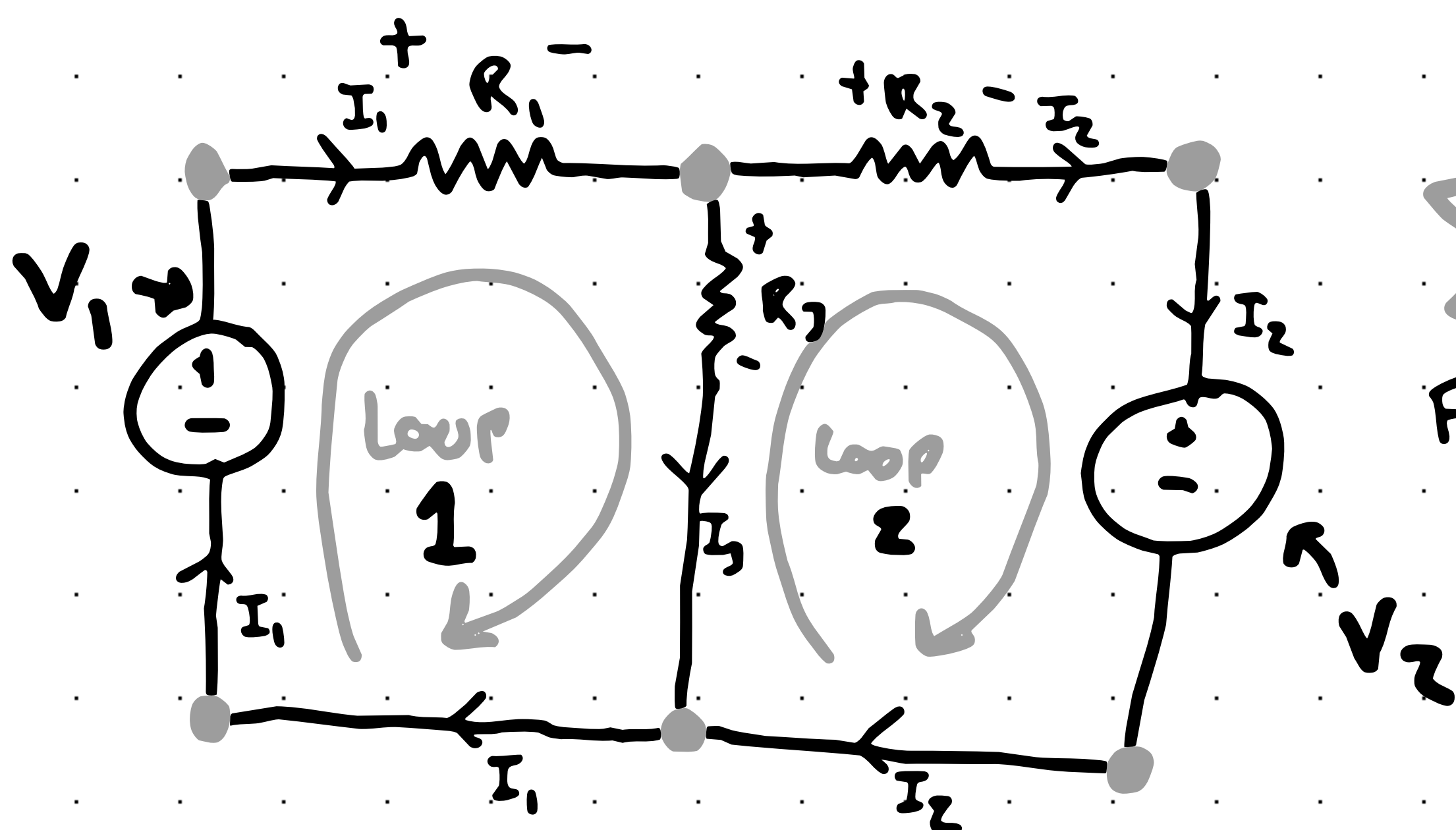

$$\sum V = 0$$

For each loop

It doesn't matter in which direction you travel around the loop, but **be consistent!**


Loop one

$$+V_1 - I_1 R_1 - I_3 R_3 = 0 \quad \text{⌚}$$

Loop Two

$$-I_2 R_2 + I_3 R_3 - V_2 = 0 \quad \text{⌚}$$

Ex:

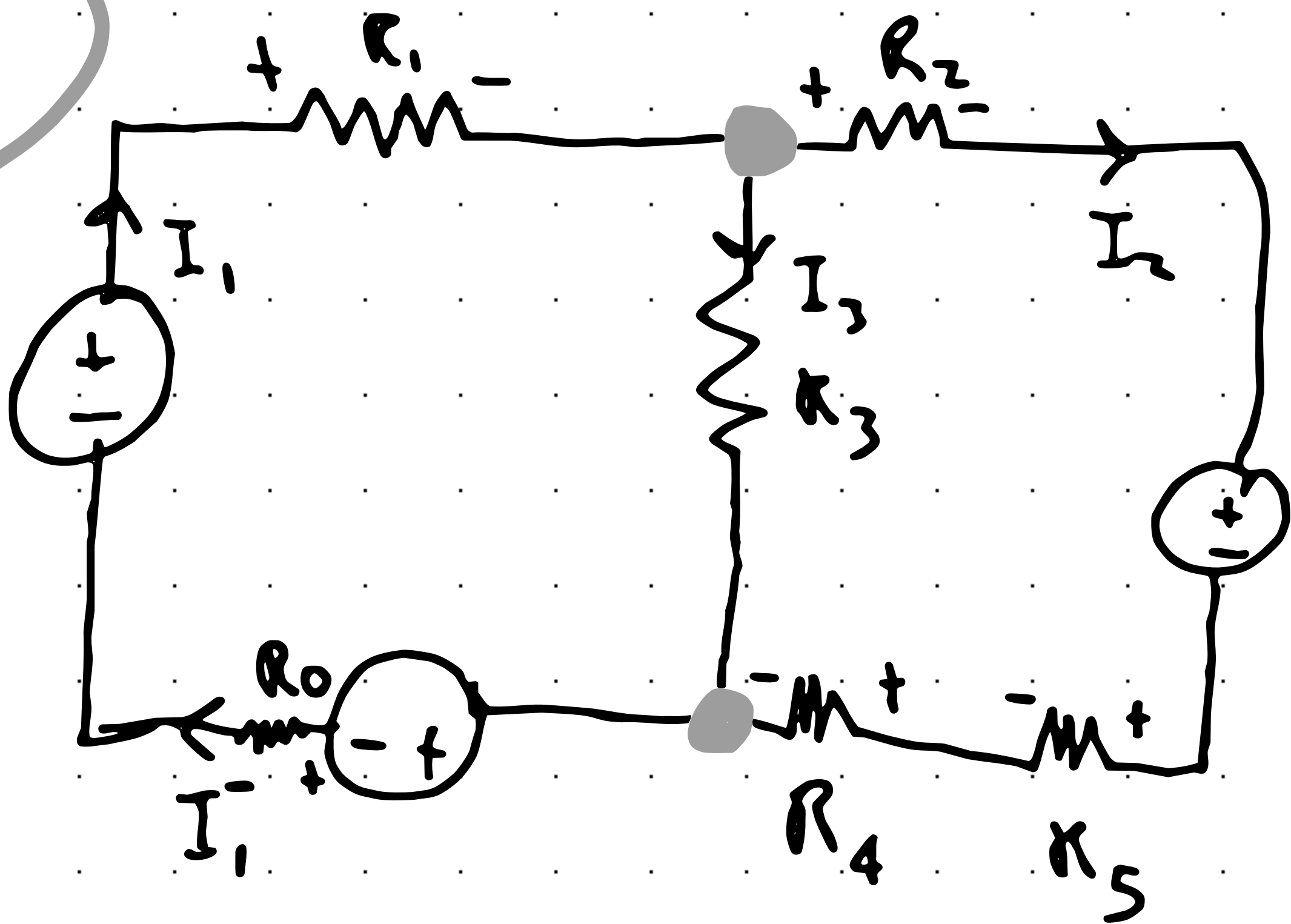

$$\sum I = 0$$

$$I_1 - I_2 - I_3 = 0$$

node 1

$$\sum V = 0$$

loop ①

$$-V_3 - I_1 R_0 + V_1 - I_1 R_1 - I_3 R_3 = 0$$

$$\sum V = 0$$

loop ②

$$-I_2 R_4 + I_3 R_3 - I_2 R_2 - V_2 - I_2 R_5 = 0$$