








Sinusoidal Steady State

Element	Time domain	Phasor domain
① Resistor	 $v = IR$	 $v = IR$
② Inductor	 $v = L \frac{di}{dt}$	 $v = i(j\omega L)$
③ Capacitor	 $v = \frac{1}{C} \int i dt + v_c(t_0)$	 $v = i(-j \frac{1}{\omega C})$

# Complex Numbers

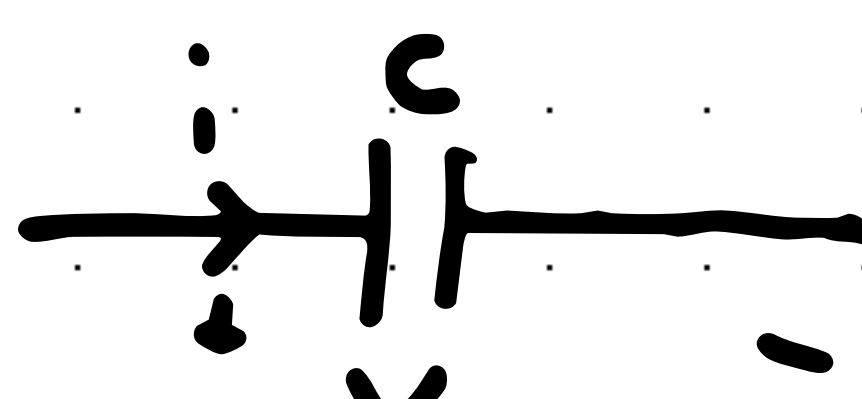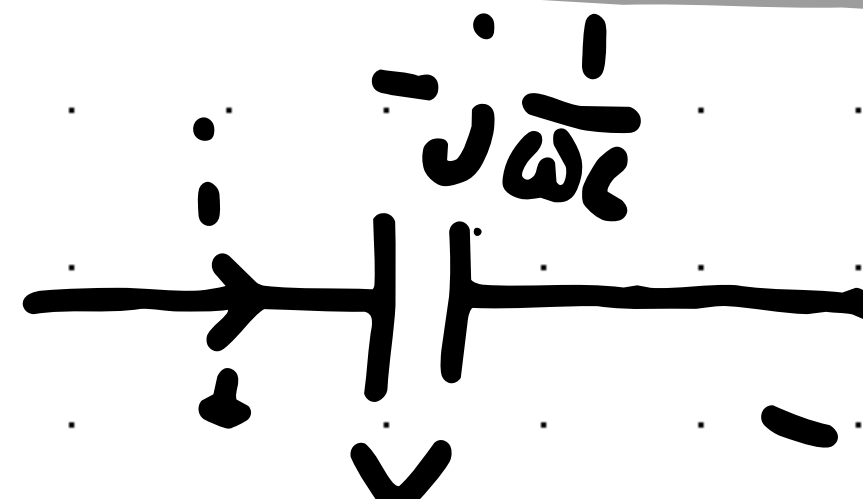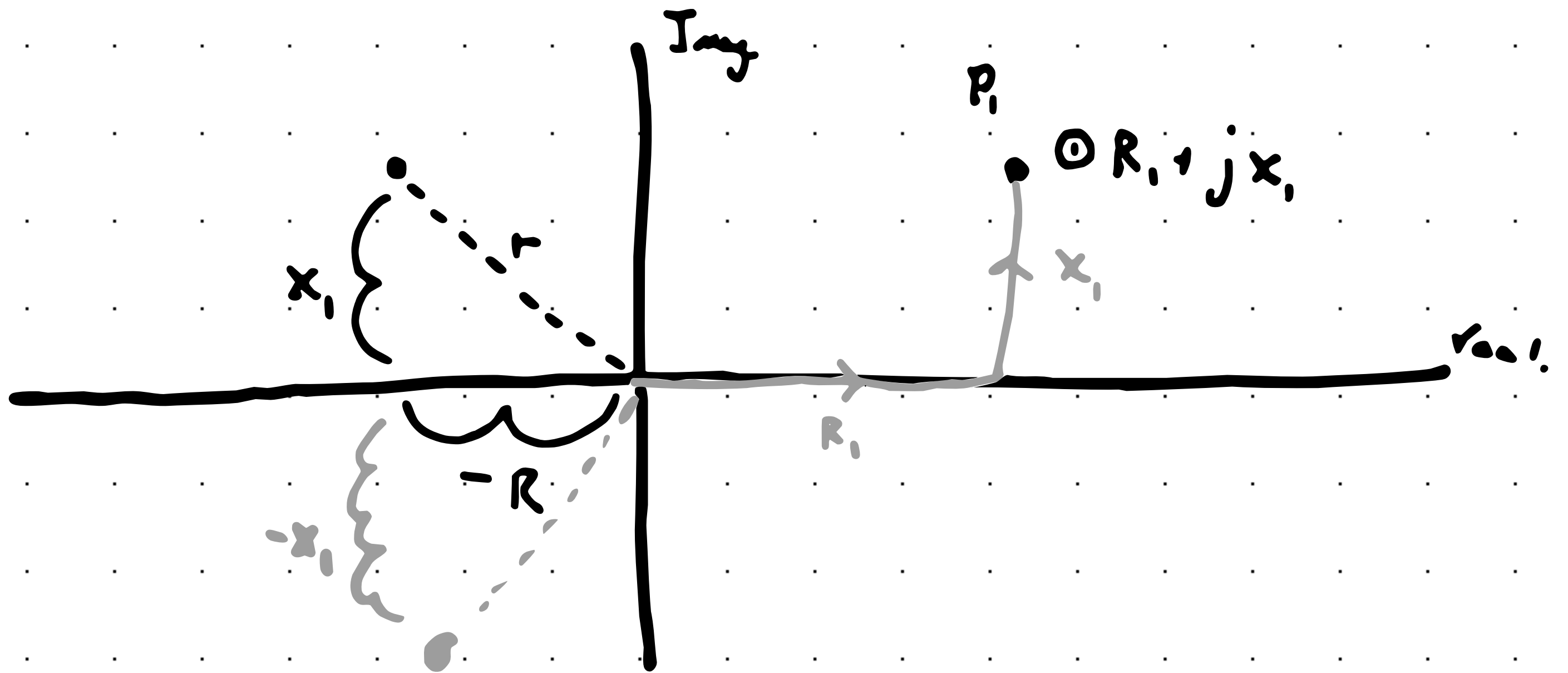

## Complex Plane

$P_1$  is represented by either:

Rectangular Form

$$R_1 + jX_1$$

Polar Form

$$r \angle \theta$$

$$r \angle \theta = R_1 + jX_1 = r \cos \theta + jr \sin \theta,$$

$$R_1 + jX_1 = \sqrt{R_1^2 + X_1^2} \angle \tan^{-1}\left(\frac{X_1}{R_1}\right) = r \angle \theta$$

For the Second Quadrant

$$-R_1 + jX_1 = \sqrt{R_1^2 + X_1^2} \angle 180 - \tan^{-1} \frac{X_1}{R_1}$$

For the Third Quadrant

$$-R_1 - jX_1 = \sqrt{R_1^2 + X_1^2} \angle 180 + \tan^{-1} \frac{X_1}{R_1}$$

For the fourth Quadrant

$$-R_1 - jX_1 = \sqrt{R_1^2 + X_1^2} \angle -\tan^{-1} \frac{X_1}{R_1}$$

As well  $j = \sqrt{-1}$ ,  $j^2 = -1$

Adding or Subtracting two Complex Numbers

$$\Rightarrow (R_1 + jX_1) \pm (R_2 + jX_2) =$$

$$= (R_1 \pm R_2) + j(X_1 \pm X_2)$$

$$\Rightarrow r_1 \angle \theta_1 + r_2 \angle \theta_2 =$$

$$= r_1 \cos \theta_1 + jr_1 \sin \theta_1 + r_2 \cos \theta_2 + jr_2 \sin \theta_2 =$$
$$= (r_1 \cos \theta_1 + r_2 \cos \theta_2) + j(r_1 \sin \theta_1 + r_2 \sin \theta_2)$$

# Multiplying or dividing two complex numbers

$$(R_1 + jX_1)(R_2 + jX_2) = R_1R_2 + jR_1X_2 + jR_2X_1 - X_1X_2$$
$$= (R_1R_2 - X_1X_2) + j(R_1X_2 + R_2X_1)$$

Multiplication

$$\left( \frac{R_1 + jX_1}{R_2 + jX_2} \right) \left( \frac{R_2 - jX_2}{R_2 - jX_2} \right)$$


Complex conjugate needed

Division

Polar

$$\frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle \theta_1 - \theta_2$$
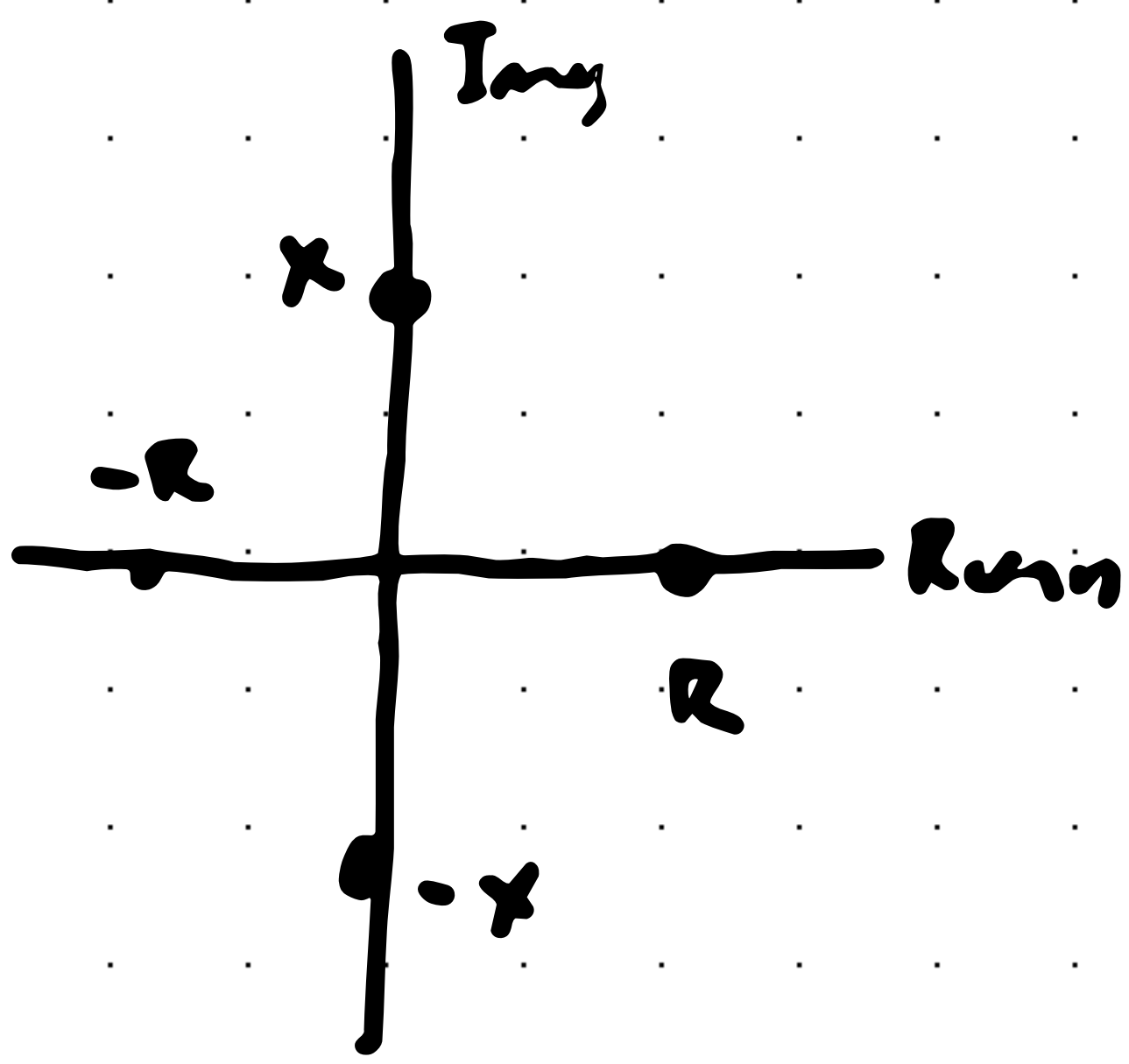
$$(r_1 \angle \theta_1)(r_2 \angle \theta_2) = r_1 r_2 \angle \theta_1 + \theta_2$$



$$R = R + j0 = R \angle 0$$

(All Real, so angle is 0°)

$$jx = x \angle 90^\circ$$

(All Imaginary, so angle is 90°)

$$-R = R \angle 180^\circ$$

$$-jx = x \angle 270^\circ$$

# Resistor



$$5i = 5 \angle 90^\circ$$

$$V = IR$$

Angle of voltage,  $\omega t$   
Angle of current is  
the same  
No phase shift.

# Inductor




$$jX_L = j\omega L = j2\pi fL$$

★ Reactance ( $\Omega$ )

$$V = i(j\omega L) \\ = i\omega L \angle 90^\circ$$

Voltage leads current  
by  $90^\circ$ . Phase shift  
is  $90^\circ$ .

# Capacitor

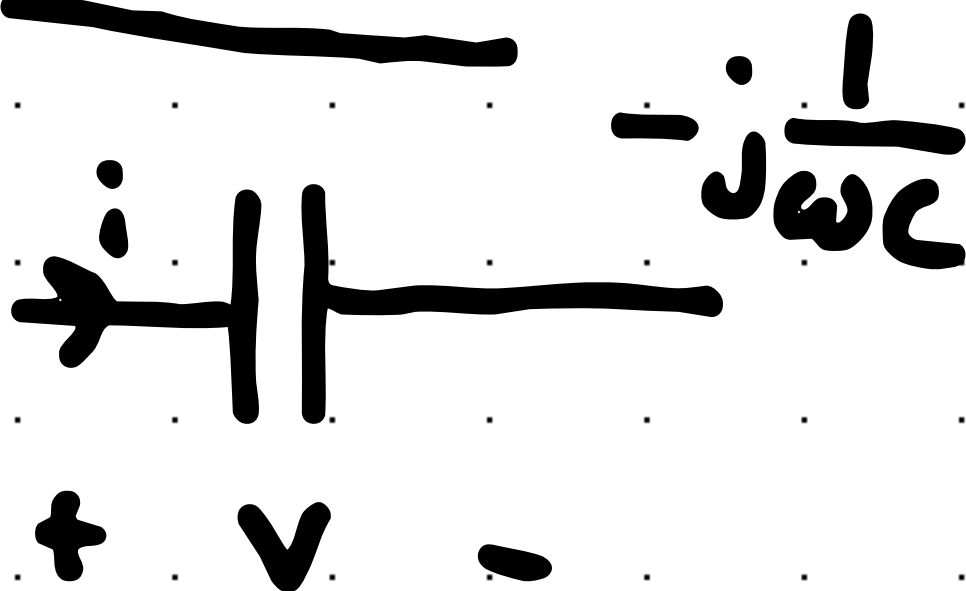

$$-j\left(\frac{1}{\omega C}\right) = -j\frac{1}{2\pi fC}$$
$$V = i\left(-j\frac{1}{\omega C}\right) = i(-jX_C)$$

## Voltage in phasor domain

- $v(t) = V_m \cos(\omega t + \phi)$

←  $\phi$

⇓

Time Domain

Phasor

$$V = V_m \angle \phi$$

---

## Current in phasor domain

- $i(t) = I_m \cos(\omega t + \theta)$

⇓

Time Domain

Phasor

$$i(t) = I_m \angle \theta$$

