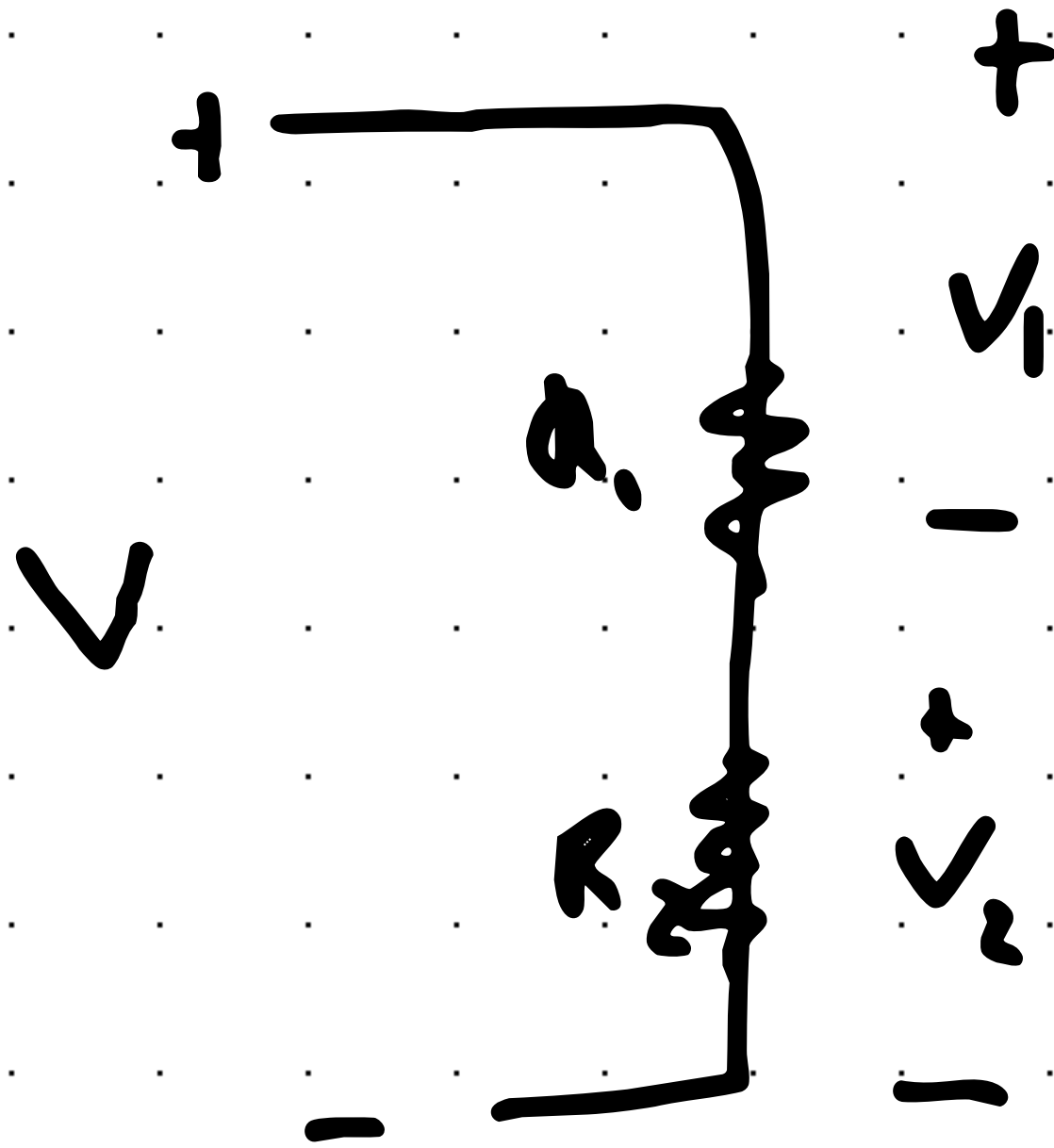


Voltage divider

$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) V$$

$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V$$




This applies for resistors in series!

Current divider

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

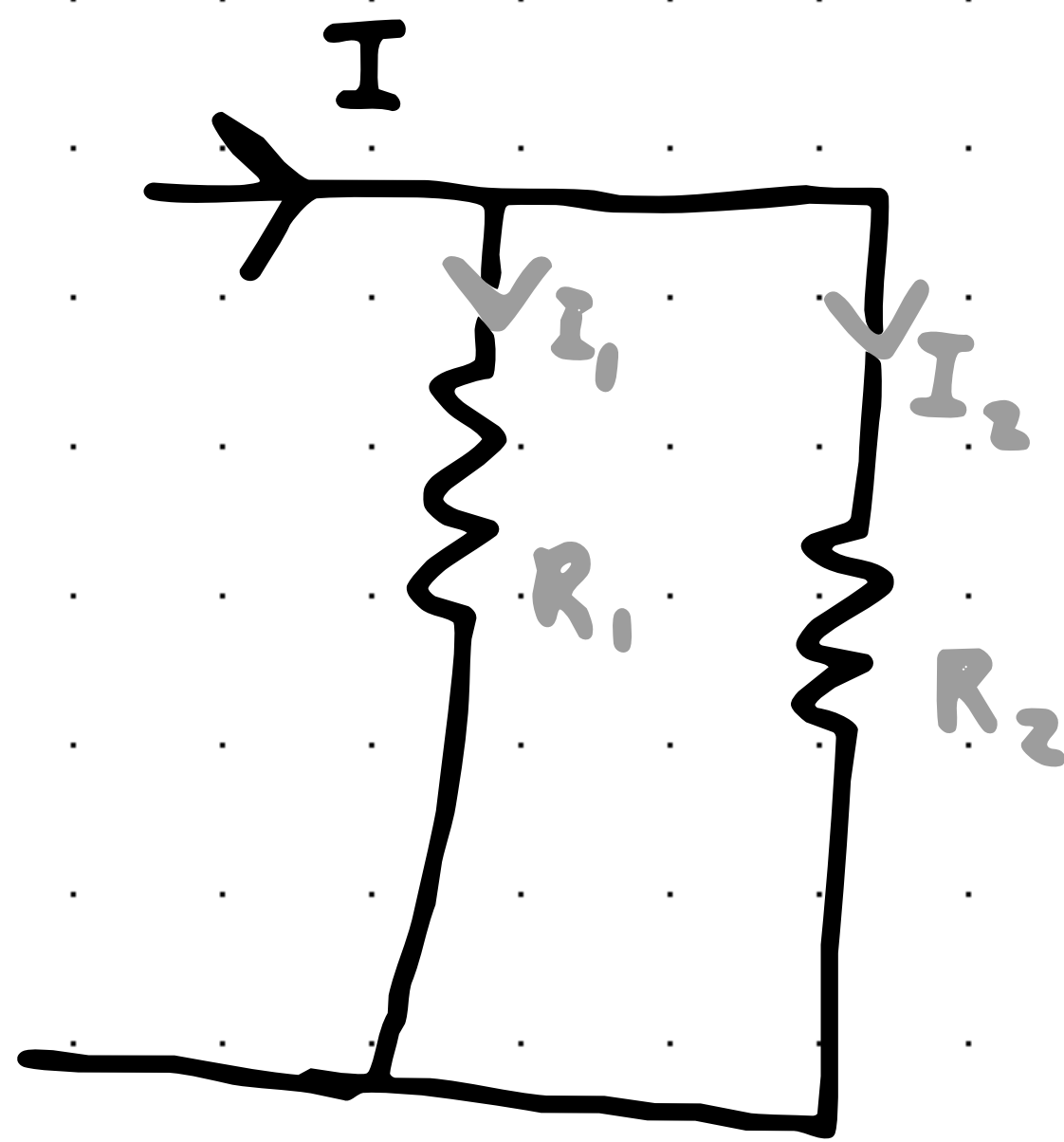

This applies to two resistors in parallel!

use in series on a parallel branch,  
make a bigger Req

# Voltage Divider Example

$$V_1 = V \left( \frac{R_1}{R_1 + R_2 + R_3 + R_4} \right)$$


$$V_2 = V \left( \frac{R_2}{R_1 + R_2 + R_3 + R_4} \right)$$

$$V_3 = V \left( \frac{R_3}{R_1 + R_2 + R_3 + R_4} \right)$$

$$V_4 = V \left( \frac{R_4}{R_1 + R_2 + R_3 + R_4} \right)$$



# Example 1

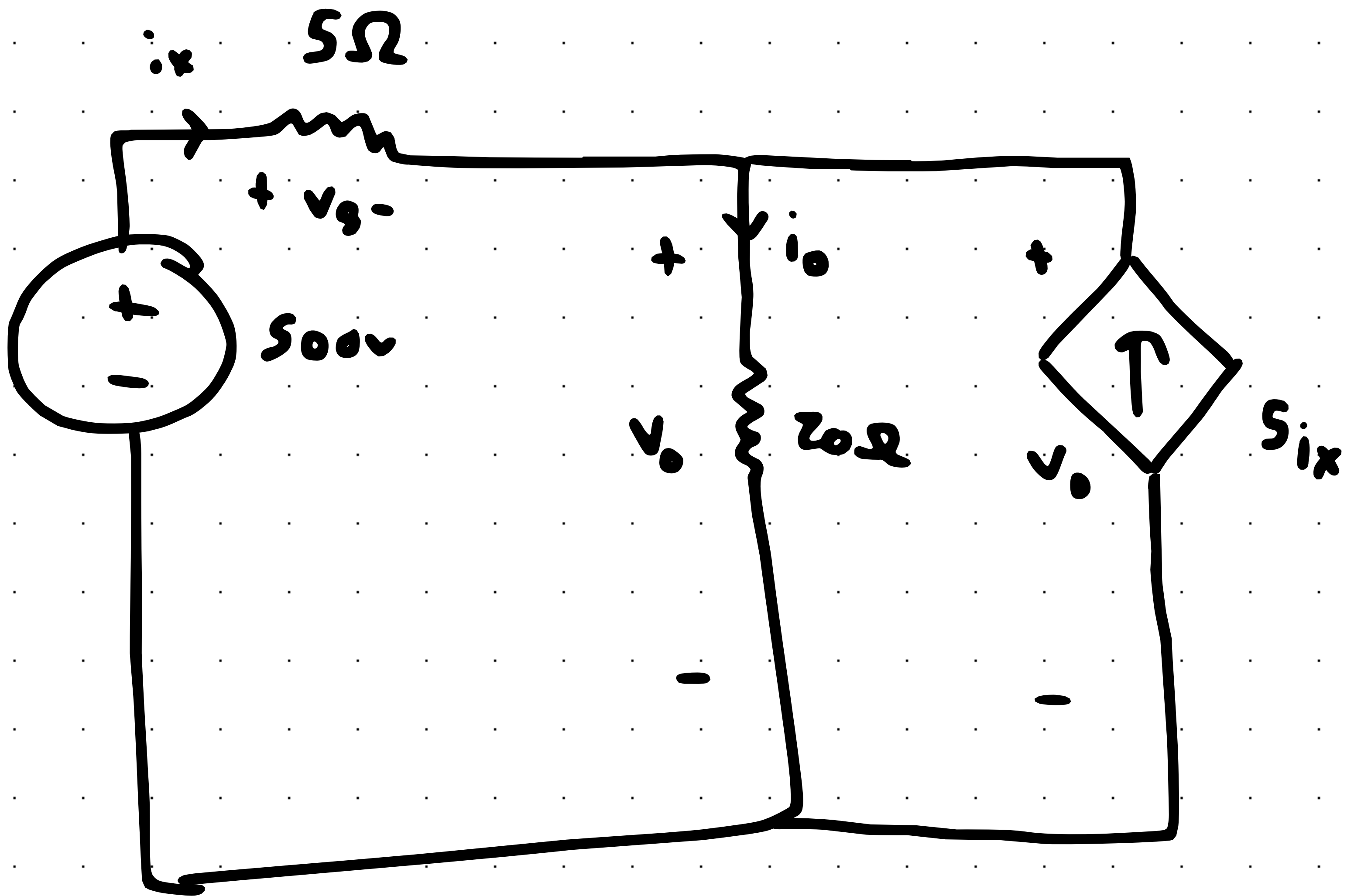

Calculate the current and the power in each branch, and verify that

$$\sum P_{\text{gen}} = \sum P_{\text{abs}}$$

