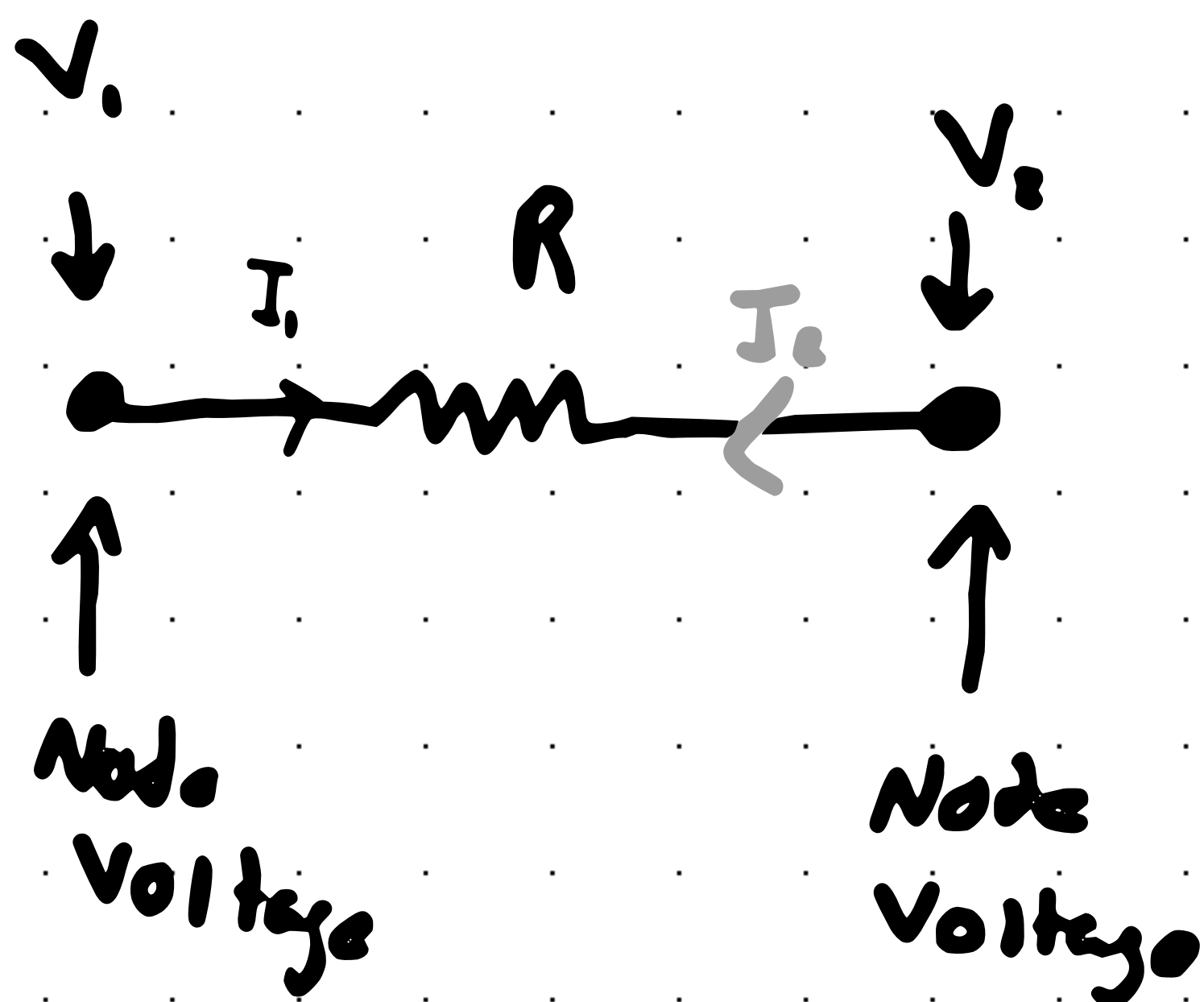


For any Resistor..

$$I_1 = \frac{V_1 - V_2}{R}$$

$$I_2 = \frac{V_2 - V_1}{R}$$



I_2 is going in the opposite direction

- I_1 and I_2 do NOT cancel each other out!
- They are the same current.

Have...



We are measuring the voltage
difference across the Resistor

$$I_1 = \frac{V_1 - V}{R}$$


~~~~~


$$I_2 = \frac{V - (-V)}{R}$$

Polarity  
Flip!

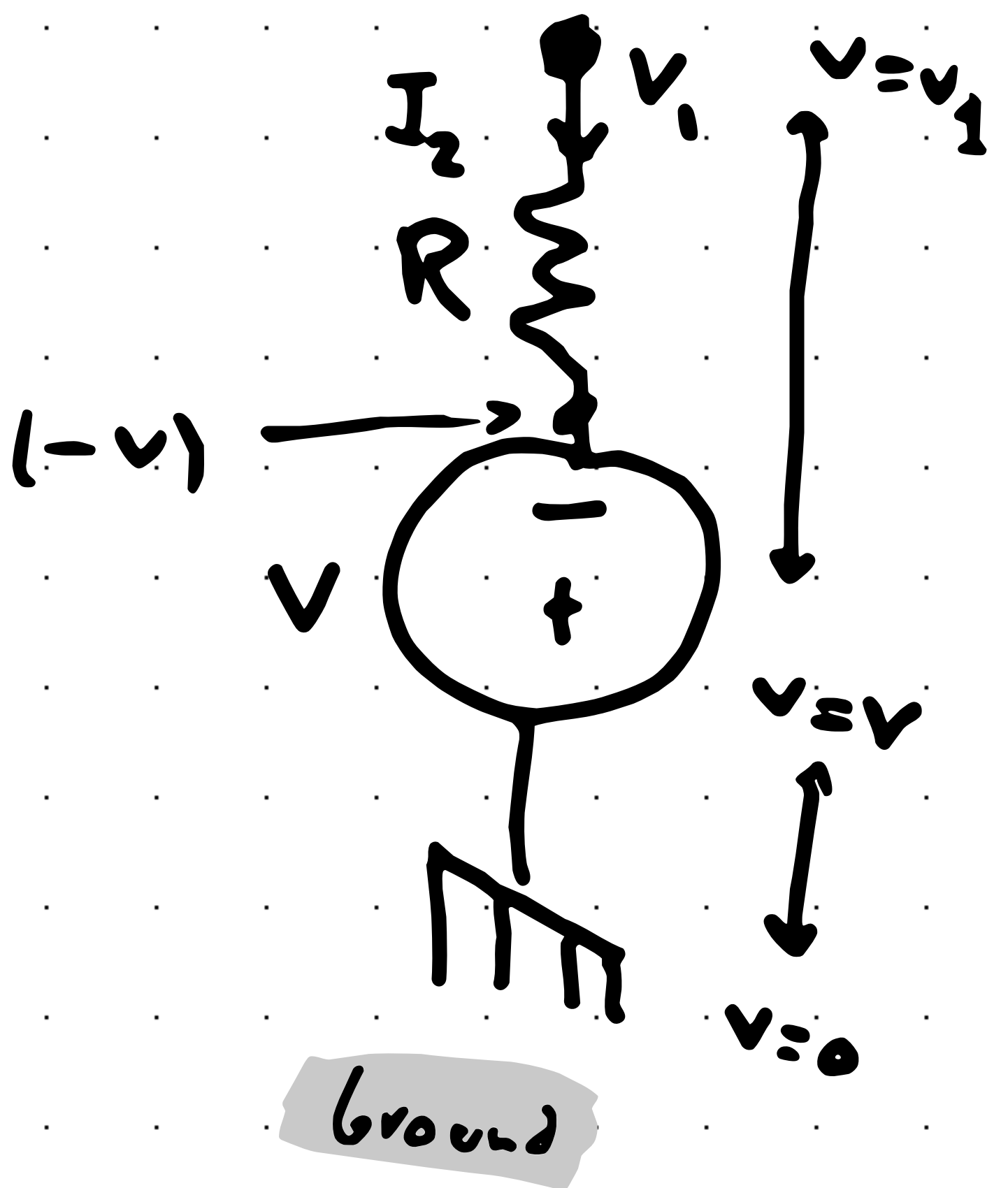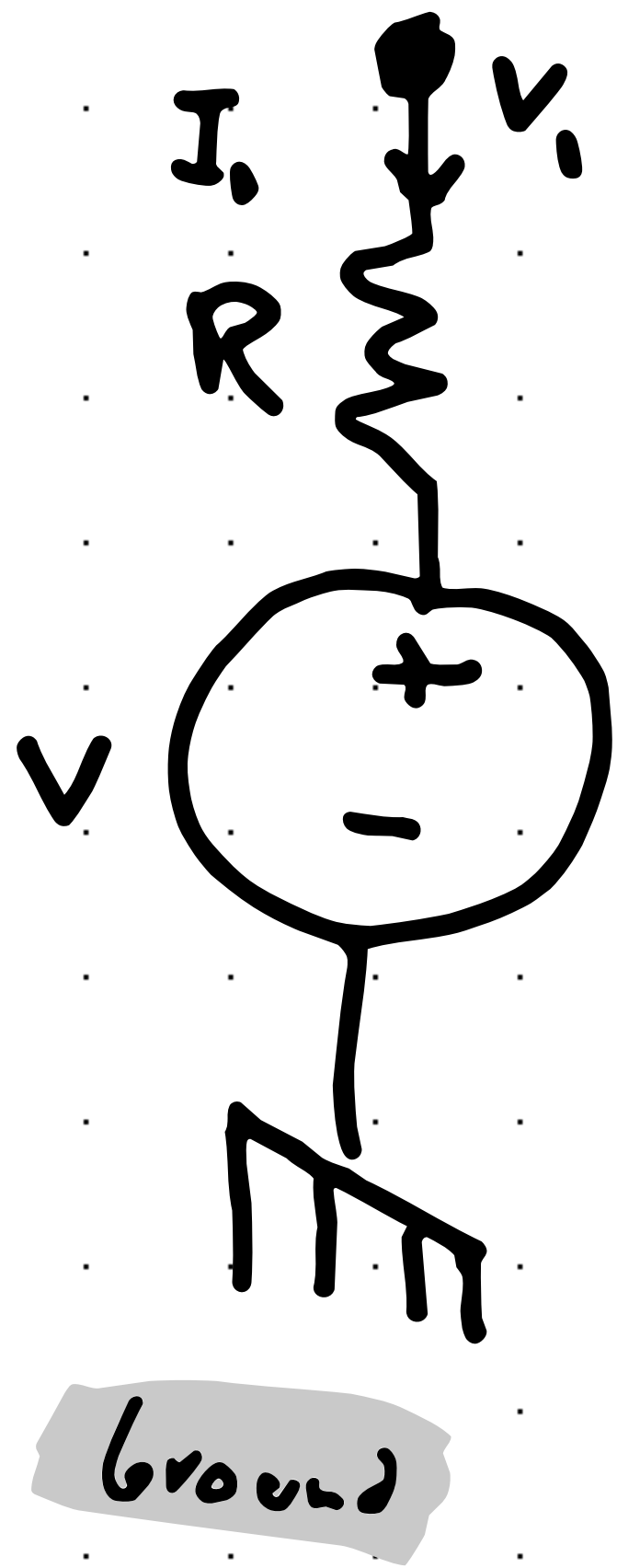

$$I = \frac{V_1 - 0}{R}$$

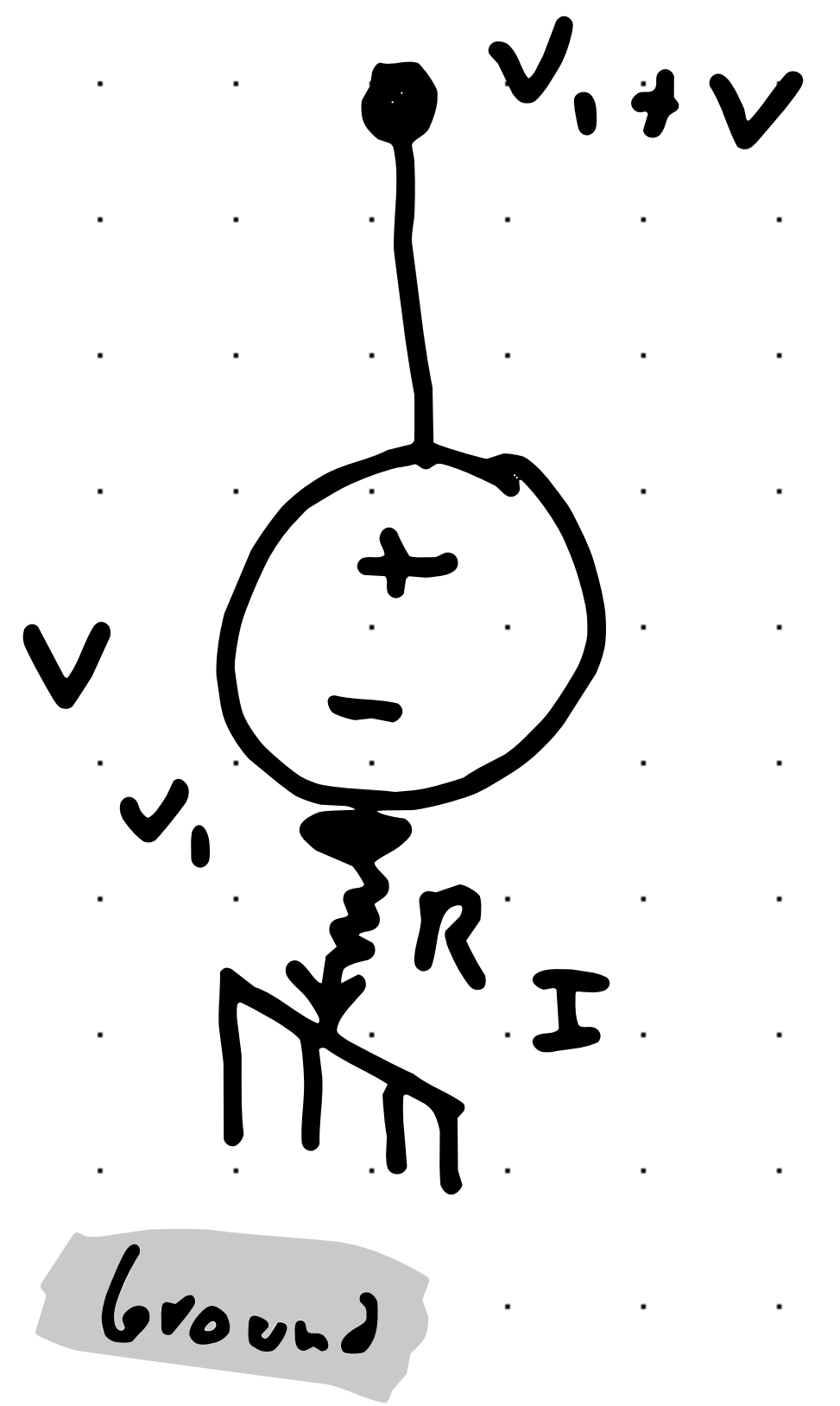

 




# Node-Voltage Method

(Nodal Analysis)

- 1) Choose any node, and connect it to ground (its voltage will be zero.)
- 2) Define the voltage for all other nodes referred to the reference node.
- 3) Use KCL ( $\sum I = 0$ )  
all nodes but reference
- 4) Solve the resulting equations

⇒ For simplicity, assume all currents are leaving the node.

Example

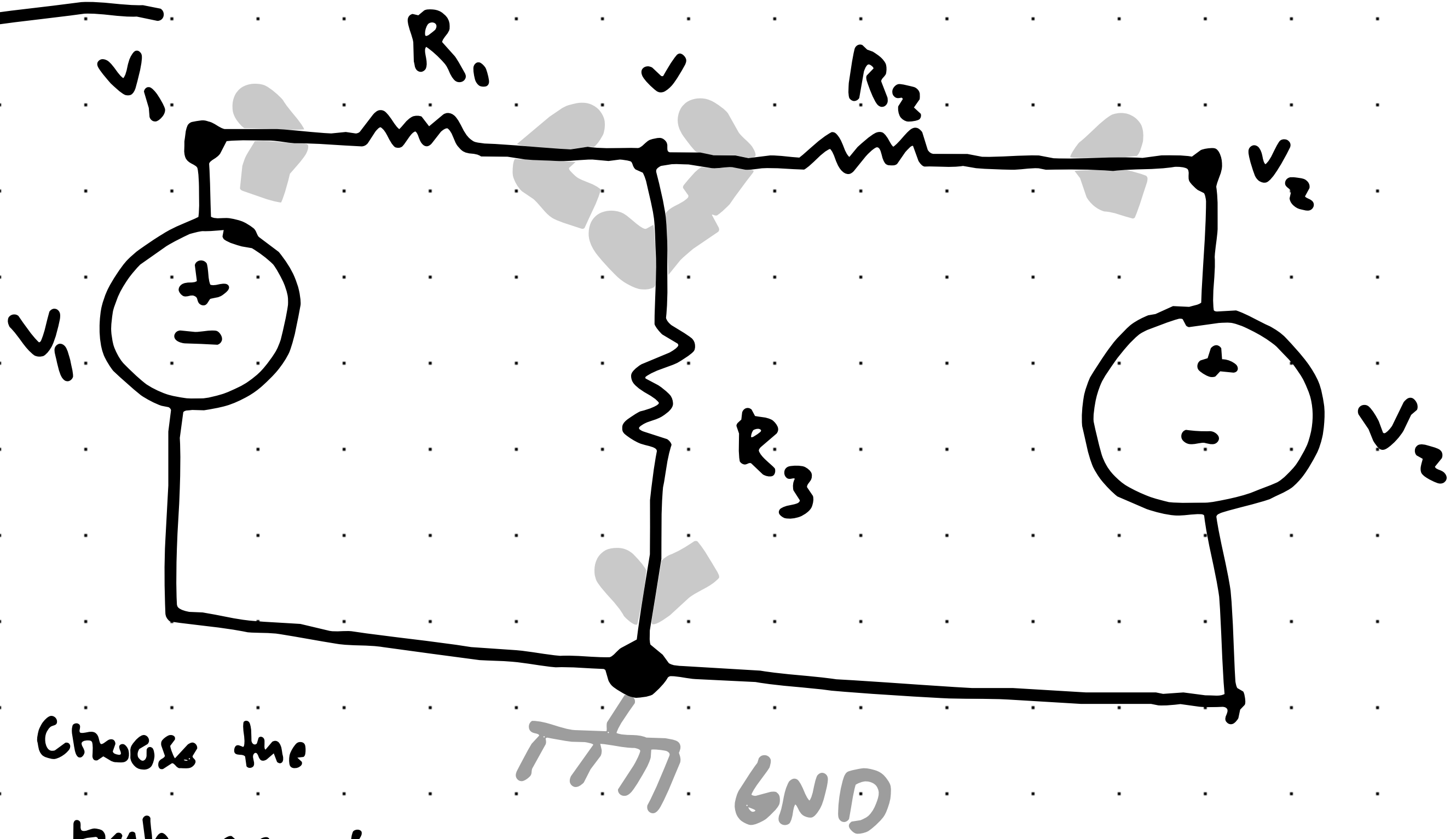

We'll choose the bottom node as the reference, for simplicity, and it is connected to most sources.

$$\sum I = 0$$

Note ①


$$\frac{V - V_1}{R_1} + \frac{V - 0}{R_3} + \frac{V - V_2}{R_2} = 0$$

We only have one unknown here!


Pretty Sweet!
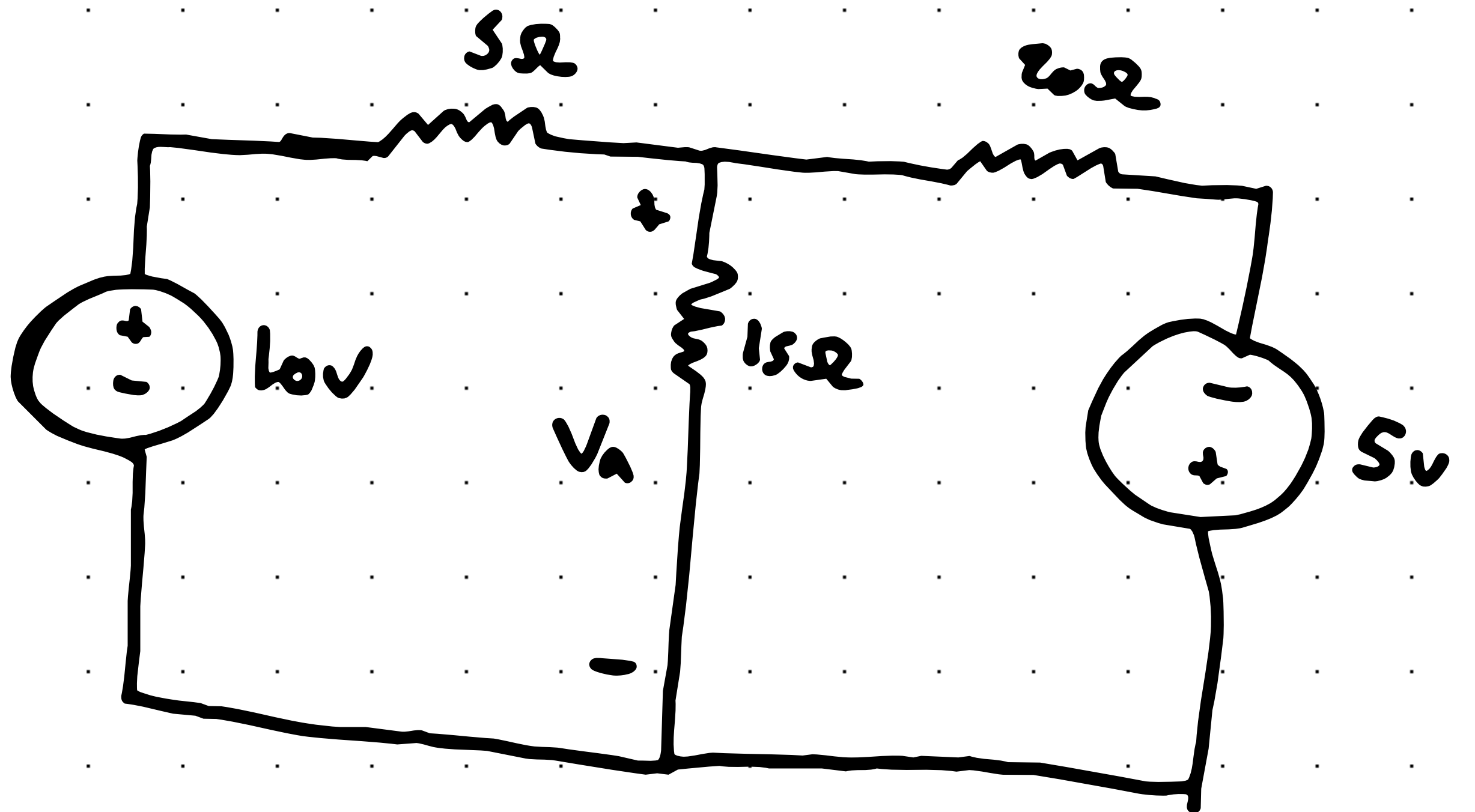
## Example 2

- Use Nodal Voltage method to calculate  $V_a$



## Solution

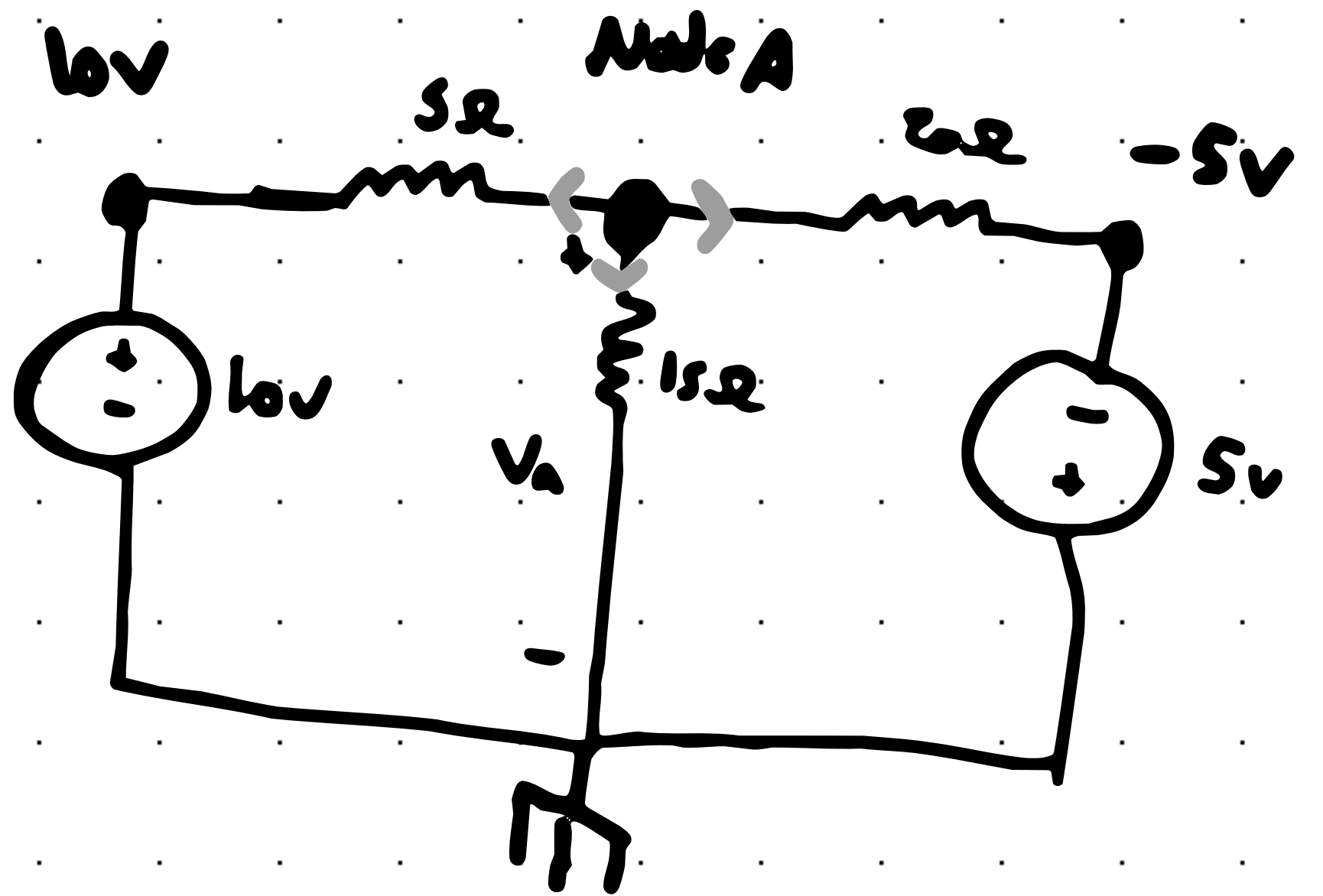

$$\sum I = 0$$

$$\text{Node A} \quad \frac{V_a - 10}{5} + \frac{V_a - 0}{15} + \frac{V_a - (-5)}{20} = 0$$

Common denominator, 60, multiply all terms by 60 and divide.



$$12(V_a - 10) + 4(V_a - 0) + 3(V_a + 5) = 0$$

$$12V_a - 120 + 4V_a + 3V_a + 15 = 0$$

$$19V_a = 105$$

$$V = \frac{105}{19} = 5.53 \text{ V}$$

# Example 3

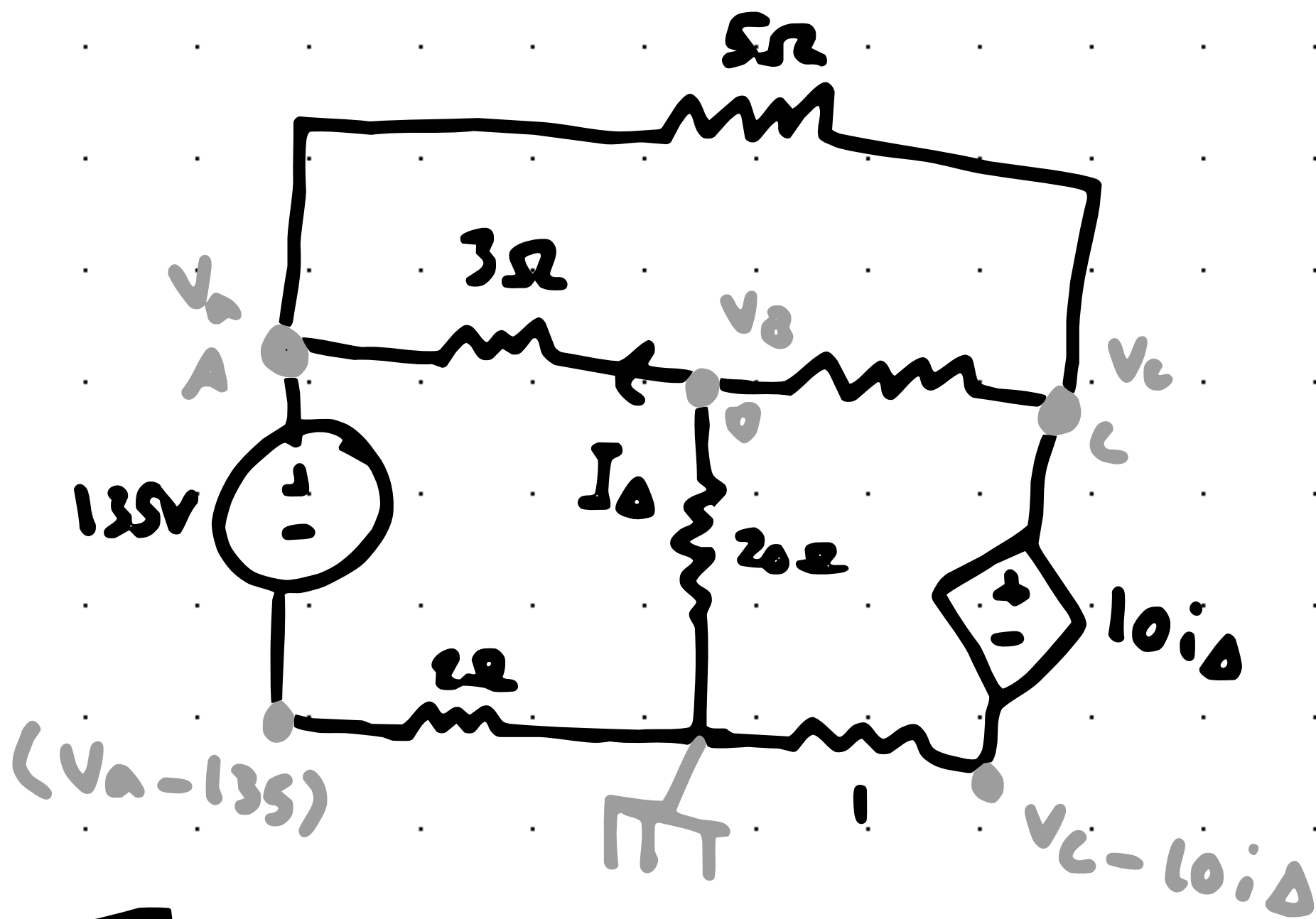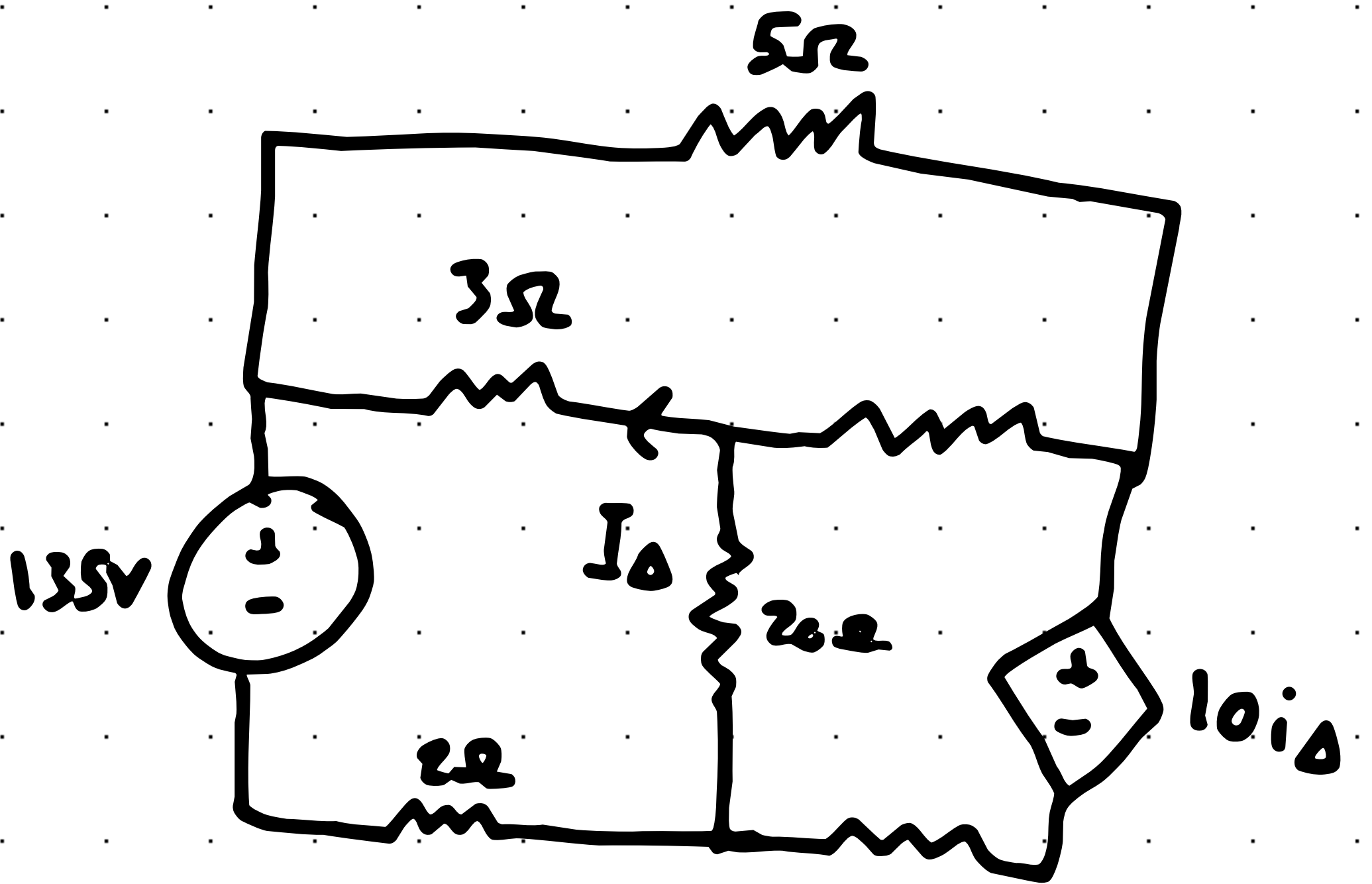

$$i_D = \frac{V_B - V_A}{3}$$

$$\sum I = 0$$

@ Node A

$$\frac{V_A - 135}{2} + \frac{V_A - V_C}{5} + \frac{V_A - V_B}{3} = 0$$

$$\sum I = 0$$

@ Node B

$$\frac{V_B - V_A}{3} + \frac{V_B - 0}{20} + \frac{V_B - V_C}{1} = 0$$

$$\sum I = 0$$

@ Node C

$$\frac{V_C - V_A}{5} + \frac{V_C - V_B}{1} + \frac{V_C - 10i_D}{1} = 0$$



