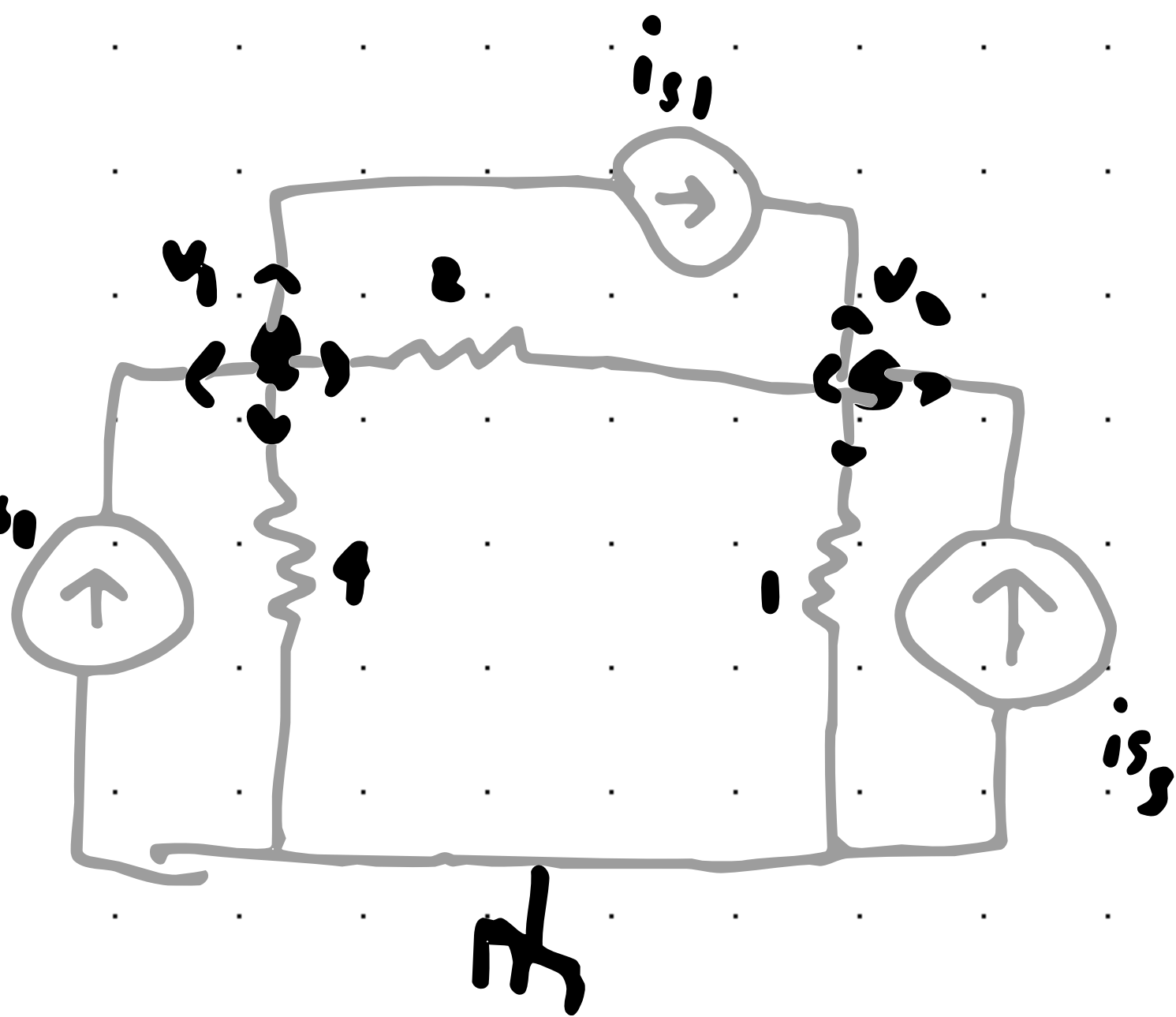


Nodal Analysis

For the following circuit, write the Node-Voltage equations.

Solution

$$\sum_{\text{Node 1}} I_{i_0} - I_{s_2} + I_{s_1} + \frac{v_1}{4} + \frac{v_1 - v_2}{2} = 0$$

$$\sum_{\text{Node 2}} = -I_{s_1} - I_{s_3} + \frac{v_1}{1} + \frac{v_2 - v_1}{2} = 0$$

$$\left(\frac{1}{4} + \frac{1}{2}\right)v_1 + \left(-\frac{1}{2}\right)v_2 = i_{s_2} - i_{s_1} \quad (1)$$

$$\left(-\frac{1}{2}\right)v_1 + \left(\frac{1}{1} + \frac{1}{2}\right)v_2 = i_{s_1} + i_{s_3} \quad (2)$$

$$\left(\frac{1}{4} + \frac{1}{2}\right)v_1 + \left(-\frac{1}{2}\right)v_2 = i_{s_2} - i_{s_1} \quad (1)$$

$$\left(-\frac{1}{2}\right)v_1 + \left(\frac{1}{1} + \frac{1}{2}\right)v_2 = i_{s_1} + i_{s_3} \quad (2)$$


$$\begin{bmatrix} \frac{1}{4} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{1} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_{s_2} - i_{s_1} \\ i_{s_1} + i_{s_3} \end{bmatrix}$$

This is known as the
Cramer's method!

Conductance ($G = \frac{1}{R}$ resistors)


→ Aly doesn't
like this method
that much, but
still wants to
do it.

Essential Node:

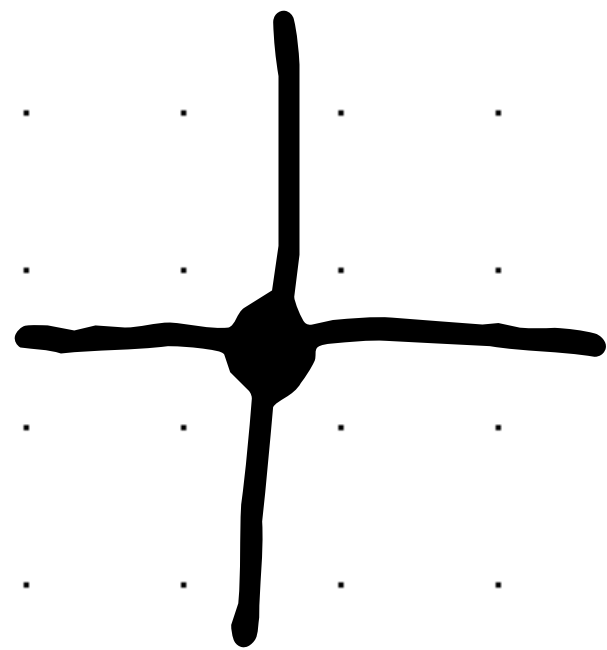

Any node that has three, or more, branches connected together.

Super Node:

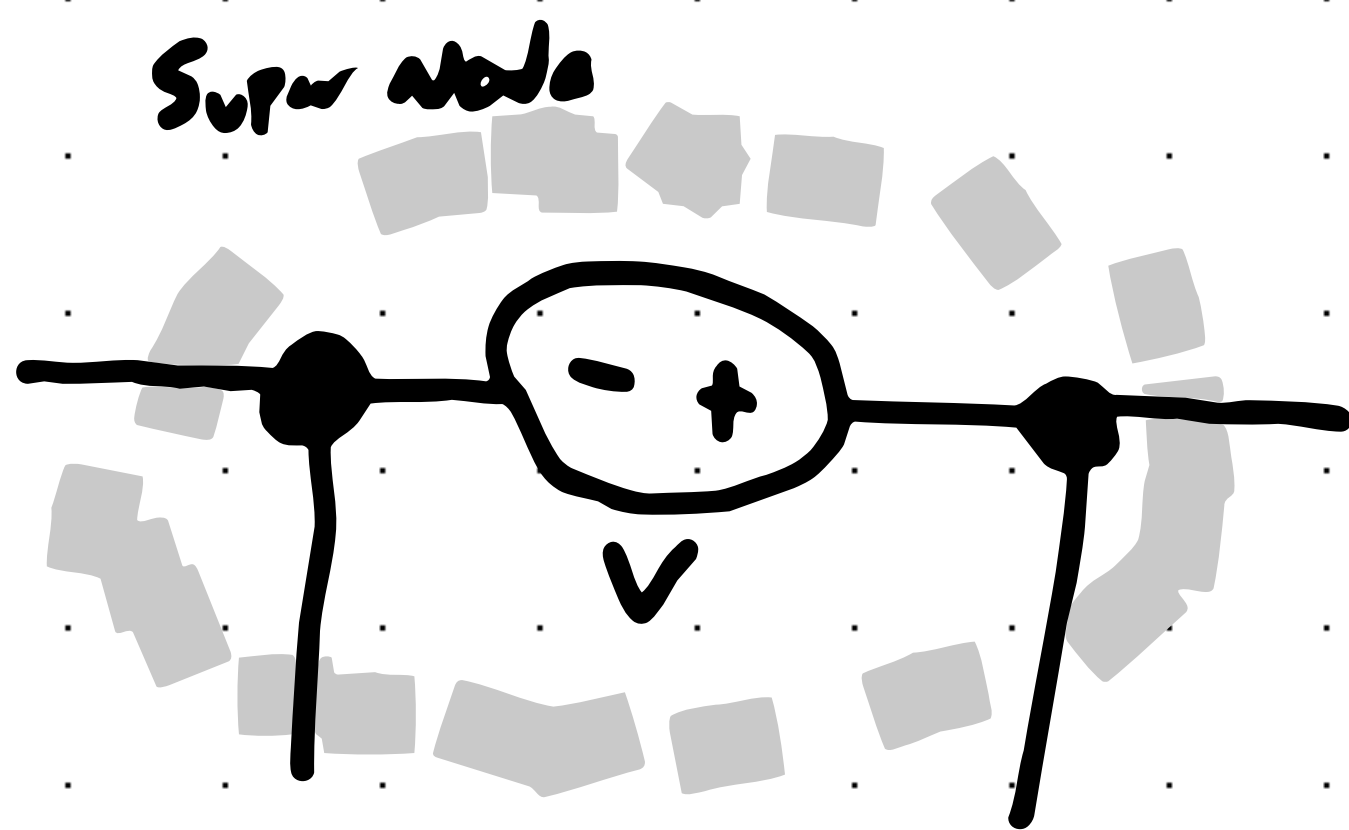


Any two nodes in between a voltage source

There is a proof to say that

$$\sum I = 0 \text{ for the entire Super node.}$$

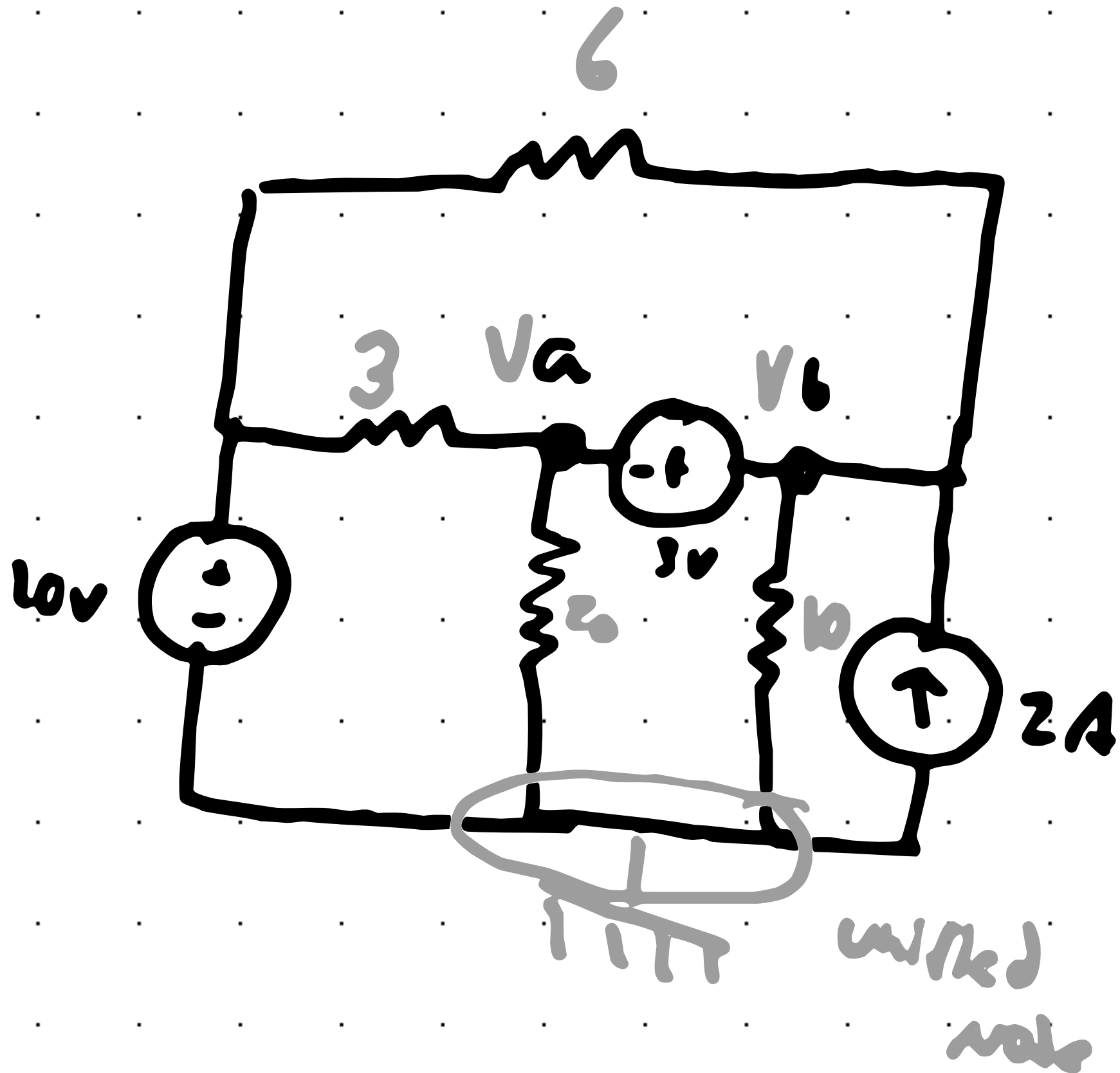Example

Use Node Voltage Method to Calculate the Value of V_c



Solution

$$\sum I = 0 \text{ Node } \textcircled{a} = \frac{V_a - 10}{3} + \frac{V_a}{20} + i_s = 0 \quad \textcircled{1}$$

$$\sum I = 0 \text{ Node } \textcircled{b} = -i_s + \frac{V_b}{6} + (-2) + \frac{V_b - 10}{6} = 0 \quad \textcircled{2}$$

Now substitute i_s

$$\frac{V_a - 10}{3} + \frac{V_a}{20} + \frac{V_b}{6} + (-2) + \frac{V_b - 10}{6} = 0 \quad \textcircled{3}$$

$$V_b - V_a = 3 \quad \textcircled{4}$$

Now Solve these...

$$\frac{V_a - 10}{3} + \frac{V_a}{20} + \frac{V_b}{10} + (-2) + \frac{V_b - 10}{6} = 0 \quad (3)$$

$$V_b - V_a = 3 \quad (9)$$

$V_a = 10.91V$

However, there is an easier way to do this....


Recognize the super node in between V_a and V_b

$\sum I = 0$, Super node

$$\frac{V_a - 10}{3} + \frac{V_a}{20} + \frac{V_b}{10} + (-2) + \frac{V_b - 10}{6}$$

Wow! That's the same equation as the one from both initial equations!

Example

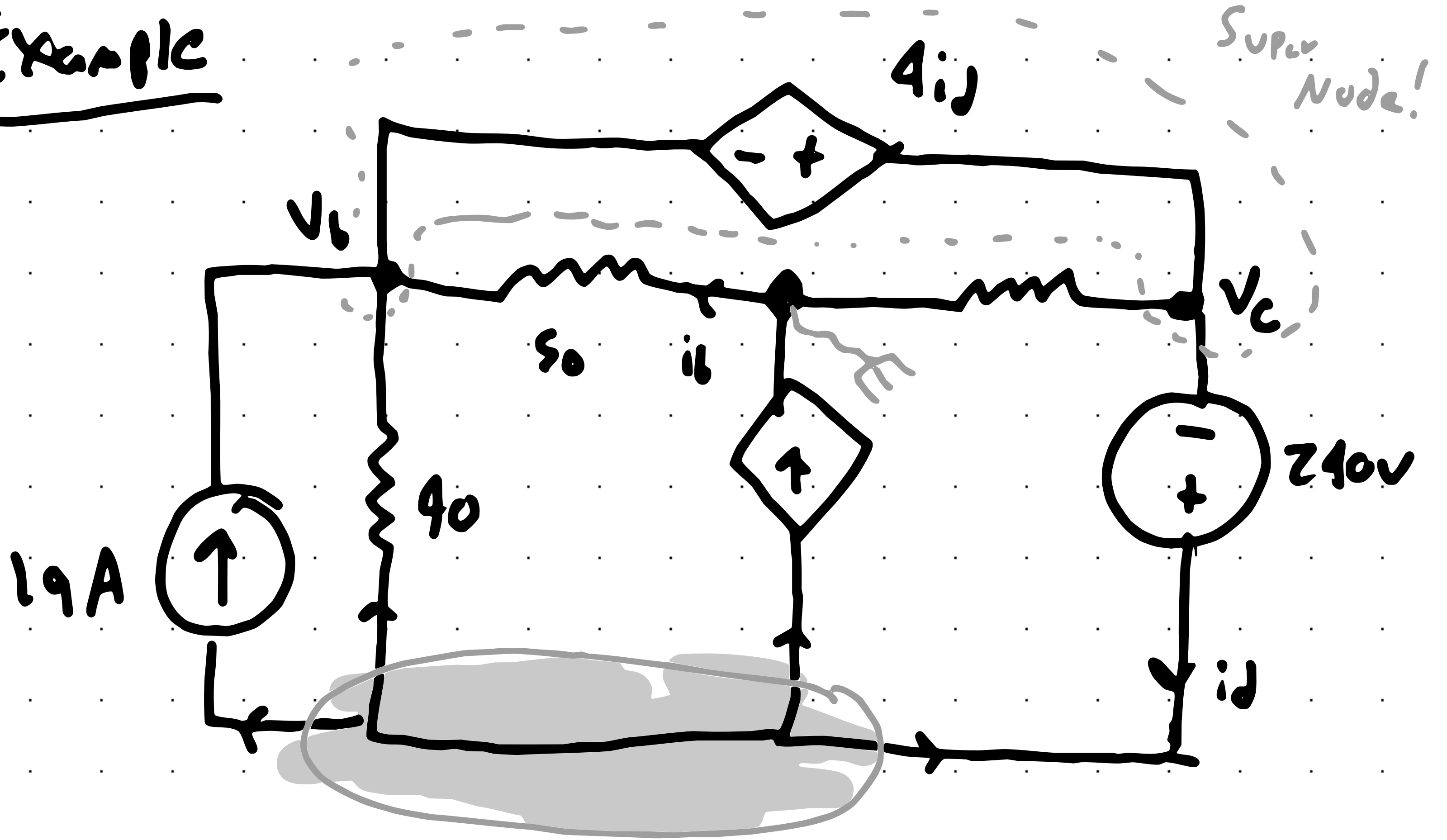

Solution

Node a
(V_a)

$$\sum I = 0 \quad \text{Node a}$$
$$19 + \frac{V_a - V_b}{40} + 2i_b + (-i_j) = 0$$

Super Node

$$\sum I = 0$$
$$-19 + \frac{V_b - V_a}{40} + \frac{V_b - 0}{5} + i_j + \frac{V_c}{5} = 0$$

$$V_c - V_b = 4i_j$$

$$i_b = \frac{0 - V_b}{5}$$

$\sum I = 0$
node c

$$i_d = 2i_b + \frac{V_a - V_b}{40} + 19$$